

Assembly Manual for the

# VHF Wattmeter

PLEASE READ DISCLAIMER CAREFULLY AS WE CAN ONLY GUARRANTEE PARTS AND NOT THE LABOUR CONTENT YOU PROVIDE

**K-6316** 

Reproduced in part by arrangement with Electronics Australia, from their June 1986 Edition.

Are you getting the most out of your VHF rig? This VHF wattmeter measures RF power to 150W in both forward and reverse directions so that you can calculate SWR and check the efficiency of your antenna system.

Sooner or later, every amateur wants to measure transmitter power and transmission line SWR. Power measurements are particularly important when checking or servicing a transmitter to ensure that the unit is capable of delivering its rated power. But it is not enough to simply adjust the transmitter for maximum power output. It is also necessary to ensure that as much power as possible is radiated by the antenna. For this to occur, the antenna must be arranged to present the correct impedance match to the transmission line. In amateur installations, the most commonly used form of transmission line is  $50\Omega$  coaxial cable. So, in order to match the cable, the input impedance of the antenna must also be  $50\Omega$ . Assum-

ing that the antenna is also resonant at the transmitter frequency, it will appear as a purely resistive load and will accept all of the RF energy arriving via the transmission line. Now consider a situation where the antenna impedance does not match the transmission line — that is, we have an impedance mismatch. This could be due to the antenna not being resonant at the frequency of interest or due to mismatch at the feedpoint. Depending upon the degree of mismatch, part of the RF energy will now be reflected by the antenna and will travel back down the line towards the transmitter. Thus, only part of the transmitted RF energy will be transferred to the antenna and subsequently radiated. This is an undesirable situation because the reflected power tends to be dissipated in the cable, even if it is subsequently reflected back up the line by the transmitter. In cases of severe mismatch, damage may even occur to the output stage of the transmitter. And the greater the degree of impedance mismatch, the greater the reflected power and the greater the risk of damage.



The VHF Wattmeter can measure RF power to 150W in both forward and reverse directions.

## Standing waves

Between them, the forward and reflected power components create standing waves in the transmission line. By measuring the forward and reflected power components, we can calculate the standing wave ratio (SWR) from the Text and Illustration courtesy of Electronics Australia following equation:

(1). SWR =  $(\sqrt{Pf} + \sqrt{Pr})/(\sqrt{Pf} - \sqrt{Pr})$ where Pf and Pr are the forward and reflected powers respectively.

What does this mean in practice? Just this — in an ideal situation, the reflected power is zero and thus the SWR is equal to 1. This, in turn, means that the antenna is correctly matched to the transmission line and that the antenna system is operating at maximum efficiency.

In practice, the ideal situation is never achieved. Instead the aim is to tune the antenna for an SWR as close to 1 as possible. For a small amount of mismatch, the SWR will be around 1.1 or 1.2, increasing for a serious mismatch to 3 or beyond.

#### What the figures mean

In order to get some feel for the figures involved, let's take a look at a practical situation. Let's suppose that we have an SWR of 3 and that we're shooting 100W "up the stick". By substituting in equation 1, the reflected power turns out to be a quite substantial 25W.

From there, the situation deteriorates quite rapidly. For an SWR of 4, the re-

flected power is 36W, while for an SWR of 10, the reflected power rises to a massive 67W. Of course, some of this power will be reflected back to the antenna at the transmitter end but, by the time cable losses are taken into consideration, it adds up to a very serious loss indeed.

## How it works

The VHF Wattmeter described here was developed by Gil McPherson, VK2ZGE for Dick Smith Electronics. Basically, it is an insertion type RF wattmeter capable of measuring power in both forward and reverse directions into a 50 $\Omega$  load. These measurements are then used to calculate SWR, thus doing away with the fiddly controls and complex scales normally required on an SWR meter.

In fact, there are only two scales on the Dick Smith VHF Wattmeter: 0-30W and 0-150W. A switch selects the re quired power range.

Fig.1 shows the basic scheme of the VHF Wattmeter. Despite its rather strange appearance, the principle of operation is quite straightforward.

This type of device often goes under the high falutin' name of SWR Reflectometer and employs what are known as microstriplines. A microstripline is simply a type of transmission line. It consists of a narrow conductor strip which runs parallel to a ground plane.

In Fig.1, we have two parallel microstriplines and these are arranged sufficiently close to each other to ensure that they are lightly coupled by virtue of their distributed mutual inductance and capacitance. As can be seen, one of these microstriplines is connected between the transmitter and the antenna while the other drives a rectifier diode and meter movement.

Here's what happens: When RF current flows down the "primary" microstripline towards the antenna, an induced RF current flows in the opposite direction in the secondary stripline. This current is then rectified and used to drive the forward meter movement.

Note, however, that current flowing in the secondary due to any reflected power is blocked by the diode and so does not affect the meter. Instead, the power is dissipated in load resistor Ra which is matched to the characteristic impedance of the secondary line.

To monitor the reflected power, we need to add a complementary secondary microstripline. Fig.2 shows the basic

require is necored ing that the anticitiants and remain of	- second in the rises whether the rest. Tarted to tomore
substitute for the second second and the former of the second sec	
also are granting regress and the second attempt our	



Fig.4: parts layout and wiring diagram for the VHF Wattmeter. Page 2 Text and Illustrations courtesy of Electronics Australia physical arrangement. The microstriplines themselves consist of strips of copper etched on one side of a small PCB, while the unetched copper laminate on the other side of the board forms the ground plane.

It's now only a short step to the final circuit shown in Fig.3. Both the forward and reverse microstriplines are present as in Fig.2, but their outputs are now switched (via S1) to a common meter movement.

The primary microstripline connects to the antenna feedline via two SO239 sockets. The impedance of the primary stripline is  $50\Omega$  while the secondary microstriplines have a characteristic impedance of 75 $\Omega$  and are thus terminated with 75 $\Omega$  load resistors.

Diodes D1 and D2 are Schottky types which are necessary to ensure good performance at 144MHz. The rectifier outputs are filtered by C1L1 and C2L2 respectively, and applied to S1 via 20k $\Omega$ calibration trimpots (VR1 and VR2). S2 selects either the 0-30W or 0-150W ranges while VR3 provides calibration of the 150W range.

## Construction

Three small printed circuit boards are used in the VHF Wattmeter assembly. The microstriplines are etched onto a PCB coded ZA1663A (120 x 50mm) and this board also holds the 75 $\Omega$  resistors, feedthrough capacitors and Schottky diodes. A second board coded ZA1663C (100 x 20mm) accommodates the trimpots and switches. The third board is coded ZA1663B and measures 74 x 50mm. It consists of a piece of single-sided unetched PCB laminate and serves as a cover plate for the microstripline PCB (ZA1663A). Begin assembly by installing the resistors and diodes. Note that the bodies of these components fit into four cutout areas and that the leads must be soldered on the top (microstripline side) of the PCB. This done, the two feedthrough capacitors can be mounted. One lead of each capacitor is soldered directly to the cathode of its corresponding diode while the earth disc is soldered direct to the top of the PCB. The remaining (looped) lead is subsequently used to terminate flying leads. The next step is to fit ten PC stakes (five at either end) through unused holes in the earth pattern of the PCB (see wiring diagram). These stakes should be soldered to both sides of the board using generous amounts of solder. This step is designed to provide a low-impedance path between the earth pattern on the top of the PCB and the groundplane on the other side. Construction of the microstripline PCB assembly can now be completed by installing the cover plate PCB. The two boards are fastened together using four 12mm nylon screws and nuts. Note that the copper laminate on the plate



Fig.3: the forward and reverse microstriplines are switched to a common meter.



Above: view inside the completed instrument showing the microstripline assembly.



Above: this view shows the completed microstripline PCB with the cover plate attached.

PCB faces outwards and that the two boards must be separated slightly by installing an insulating shim (Melinex paper, cut to the size of the coverplate PCB) between the microstripline PCB and the coverplate PCB. (see Fig. 5)

Once the microstripline assembly has been completed, attention can be turned to the remaining board. Install PC stakes at the two external wiring points, then mount the trimpots and switches. Note that the switches are soldered directly to the underside of the PCB.

The remaining component, capacitor C3 (.001uF), is soldered directly across the meter terminals. Install the capacitor as shown in Fig. 4, together with two 70mm-long flying leads.

Text and Illustrations courtesy of Electronics Australia Page 3

## Final assembly

The VHF Wattmeter is housed in a black aluminium case, with the input and output BNC sockets mounted on the rear panel. Fig.5 shows the rear panel assembly details. Note that the tinplate bracket is used to provide a reliable earth connection between the sockets and the microstripline assembly.

The assembly procedure is as follows:

(1). Mount the tinplate bracket and sockets and secure them using nuts and washers.

(2). Push the microstripline assembly down onto the socket terminals as far as it will go and solder the terminals to the pads.

(3). Working through the meter cutout, run a rivet of solder between the tinplate bracket and the adjacent earth pattern at both ends of the microstripline PCB.

(4). Attach flying leads to the PC stakes on the switch PCB and mount the assembly on the front panel. Trim the flying leads to length, slip a ferrite bead over each of the free ends, and solder the leads to the feedthrough capacitors on the microstripline assembly. Glue the ferrite beads in position using a dab of epoxy adhesive.

(5). Mount the meter and solder the flying leads to the switch PCB and tinplate shield as shown in Fig.4.

## Calibration

There are two ways of calibrating the VHF Wattmeter; (1) by following the basic calibration procedure outlined below; or (2) by calibrating against a known reference. No specialised RF test equipment is required for the basic calibration procedure which gives sufficient accuracy to allow relative power measurements to be performed. However, you do require a 3-10V variable DC supply, a multimeter (preferably digital), and a 100 $\Omega$  0.5W resistor.



The two front panel switches are soldered directly to the underside of the trimpot PCB.



The basic calibration procedure is as follows:

(1). Set the power supply to 3.7V as measured on the multimeter.

(2). Connect the  $100\Omega$  resistor in series with the positive lead from the power supply.

(3). Connect the negative supply lead to the tinplate bracket in the wattmeter.

(4). Set the direction switch to reverse
(ie, to the left) and the range switch to
the 30W position, and connect the
power supply positive lead (via the
100Ω resistor) to non-earth side of R2.
(5). Adjust trimpot VR2 for full scale
deflection on the meter.

(6). Disconnect the supply lead from R2, set the direction switch to forward, and connect the supply lead to the non-earth side of R1.

(7). Adjust trimpot VR1 for full scale deflection.

(8). Set the range switch to the 150W proce Page 4 Text and Illustrations courtesy of Electronics Australia

Fig.5: rear panel assembly details. The copper side of the cover plate faces outwards.



position and wind up the power supply to 9V as measured at the supply terminals.

(9). Adjust VR3 for full scale deflection on the meter, then disconnect the lead to R1.

That completes the basic calibration procedure which should give sufficient

accuracy for most uses. Alternatively, if greater overall accuracy is required. Dick Smith Electronics will calibrate your completed wattmeter against a Bird Model 43 Throughline Directional Wattmeter, an industry standard instrument

tronics Australia

## How to use it

In a practical system, the forward and reflected power components vary along the length of the transmission line due to line losses. This means that the SWR is not constant along the transmission line but reduces progressively as one moves back from the antenna to the transmitter. Not surprisingly, the amount of this reduction depends upon the losses contributed by the line.

Because it is the antenna-feedline match that is of interest, there is only one correct place to make SWR measurements: as close as possible to the antenna end of the feedline. Unless feedline losses are quite small, any measurements taken at the transmitter end will be quite misleading.

An example will serve to illustrate the point. Let's say that transmission line losses are 3dB and that the antenna mismatch is such that the SWR is 2:1. Thus, if 100W is fed up the line, only 50W reaches the antenna due to line losses.

By substituting in equation 1, we find that only 44.4W will be delivered to the antenna while 5.6W will be reflected down the line. And, because of the 3dB line loss, only half this reflected power will reach the transmitter, ie. 2.8W.

Thus, inserting the wattmeter at the transmitter end results in a forward reading of 100W and a reverse reading of 2.8W. If we plug these figures into equation 1, we get a quite acceptable

## lanag balang melalang panel

mismatch.

It gets worse as cable losses increase. In the foregoing example, a 6dB line loss would result in a measured SWR at the transmitter end of only 1.18:1, while a seriously mismatched antenna with an SWR of 3:1 (6dB line loss) will still only give an SWR of 1.29:1 at the transmitter.

The message is clear. If you want to make accurate SWR measurements, in-

stall the wattmeter at the antenna end of the feedline.

Finally, in cases of serious mismatch, it will be necessary to make adjustments to the antenna. For example, it may be necessary to employ an antenna tuning unit (ATU), a matching transformer or to make adjustments by one means or another to the antenna itself. The exact approach will vary according to the installation.



SWR figure of 1.46:1. This is significantly less than the real figure of 2:1, the latter representing a fairly serious

the latter representing a fairly serious The rear panel accommodates the two SO-239 sockets (socket 1 right; socket 2 left).

	PARTS LIST	
R	esistors	100
2x	75R Resistors C/Carbon(R1,R2)	
Ca	apacitors	J.R.M
2x 1x	1000pF F/Through Cap <b>(C1,C2)</b>	
Se	emiconductors	
1x	20K/25K Trimpot(VR1,VR2)	
M	iscellaneous	
Ins	rrite Bead, sockets, toggle switches, screws, nuts, PCB pins, H/U wire, sulating shim, solder, PCB (set of three), case & ends, panel meter, VHF eter face, tin plate bracket, Power Chart	「「「「」」の「「」」の「」

## CHANGING METER PANEL

Unscrew the two phillips-head screws located at either side of the meter panel. Once these screws are removed the meter face will come off with just a little persuasion.

To remove the scale plate, another two small phillips-head screws will have to be removed. These are located either side of the moving coil. Once removed, slide the scale plate away from the meter needle. Care must be taken when changing the panels, as damage may be caused to the coil unless the panels are slid into position. Having attached the new meter face, installation is simply the opposite procedure to the above.



	This coupon will enable customers to return their fully constructed K-6316 VHF Wattmeter to our Service Department,
	together with a calibration of only \$15.00. All kits
	received must be in working condition and we reserve the
	right to return faulty kits uncalibrated with the \$15.00. A Bird Model 43 Throughline RF Directional Watt Meter,
	with an accuracy of within 5% will be used as the standard.
	NAME
93	ADDRESS
	POSTCODE PHONE
	DATE KIT PURCHASED PURCHASED FROM
	I AM A - COMPLETE BEGINNER HOBBYIST EXPERIENCED
	I have included the \$ 15.00 calibration fee.

## **STORE LOCATIONS**

HEAD OFFICE & DS XPRESS ORDER SERVICE P.O. Box 321, North Ryde, N.S.W. 2113. Tel (02) 888 3200 AUSTRALIA.

McPacific Hwit         Gold Hill         (02)         439 5311         For Facility of a 100 (01)         229 9377         For Facility of a 100 (01)         Augkland City         (07)         38 9974           315 March 51         Gasterid         (043)         25 0235         Facility of a 100 (07)         39 4293         Hamilton         (07)         39 4293         Hamilton         (07)         39 4493         Line	
St Woode (a.e.)         Bankstown So         (32)         107 4080         bankstown St         Coourg         (03)         383 4455         NI           Incol 1 05/15/101 9         Blockhown         (02)         55 female 12         Coourg         (03)         383 4455         NI           C13 Princes Hw         (02)         56 7744         Female 12         Frankston         (03)         370 7444         Frankston         (03)         763 9144         Frankston         (03)         763 9144         Frankston         (03)         763 9144         Frankston         (03)         77 913         New Zealand         New Zealand         New Zealand         New Takes Frankste         (09)         373 913         New Takes Frankste         (09)         373 913         New Takes Frankste         New Takes Frankste	

Text and Illustrations courtesy of Electronics Australia