

**APPLICATION NOTE**

**Behaviour of Circulators under  
practical conditions**

**AN98034**

## 0. Contents

1. Introduction	1
2. Measuring circulator data	1
2.1 Isolation	1
2.2 Input reflection	4
2.3 Insertion loss	9
3. Some applications	14
3.1 Reduction of the vswr or return loss of a load by using an isolator	14
3.2 Behaviour of the input vswr or return loss of a circulator terminated with a filter	17

## 1. Introduction

The data of circulators and isolators given in the data sheets or other publications assume, that all ports of the device are matched with the nominal impedances of the lines. When measuring the devices or in the application these impedances will deviate from the ideal matching, often very drastically. Therefore we will investigate what happens when we use not ideal loads and equipment to measure circulators and isolators, and how these devices behave in the practical environment.

## 2. Measuring circulator data

### 2.1 Isolation

When measuring the isolation of a 3-port-circulator we connect one port with the source, on the next port in the sense of circulation we put a matched load, and the third port is connected to a detecting device (Figure 1). This technique can be done with low signal level but also with high power. For

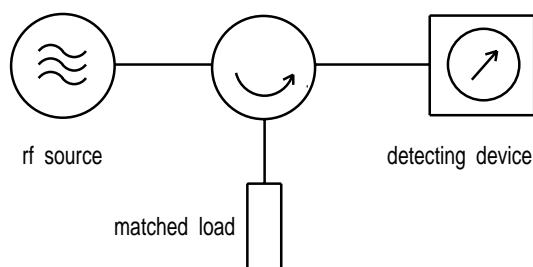


Fig.1: Measurement of isolation

low level measurements we can use also a network analyzer, connecting two ports to it and the remaining port gets a matched load.

The "matched load" used for terminating one port is not an ideal matching but has a small vswr  $s_{load}$ . This small reflection superimposes the signal caused by the not ideal isolation of the circulator. Therefore we measure a combination of the circulator isolation and the vswr of the connected load, the value of which depends on the phase between the two signals. The minimum value of isolation is measured when both signals add, the maximum when the signals subtract one from the other.

For the calculation we convert the isolation of the circulator  $D$  into an equivalent vswr  $s_D$ . Then we combine the vswr of the load  $s_{load}$  and  $s_D$  to the maximum and minimum vswr of both ( $s_{meas\ max}$  and  $s_{meas\ min}$ ) and convert these back to the extremes of the measured isolation  $D_{meas\ max}$  and  $D_{meas\ min}$ :

$$s_D = \frac{1 + \frac{1}{10^{\frac{D}{20}}}}{1 - \frac{1}{10^{\frac{D}{20}}}}$$

$$s_{meas\ min} = s_D \times s_{load}$$

$$s_{meas\ max} = s_D / s_{load} \quad \text{if } s_D / s_{load} \geq 1$$

$$s_{meas\ max} = s_{load} / s_D \quad \text{if } s_D / s_{load} < 1$$

$$D_{meas\ max, min} = 20 \lg \frac{s_{meas\ max, min} + 1}{s_{meas\ max, min} - 1}$$

These correlations between maximum and minimum measured isolation  $D_{meas}$ , the real isolation of the circulator  $D$ , and the vswr of the load  $s_{load}$  can be seen as a graph in figure 2. The measured isolation will lie between the upper and lower curve of the relevant load vswr.

If for example we use a load with a vswr of  $s_{load}=1,02$  and the isolation of our circulator is 25 dB, our measurement can lie between 23,6 and 27,6 dB.

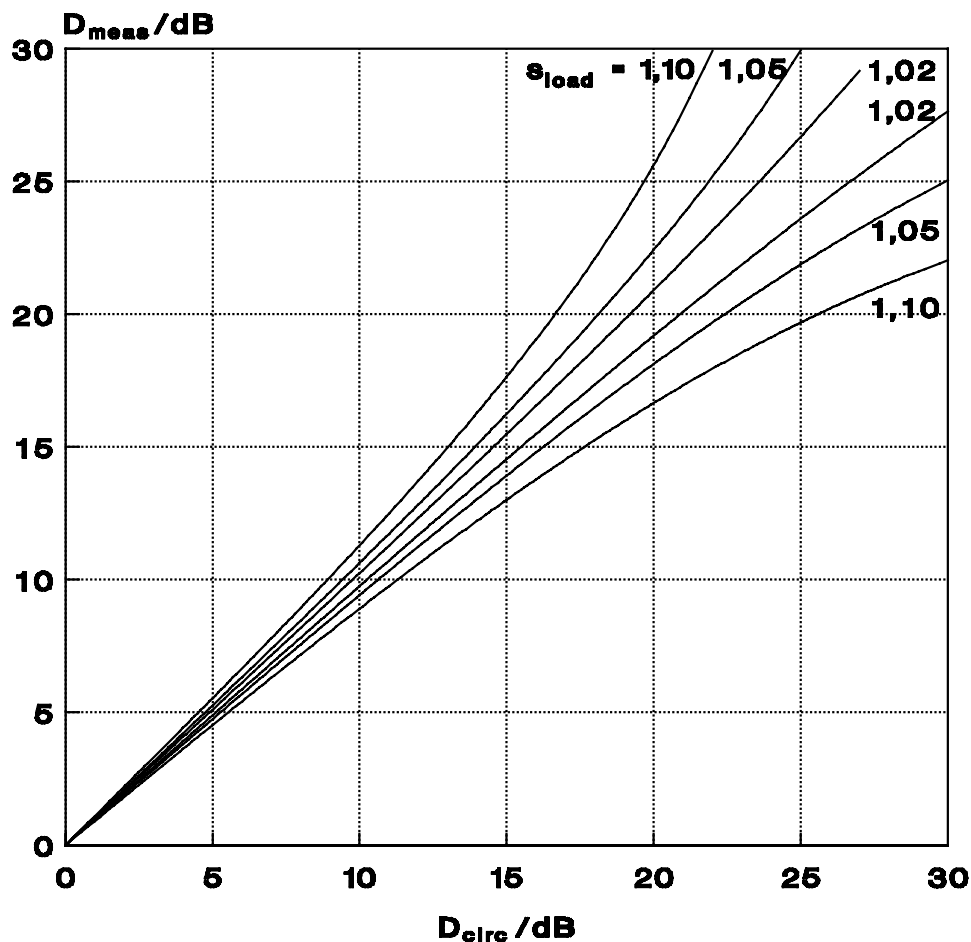


Fig.2: Measured maximum and minimum isolation as a function of the isolation of the circulator  $D_{\text{circ}}$  with the load vswr  $s_{\text{load}}$  as a parameter

To give a better idea how big the difference between the real isolation of the circulator and the measured isolation can be, figure 3 shows this difference as a function of the isolation of the circulator  $D_{\text{circ}}$  with the vswr of the load  $s_{\text{load}}$  as a parameter.

For example for a load with a vswr of  $s_{\text{load}}=1,05$  and an isolation of the circulator of 20 dB the maximum difference of the measured isolation and the real isolation of the circulator is +2,4 dB and -1,9 dB.

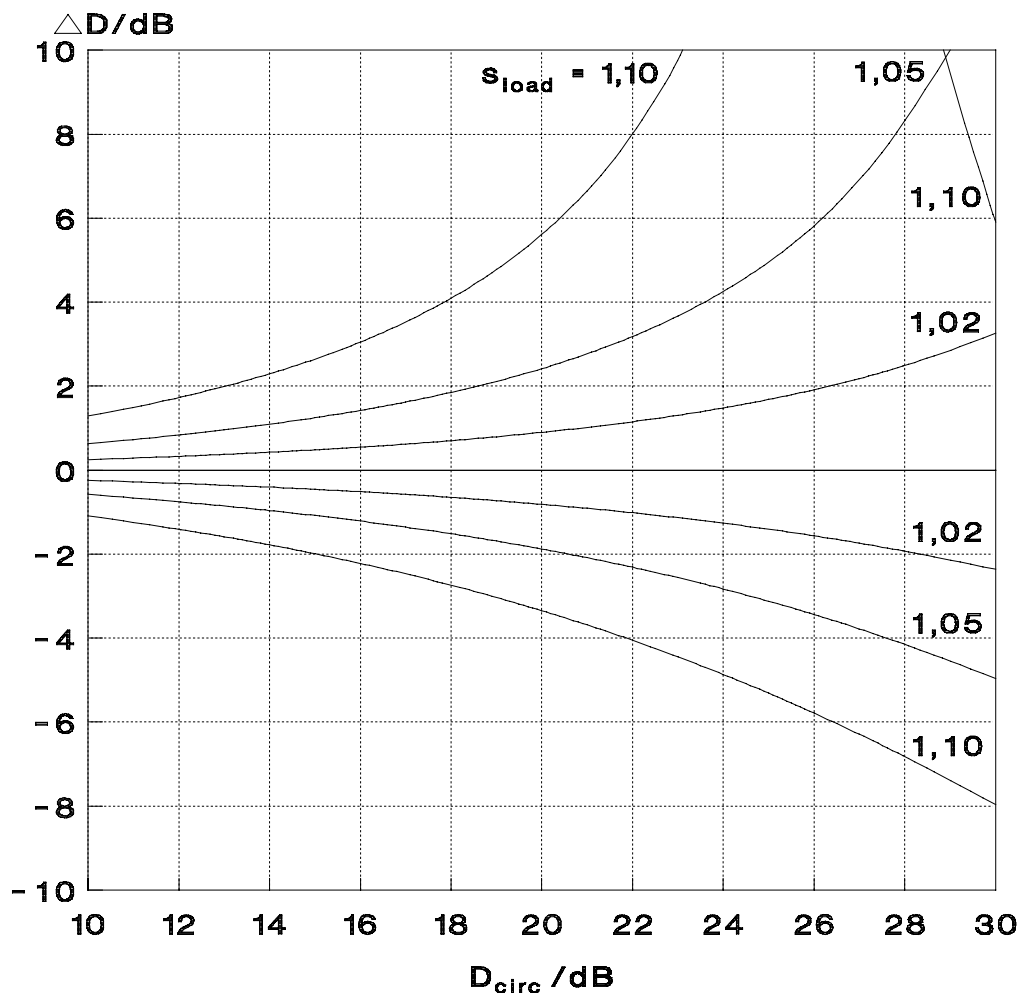


Fig.3: Maximum difference between the isolation of the circulator and the measured isolation as a function of the isolation of the circulator  $D_{\text{circ}}$  with the load vswr  $s_{\text{load}}$  as a parameter

## 2.2 Input reflection

The input reflection of the ports of a circulator is often measured by directional couplers. For low level measurements network analyzers, bridges, and slotted lines can be used too. On the ports not being measured we put matched loads, and the port being measured is connected to the directional coupler, bridge, slotted line or network analyzer. If the loads used have an input vswr lower than 1,1 we can neglect their influence on the measurement of the input reflection.

When using a directional coupler or bridge the main source of failures in this measurement is the directivity  $D_R$  of the directional coupler or bridge measured in dB. The signal resulting from the directivity combines with the signal returning from the circulator and we measure a vswr which lies between a maximum value  $s_{\text{meas max}}$  when both signals add and a minimum value  $s_{\text{meas min}}$  when the signals subtract one from the other. We can calculate these limits in the following way.

We transform the directivity  $D_R$  into the equivalent vswr  $s_D$

$$s_D = \frac{1 + \frac{1}{10^{\frac{D_R}{20}}}}{1 - \frac{1}{10^{\frac{D_R}{20}}}}$$

and now we combine  $s_D$  with the vswr of the circulator port  $s$  to the extremes  $s_{\text{meas max}}$  and  $s_{\text{meas min}}$

$$\begin{aligned} s_{\text{meas max}} &= s_D \times s \\ s_{\text{meas min}} &= s_D / s \quad \text{if } s_D / s \geq 1 \\ s_{\text{meas min}} &= s / s_D \quad \text{if } s_D / s < 1 \end{aligned}$$

This relationship is given in figure 4. In this diagram we can see, that a circulator with an input vswr of 1,25 will show figures between 1,22 and 1,28 if measured with a directional coupler or bridge having a directivity of 40 dB.

When using a slotted line the residual vswr of this line corresponds to the directivity of the bridge or directional coupler. If we transform the residual vswr  $s_D$  to the directivity

$$D_R = 20 \lg \frac{s_D + 1}{s_D - 1}$$

then we can use figure 4 for estimating the maximum failure.

When measuring the input reflection with modern network analyzers, the analyzer corrects the failure during calibration with the calibration kit. If there is no calibration kit for the line used and we have to use additional transitions, this results in measurement uncertainties.

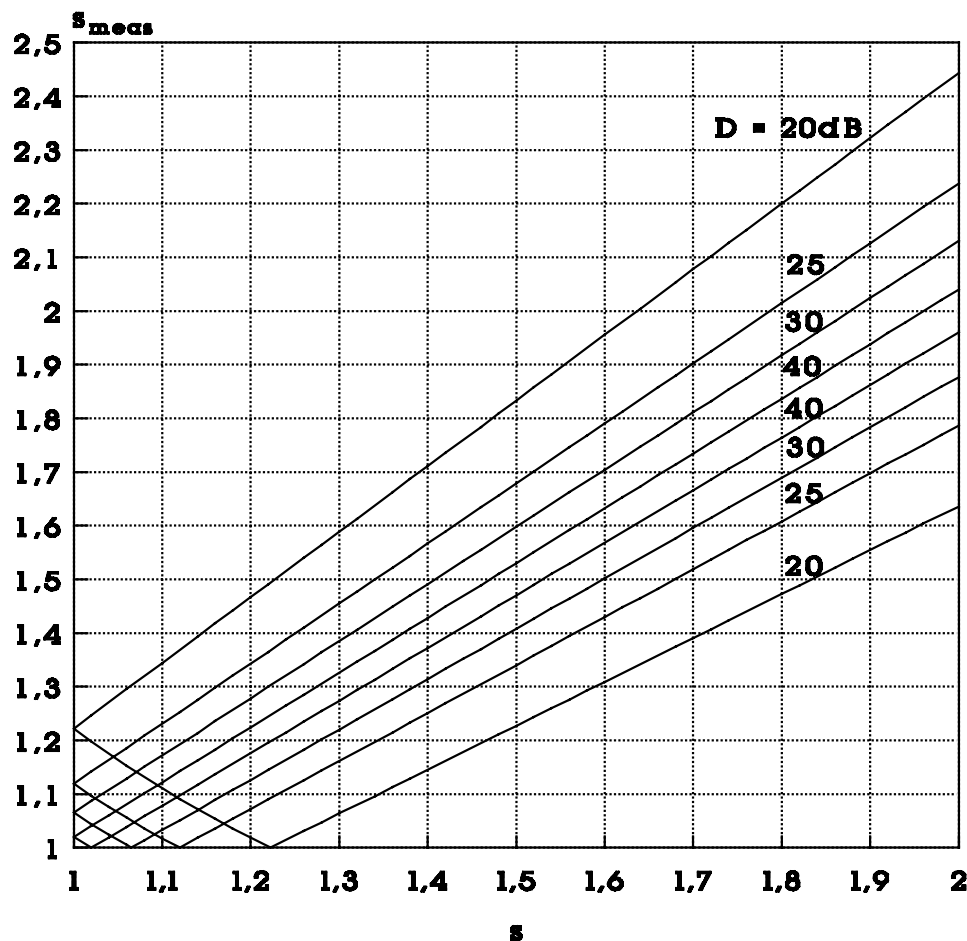


Fig.4: Measured maximum and minimum input vswr  $s_{\text{meas}}$  as a function of the input vswr of the circulator  $s$  with the directivity  $D$  of the directional coupler or bridge as a parameter

Up till now we assumed that we have a pure signal. If there are harmonics on our signal, which happens very often when measuring with power, we can get big failures. A normal circulator or isolator represents a more or less good match in its operating band, but reflects nearly all harmonics or other spurious frequencies far outside the operating band. Therefore these frequencies have to be removed by suitable filters.

To estimate the failures, which may happen, we can calculate in the following way.

If we have a harmonic  $x$  dB under our signal level and we measure with a power measuring device (e.g. a thermistor or baretter, or a diode in

the square-law-region), the harmonic power adds to the reflected power of the carrier:

reflected power of the carrier

$$P_r = P \times \left( \frac{S-1}{S+1} \right)^2$$

harmonic power, totally reflected

$$P_h = P \times 10^{-\frac{x}{10}}$$

$$S_{meas} = \frac{1 + \sqrt{P_r + P_h}}{1 - \sqrt{P_r + P_h}}$$

In figure 5 we see, that with a harmonic content of -20 dBc we will measure the vswr of a circulator to  $s_{meas}=1,31$  instead of its real value of  $s_{circ}=1,20$ .

If we measure with an amplitude measuring device (e.g. a diode in the linear region) we have to calculate the areas between the time axis and the curve resulting from the reflected original signal and the totally reflected harmonics. We get the biggest deviation for the third harmonic, which is one of the most important too.

For small vswr's of the circulator the resulting curve cuts the time axis more often than for a normal sine wave, and we have to integrate the parts. There are two extremes for the phase of signal and harmonic: they are in phase or in antiphase.

With

$$r_{circ} = \frac{s_{circ} - 1}{s_{circ} + 1}$$

$$a_3 = 10^{-\frac{x}{20}}$$

we get the following equations for a third harmonic of x dBc:

a. time axis cut also within a half sine wave of the signal

$$\omega t_1 = \arcsin \sqrt{\frac{3}{4} \pm \frac{r_{circ}}{4a_3}}$$

$$r_{meas} = |r_{circ}(1 - \cos \omega t_1) \pm \frac{a_3}{3}(1 - \cos 3\omega t_1)| +$$

$$+ |r_{circ} \cos \omega t_1 \pm \frac{a_3}{3} \cos 3\omega t_1|$$



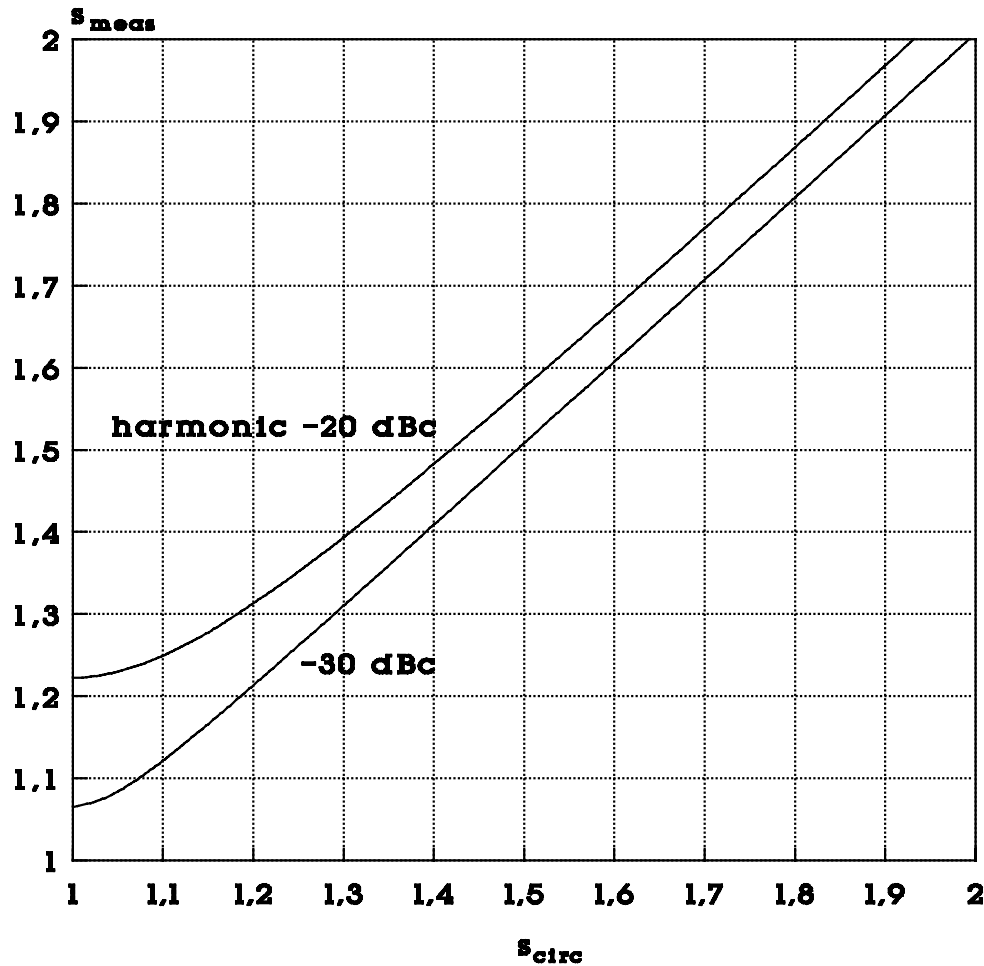


Fig.5: Measured input vswr  $s_{meas}$ , using a power measuring device, as a function of the vswr of the circulator  $s_{circ}$ , with the harmonic level as a parameter

b. time axis not cut within the half sine wave of the signal

$$r_{meas} = r_{circ} \pm \frac{a_3}{3}$$

and

$$s_{meas} = \frac{1 + r_{meas}}{1 - r_{meas}}$$

This relationship is given in the figures 6.

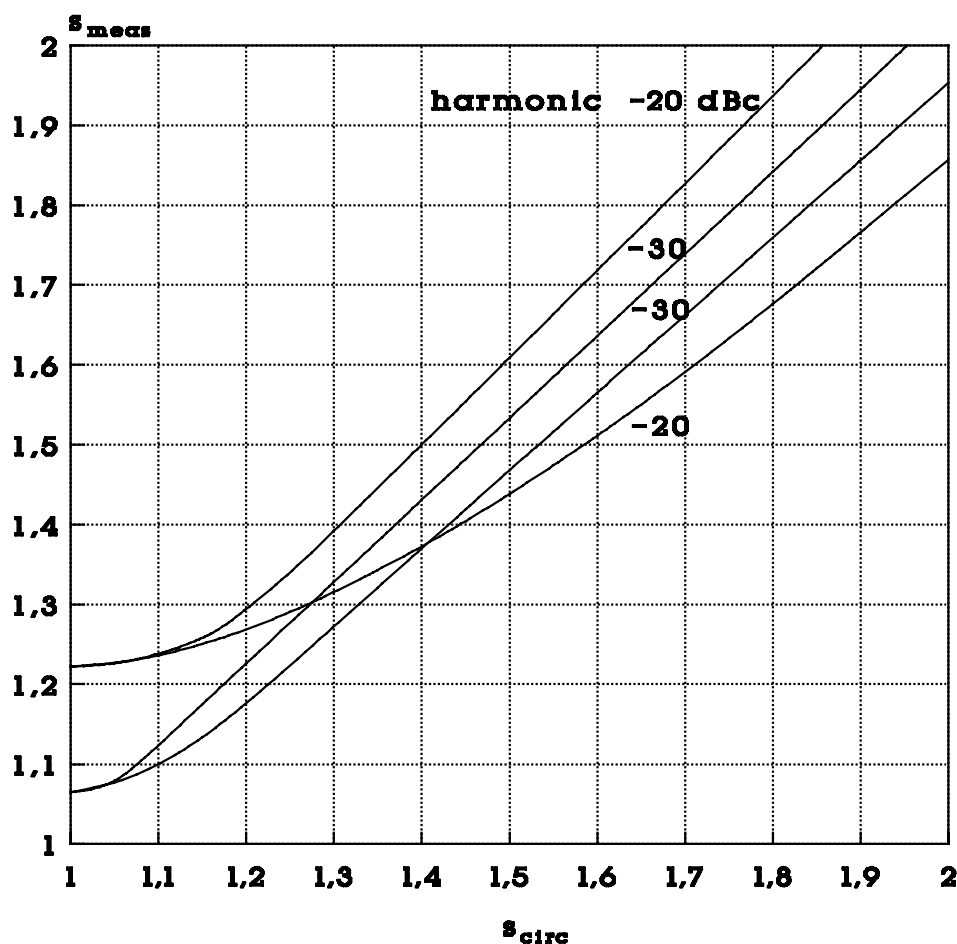


Fig.6: Measured maximum and minimum input vswr  $s_{\text{meas}}$ , using an amplitude measuring device, as a function of the vswr of the circulator  $s_{\text{circ}}$ , with the third harmonic level as a parameter

For a circulator with a vswr  $s_{\text{circ}} = 1,20$  and a third harmonic of  $-20$  dBc the reading of an amplitude measuring device may lie between  $s_{\text{meas}} = 1,31$  and  $s_{\text{meas}} = 1,27$ .

### 2.3 Insertion loss

At high power level the insertion loss of a circulator will be measured between isolators and directional couplers, similar to the measurement of the isolation, but with the circulator put in the forward direction, see figure 7. The value to be measured is very small, therefore we have to

look for some sources of failure which could be neglected when we measured the isolation. On the other hand the loads on the ports not used in this measurement do not influence the result as long as they have a vswr lower than 1,1.

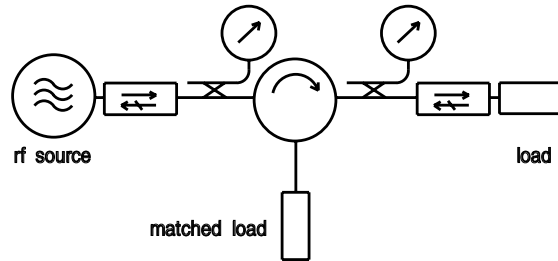


Fig.7: Measurement of the insertion loss

With  $s_i$ , the vswr of the isolators used, and  $s$ , the vswr of the circulator to be measured, we get a maximum reading of the input power  $P_{in \max}$  which deviates from the power of the generator due to the reflected waves

$$P_{in \max} = P \left( \frac{1}{1 - rr_i} \right)^2$$

with

$$r = \frac{s - 1}{s + 1} \quad r_i = \frac{s_i - 1}{s_i + 1}$$

and a minimum reading

$$P_{in \min} = P \left( \frac{1 - 2rr_i}{1 - rr_i} \right)^2$$

For this calculation we assume that the vswr of the directional couplers is very low compared to the other reflections and can be neglected. For the output power we have a maximum reading with  $d$ , the real insertion loss of the circulator

$$\begin{aligned} P_{out \max} &= P \left( \frac{1}{1 - rr_i} \right)^2 10^{-\frac{d}{10}} \left( \frac{1}{1 - rr_i} \right)^2 \\ &= P \times 10^{-\frac{d}{10}} \times \left( \frac{1}{1 - rr_i} \right)^4 \end{aligned}$$

and a minimum reading

$$P_{out\ min} = P \left( \frac{1 - 2rr_i}{1 - rr_i} \right)^2 10^{-\frac{d}{10}} \left( \frac{1 - 2rr_i}{1 - rr_i} \right)^2$$

$$= P \times 10^{-\frac{d}{10}} \times \left( \frac{1 - 2rr_i}{1 - rr_i} \right)^4$$

The measured insertion loss lies now between

$$d_{meas\ max} = \frac{P_{in\ max}}{P_{out\ min}} = d + 20 \lg \frac{1 - rr_i}{(1 - 2rr_i)^2}$$

$$d_{meas\ min} = \frac{P_{in\ min}}{P_{out\ max}} = d + 20 \lg [(1 - rr_i)(1 - 2rr_i)]$$

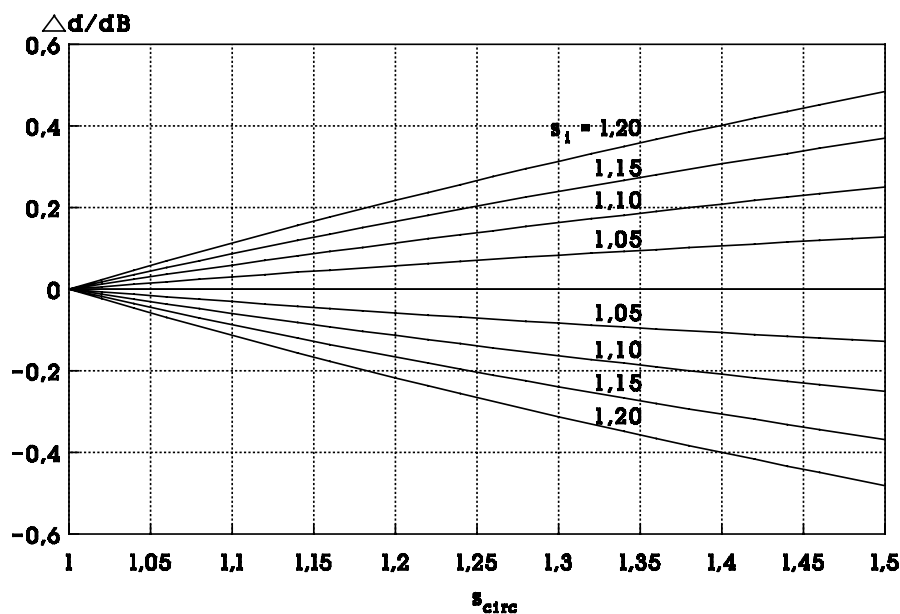


Fig.8: Max. diff. between the insertion loss of the circ. and the measured insertion loss as a function of the vswr of the circ.  $s_{circ}$  with the vswr  $s_i$  of the isolator of the measurement setup as a parameter

For small values of  $r$  and  $r_i$  we get the following deviation from the real value of the insertion loss

$$\Delta d_{meas} = 20 \lg (1 \pm 3 r r_i)$$

The exact values of the deviation are presented in figure 8. It shows, that the measured insertion loss of a circulator with a vswr of  $s=1,25$  measured between isolators with a vswr of  $s_i=1,10$  may deviate from the real value by  $\pm 0,14$  dB.

The same measurement setup can be used also at low power levels. Here we can use attenuators instead of isolators too.

But we can use also network analyzers. If we calibrate the network analyzer with the simple through calibration, then we get the same failures as discussed, taking  $s_i$  as the vswr of the ports. But using the 2-port-calibration the failure is reduced drastically by calculations.

There is also another method some times used, given in figure 9. It is very inaccurate and therefore not recommended. Here the measurement is done by connecting at first the signal source, which is decoupled by an isolator, directly to the detecting device, which is also decoupled by an isolator.

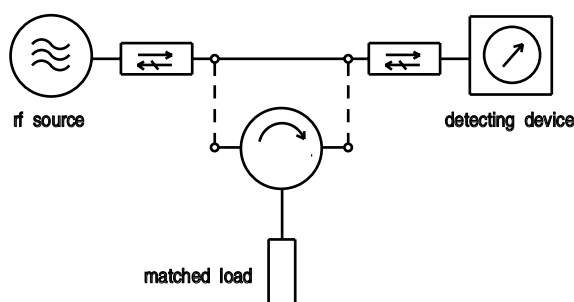


Fig.9: Another measurement setup for the insertion loss

For small signal measurements we can use attenuators instead of the isolators. Then the circulator to be measured is inserted. If the isolation of the isolators is higher than 20 dB or the attenuation of the attenuators is higher than 10 dB, the main sources of failure in the measurement of the insertion loss are the input and output reflections of the isolators or attenuators and the circulator being measured. During calibration the detected signal will lie between a maximum value  $A(1+r_i)$  and a minimum value  $A(1-r_i)$  caused by the vswr of the isolators or attenuators  $s_i$ , which multiply in the worst case.

$$r_i = \frac{s_i^2 - 1}{s_i^2 + 1}$$

If we now put the circulator with its vswr  $s$  in, then we get a maximum reading  $A_1(1+r)$  and a minimum reading  $A_1(1-r)$  with

$$r = 2 \frac{SS_i - 1}{SS_i + 1}$$

The measured insertion loss lies now between

$$d_{\text{meas max}} = 20 \lg \frac{A (1 + r_i)}{A_1 (1 - r)} = d + 20 \lg \frac{1 + r_i}{1 - r}$$

and

$$d_{\text{meas min}} = 20 \lg \frac{A (1 - r_i)}{A_i (1 + r)} = d + 20 \lg \frac{1 - r_i}{1 + r}$$

with  $d$  the real insertion loss of the circulator, or given as the deviation from the real value

$$\Delta d_{\text{max}} = 20 \lg \frac{1 + r_i}{1 - r}$$

$$\Delta d_{\text{min}} = 20 \lg \frac{1 - r_i}{1 + r}$$

and as an approximation for small values of  $r_i$  and  $r$

$$\Delta d_{\text{max, min}} = 20 \lg [1 \pm (r_i + r)]$$

When measuring in this setup the measured insertion loss of a circulator with a vswr of  $s=1,20$  measured between attenuators or isolators with a vswr of  $s_i=1,05$  may deviate from the real value by +2,7 dB and -2,2 dB.

Also the measurement of the insertion loss is influenced by harmonics and other spurious signals for the same reason as under 2.2, and we have to remove them by filters.

### 3. Some applications

#### 3.1 Reduction of the vswr or return loss of a load by using an isolator

Often the vswr of a load is high and fluctuating. For example the vswr of a gas filled chamber is very high, but after ignition this gas forms a plasma with high absorption. Or when curing rubber the impedance of the rubber changes with the progress of the process. Or the impedance of an antenna changes with obstacles in its neighbourhood.

To reduce this vswr we can use isolators.

The resulting input vswr of the cascade load and isolator depends on the load vswr, the isolation of the isolator, the vswr of the isolator, and the phase between load and isolator. For the calculation of the resulting input vswr we use the signal flow diagram of a circulator as given in figure 11.

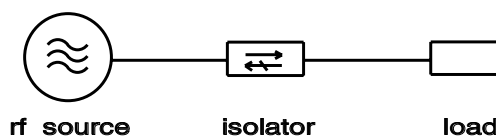


Fig.10: Reduction of the input vswr of a load by using an isolator

- port 1 the input port, connected to the generator
- port 2 the output port, connected to the fluctuating load with the reflection coefficient  $r_L$
- port 3 the internal port when using a circulator as an isolator, terminated with a matched load with the reflection coefficient  $r_H$
- $c_2$  the insertion loss of the circulator, given as a vector,  $|c_2| = 10^{-d/20}$  with  $d$  = insertion loss in dB
- $c_3$  the isolation of the circulator, given as a vector,  $|c_3| = 10^{-D/20}$  with  $D$  = isolation in dB

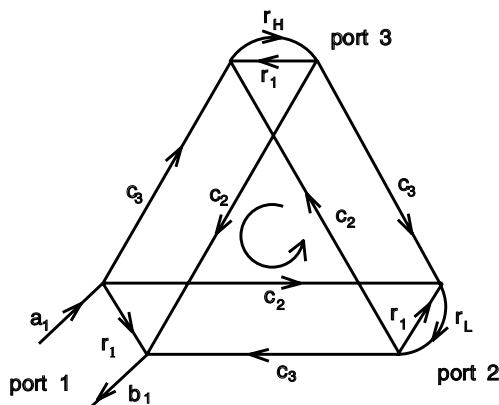


Fig.11: Signal flow diagram of a circulator

Using the rules of the signal flow diagram, we get the reflection coefficient  $r$  at the input of the circulator

$$r = \frac{b_1}{a_1} = \frac{r_1(1 - r_1 r_H - r_1 r_L - c_2 c_3 r_L r_H + r_1^2 r_H r_L) + c_2 c_3 r_L(1 - r_1 r_H) + c_2 c_3 r_H(1 - r_1 r_L) + c_2^3 r_H r_L + c_3^3 r_H r_L}{1 - r_1 r_H - r_1 r_L - c_2 c_3 r_H r_L + r_1^2 r_H r_L}$$

This expression looks very complicated, but it simplifies, if we take the following assumptions of practical nature:

1. The isolation of the circulator terminated with matched loads is equivalent to the return loss of the input:  $c_3=r_1$ .  
In practice these values differ only slightly.
2. The insertion loss of the isolator is very small, and we can neglect it:  $c_2=1$ .  
In practice the small attenuation will improve the maximum vswr calculated a bit.
3. The third port has a perfectly matched load:  $r_H=0$ . Normally the loads used for terminating the third port are much better than the input reflection of the circulator, therefore the failure made by this assumption is negligible.

With these assumptions we get for the reflection factor

$$r = \frac{r_1(1 - r_1 r_L + r_L)}{1 - r_1 r_L} = r_1 + \frac{r_L}{1 - r_1 r_L}$$

where  $r$ ,  $r_1$ ,  $r_L$  are complex. Depending of the phase of the load reflection we will get different values for the input reflection of the isolator. In figure 12 the input vswr is calculated for an isolator with a vswr of 1,25 terminated with a phase varying load with a vswr of 5. As we can see the input vswr can lie between 1,47 and 1,09.

We get the maximum reflection factor, which is very interesting for the design of systems, from the last equation when taking the magnitude of the complex numbers and maximizing the whole expression:

$$r_{\max} = r_1 + \frac{r_L}{1 - r_1 r_L}$$



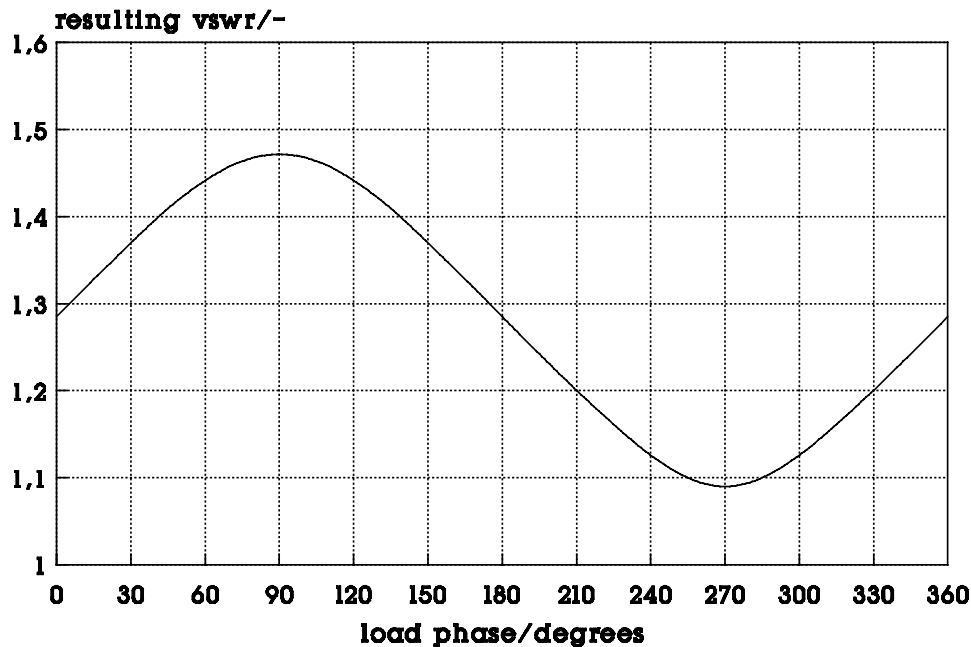


Fig.12: Resulting vswr at the input of an isolator with vswr of 1,25 terminated with a load of vswr=5 varying in phase

The maximum input vswr is then

$$S_{\max} = \frac{1 + r_{\max}}{1 - r_{\max}}$$

In figure 13 the maximum vswr of the input of an isolator is given as a function of the load vswr with the vswr of the isolator as a parameter. For high load vswr's it is easier to look not at the vswr but at the return loss

$$r_{\text{return loss}} = -20 \lg(r)$$

Therefore in figure 14 the minimum input return loss of an isolator is given as a function of the return loss of the terminating load with the return loss of the isolator as a parameter. Here we can see, that the return loss of a load of 0 dB (vswr=∞, total reflection) is increased by an isolator with a return loss of 20 dB to a minimum return loss of 13,5 dB.

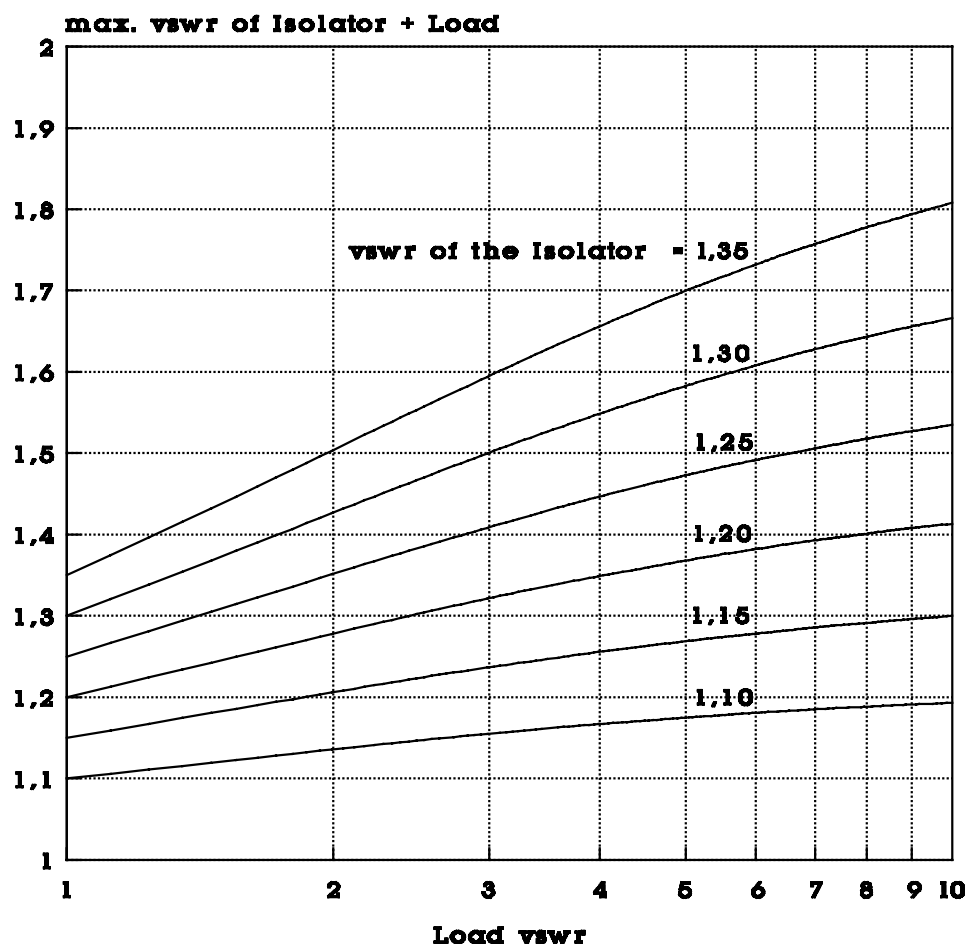


Fig.13: Reduction of the load vswr by an isolator. The maximum vswr of the cascade load plus isolator is given as a function of the load vswr with the vswr of the isolator

### 3.2 Behaviour of the input vswr or return loss of a circulator terminated with a filter

In applications with one transmitter and one receiver on one aerial or two or more transmitters or receivers on one aerial the circulator used is terminated with filters on two ports (see figure 15).

We assume that the transmitter and the receiver are reasonably matched at their ports. When looking into the filters from the circulator,

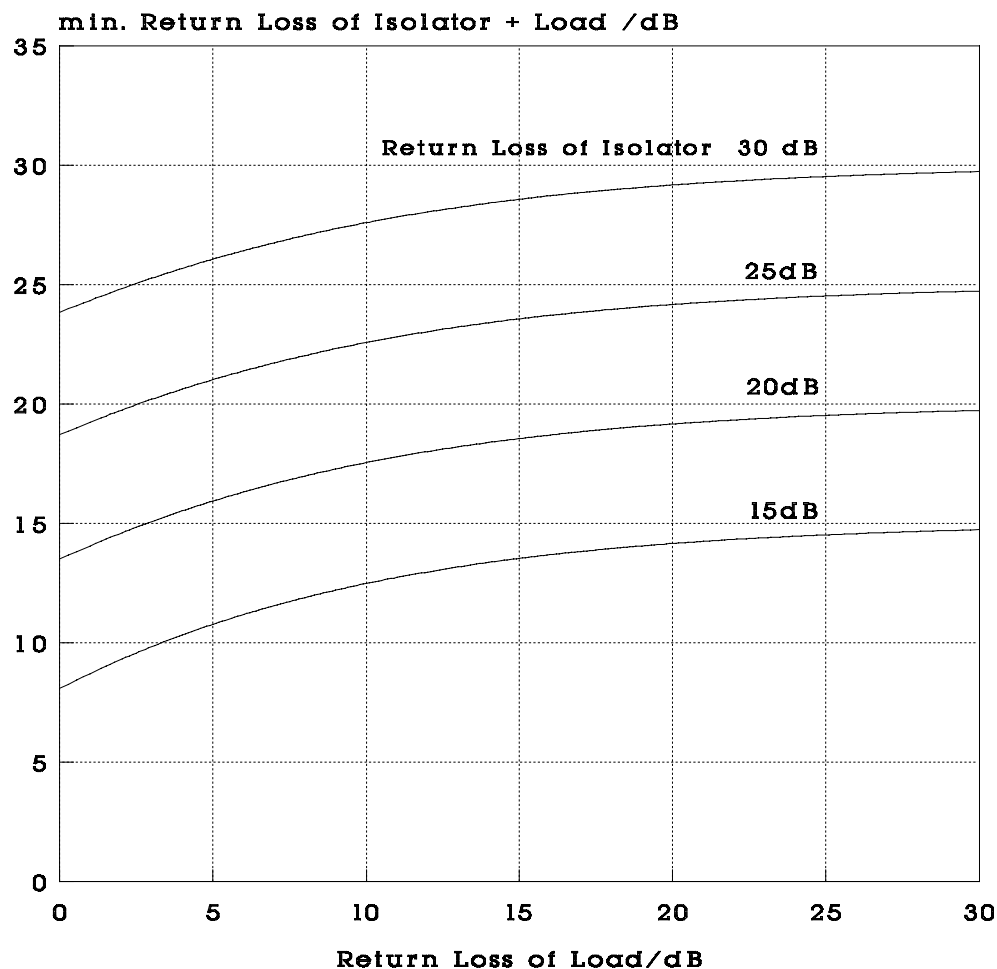


Fig.14: Increasing the load return loss by an isolator. The minimum return loss of the cascade load plus isolator is given as a function of the load return loss with the return loss of the isolator as a parameter

we see a reasonable match in the pass-band, but about total reflection in the stop-bands. These reflections influence the  $v_{swr} s_a$  of the circulator at the antenna port.

We can calculate  $s_a$  by using the signal flow diagram of figure 11. As in the previous paragraph we can assume that

1. the isolation of the circulator terminated with matched loads is equivalent to the return loss of the input:  $c_3=r_1$ ,
2. the insertion loss of the isolator is very small and can be neglected:  $c_2=1$ .

For the frequency bands of interest, receiving band and transmitting band, we have total reflection on one port ( $r_H=1$ ) and a vswr  $s_L$  on the other port.

With these assumptions and the calculation of  $r_L$  out of  $s_L$

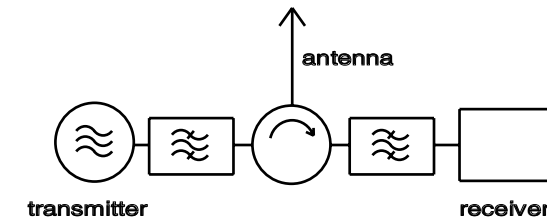


Fig.15: Transmitter and receiver on one antenna

$$r_L = \frac{s_L - 1}{s_L + 1}$$

we can simplify the complicated expression of page 15 to

$$r_a = \frac{r_1(2 - r_1 - 4r_1r_L + 2r_1^2r_L + r_L) + r_L}{1 - r_1 - 2r_1r_L + r_1^2r_L}$$

This approximation is valid for circulators with a vswr up to 1,30 and load vswr's up to 2. For higher values we have to take into account the insertion loss and the possible phases of  $r_1$  and  $c_3$ . The maximum value of the reflection coefficient is

$$r_{a \max} = \frac{r_1(2 - r_1 - 4r_1r_L + 2r_1^2r_L + r_L) + r_L}{1 - r_1 - 2r_1r_L + r_1^2r_L}$$

or as a standing wave ratio

$$s_{a \max} = \frac{1 + r_{a \max}}{1 - r_{a \max}}$$

This is the worst vswr of the circulator at the antenna port when all the reflections add (see figure 16). But with variations in the line length between the filters and the circulator it can be improved drastically.

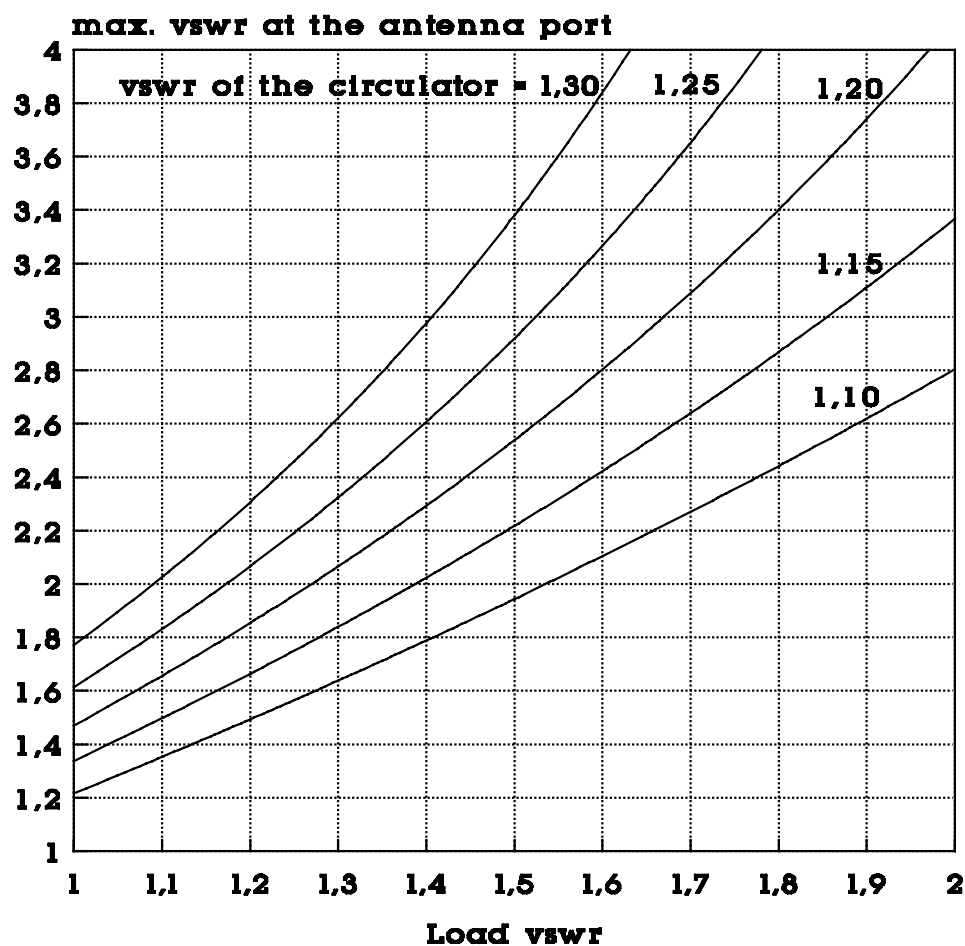


Fig.16: Worst vswr at the antenna port of a circulator terminated with a filter and a reflecting load

#### Literature:

1. Butterweck, H.J.: Der Y-Zirkulator, AEÜ 17(1963) S.163ff
2. Fiebig, A.: Lineare Signalfußdiagramme, AEÜ(1961), S.285ff

1992-08

# Philips Semiconductors – a worldwide company

**Argentina:** see South America

**Australia:** 34 Waterloo Road, NORTH RYDE, NSW 2113,  
Tel. +61 2 9805 4455, Fax. +61 2 9805 4466

**Austria:** Computerstr. 6, A-1101 WIEN, P.O. Box 213, Tel. +43 160 1010,  
Fax. +43 160 101 1210

**Belarus:** Hotel Minsk Business Center, Bld. 3, r. 1211, Volodarski Str. 6,  
220050 MINSK, Tel. +375 172 200 733, Fax. +375 172 200 773

**Belgium:** see The Netherlands

**Brazil:** see South America

**Bulgaria:** Philips Bulgaria Ltd., Energoprojekt, 15th floor,  
51 James Bourchier Blvd., 1407 SOFIA,  
Tel. +359 2 689 211, Fax. +359 2 689 102

**Canada:** PHILIPS SEMICONDUCTORS/COMPONENTS,  
Tel. +1 800 234 7381

**China/Hong Kong:** 501 Hong Kong Industrial Technology Centre,  
72 Tat Chee Avenue, Kowloon Tong, HONG KONG,  
Tel. +852 2319 7888, Fax. +852 2319 7700

**Colombia:** see South America

**Czech Republic:** see Austria

**Denmark:** Prags Boulevard 80, PB 1919, DK-2300 COPENHAGEN S,  
Tel. +45 32 88 2636, Fax. +45 31 57 0044

**Finland:** Sinikalliontie 3, FIN-02630 ESPOO,  
Tel. +358 9 615800, Fax. +358 9 61580920

**France:** 51 Rue Carnot, BP317, 92156 SURESNES Cedex,  
Tel. +33 1 40 99 6161, Fax. +33 1 40 99 6427

**Germany:** Hammerbrookstraße 69, D-20097 HAMBURG,  
Tel. +49 40 23 53 60, Fax. +49 40 23 536 300

**Greece:** No. 15, 25th March Street, GR 17778 TAVROS/ATHENS,  
Tel. +30 1 4894 339/239, Fax. +30 1 4814 240

**Hungary:** see Austria

**India:** Philips INDIA Ltd, Band Box Building, 2nd floor,  
254-D, Dr. Annie Besant Road, Worli, MUMBAI 400 025,  
Tel. +91 22 493 8541, Fax. +91 22 493 0966

**Indonesia:** see Singapore

**Ireland:** Newstead, Clonskeagh, DUBLIN 14,  
Tel. +353 1 7640 000, Fax. +353 1 7640 200

**Israel:** RAPAC Electronics, 7 Kehilat Saloniki St, PO Box 18053,  
TEL AVIV 61180, Tel. +972 3 645 0444, Fax. +972 3 649 1007

**Italy:** PHILIPS SEMICONDUCTORS, Piazza IV Novembre 3,  
20124 MILANO, Tel. +39 2 6752 2531, Fax. +39 2 6752 2557

**Japan:** Philips Bldg 13-37, Kohnan 2-chome, Minato-ku, TOKYO 108,  
Tel. +81 3 3740 5130, Fax. +81 3 3740 5077

**Korea:** Philips House, 260-199 Itaewon-dong, Yongsan-ku, SEOUL,  
Tel. +82 2 709 1412, Fax. +82 2 709 1415

**Malaysia:** No. 76 Jalan Universiti, 46200 PETALING JAYA, SELANGOR,  
Tel. +60 3 750 5214, Fax. +60 3 757 4880

**Mexico:** 5900 Gateway East, Suite 200, EL PASO, TEXAS 79905,  
Tel. +9-5 800 234 7381

**Middle East:** see Italy

**Netherlands:** Postbus 90050, 5600 PB EINDHOVEN, Bldg. VB,  
Tel. +31 40 27 82785, Fax. +31 40 27 88399

**New Zealand:** 2 Wagener Place, C.P.O. Box 1041, AUCKLAND,  
Tel. +64 9 849 4160, Fax. +64 9 849 7811

**Norway:** Box 1, Manglerud 0612, OSLO,  
Tel. +47 22 74 8000, Fax. +47 22 74 8341

**Philippines:** Philips Semiconductors Philippines Inc.,  
106 Valero St. Salcedo Village, P.O. Box 2108 MCC, MAKATI,  
Metro MANILA, Tel. +63 2 816 6380, Fax. +63 2 817 3474

**Poland:** Ul. Lukiska 10, PL 04-123 WARSZAWA,  
Tel. +48 22 612 2831, Fax. +48 22 612 2327

**Portugal:** see Spain

**Romania:** see Italy

**Russia:** Philips Russia, Ul. Usatcheva 35A, 119048 MOSCOW,  
Tel. +7 095 755 6918, Fax. +7 095 755 6919

**Singapore:** Lorong 1, Toa Payoh, SINGAPORE 1231,  
Tel. +65 350 2538, Fax. +65 251 6500

**Slovakia:** see Austria

**Slovenia:** see Italy

**South Africa:** S.A. PHILIPS Pty Ltd., 195-215 Main Road Martindale,  
2092 JOHANNESBURG, P.O. Box 7430 Johannesburg 2000,  
Tel. +27 11 470 5911, Fax. +27 11 470 5494

**South America:** Al. Vicente Pinzon, 173, 6th floor,  
04547-130 SÃO PAULO, SP, Brazil,  
Tel. +55 11 821 2333, Fax. +55 11 821 2382

**Spain:** Balmes 22, 08007 BARCELONA,  
Tel. +34 3 301 6312, Fax. +34 3 301 4107

**Sweden:** Kottbygatan 7, Akalla, S-16485 STOCKHOLM,  
Tel. +46 8 632 2000, Fax. +46 8 632 2745

**Switzerland:** Allmendstrasse 140, CH-8027 ZÜRICH,  
Tel. +41 1 488 2686, Fax. +41 1 488 3263

**Taiwan:** Philips Semiconductors, 6F, No. 96, Chien Kuo N. Rd., Sec. 1,  
TAIPEI, Taiwan Tel. +886 2 2134 2865, Fax. +886 2 2134 2874

**Thailand:** PHILIPS ELECTRONICS (THAILAND) Ltd.,  
209/2 Sanpavuth-Bangna Road Prakanong, BANGKOK 10260,  
Tel. +66 2 745 4090, Fax. +66 2 398 0793

**Turkey:** Talatpasa Cad. No. 5, 80640 GÜLTEPE/ISTANBUL,  
Tel. +90 212 279 2770, Fax. +90 212 282 6707

**Ukraine:** PHILIPS UKRAINE, 4 Patrice Lumumba str., Building B, Floor 7,  
252042 KIEV, Tel. +380 44 264 2776, Fax. +380 44 268 0461

**United Kingdom:** Philips Semiconductors Ltd., 276 Bath Road, Hayes,  
MIDDLESEX UB3 5BX, Tel. +44 181 730 5000, Fax. +44 181 754 8421

**United States:** 811 East Arques Avenue, SUNNYVALE, CA 94088-3409,  
Tel. +1 800 234 7381

**Uruguay:** see South America

**Vietnam:** see Singapore

**Yugoslavia:** PHILIPS, Trg N. Pasica 5/v, 11000 BEOGRAD,  
Tel. +381 11 625 344, Fax. +381 11 635 777

**For all other countries apply to:** Philips Semiconductors,  
International Marketing & Sales Communications, Building BE-p, P.O. Box 218,  
5600 MD EINDHOVEN, The Netherlands, Fax. +31 40 27 24825

**Internet:** <http://www.semiconductors.philips.com>

© Philips Electronics N.V. 1998

SCA57

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

Printed in The Netherlands

Date of release: 1998 Mar 23

*Let's make things better.*

**Philips**  
**Semiconductors**



**PHILIPS**