

TECHNICAL PUBLICATION

**Power transformers for the
frequency range of 30 – 80 MHz**

ECO7703

**Power transformers for the frequency
range of 30 – 80 MHz**

**Technical Publication
ECO7703**

CONTENTS

1	ABSTRACT
2	SUMMARY
3	INTRODUCTION
4	CHOICE OF CORE MATERIAL
5	POWER HANDLING CAPABILITY
6	DETERMINATION OF THE NUMBER OF TURNS
7	WINDING LOSSES
8	PRACTICAL EXAMPLE
8.1	Reference:
9	APPENDIX

Power transformers for the frequency range of 30 – 80 MHz

Technical Publication
ECO7703

1 ABSTRACT

In this report design information is given for transformers with a power handling capability up to 300 W in the frequency range of 30 – 80 MHz.

The most suitable core material is ferrite type 4C6. The efficiency of these transformers is typically 98%.

2 SUMMARY

In this frequency range only transmission line transformers can be used. For the windings coaxial cables with P.T.F.E. isolation are recommended.

The size of the core is based on a 1% power loss and a dissipation of 350 mW/cm³ corresponding with a flux density of 6 Gauss at 80 MHz.

The required number of turns is determined by the ratio $R_P/L = 860 \Omega/\mu H$ in which R_P is the loss resistance and L the inductance in parallel with the input or output terminals.

In the appendix the relation between the above mentioned quantities is derived.

In the report a practical example is given of a symmetrical 1 : 4 impedance transformer with a power handling capability of 120 W.

3 INTRODUCTION

In Ref.1 information was given on the design of power transformers mainly intended for the frequency range of 1.6 to 28 MHz. In this report some additional information will be presented for the frequency range of 30 to 80 MHz.

4 CHOICE OF CORE MATERIAL

The best available ferrite for this frequency range is 4C6. In this material a series of toroids can be obtained in different sizes according to Table 1.

Table 1

D ⁽¹⁾ (mm)	d ⁽²⁾ (mm)	h ⁽³⁾ (mm)	A ⁽⁴⁾ (mm ²)	A/l ⁽⁵⁾ (mm)	V ⁽⁶⁾ (mm ³)
36	23	15	97.7	1.06	8 500
23	14	7	31.5	0.552	1 790
14	9	5	12.5	0.351	445
9	6	3	4.51	0.193	105

Notes

1. Outside diameter.
2. Inside diameter.
3. Height.
4. Cross-section.
5. Average length of the lines of force.
6. Volume.

Power transformers for the frequency range of 30 – 80 MHz

Technical Publication
ECO7703

5 POWER HANDLING CAPABILITY

An important question in the design of a power transformer is how much R.F. power can be handled by a given toroid. Restricting ourselves to the core losses at this moment it can be said that these losses are highest at the maximum frequency of operation i.e. 80 MHz.

From practical experience we have found that a core dissipation of 350 mW/cm³ can be allowed without excessive rise of the core temperature. As it is a realistic target to keep the core losses below 1% of the power handled by the transformer we come to the following recommendations for the power handling of the different toroids (see Table 2).

Table 2

$D \times d \times h$ (mm ³)	P_{RF} (W)
$36 \times 23 \times 15$	300
$23 \times 14 \times 7$	60
$14 \times 9 \times 5$	15
$9 \times 6 \times 3$	3

The core dissipation of 350 mW/cm³ mentioned above corresponds with a flux density of 6 Gauss at 80 MHz as can be found in earlier versions of Data Handbook MA01 of Philips series on Magnetic Products: Soft ferrites.

6 DETERMINATION OF THE NUMBER OF TURNS

In the frequency range of 30-80 MHz the number of turns is entirely determined by the loss resistance in parallel with the input or output terminals of the transformer being caused by the core losses. According to the Appendix the core loss figures given Chapter 5 can be expressed in another way, viz:

$$\frac{R_p}{L} = \frac{\omega^2 B_{max}^2}{2\mu_o\mu_r} \times \frac{V}{P_L}$$

in which:

R_p = loss resistance in parallel with input or output terminals

L = inductance in parallel with input or output terminals

B_{max} = maximum flux density

μ_r = relative permeability being typ. 120 for 4C6 material

V = volume of transformer core

P_L = power loss in core.

Using the figures given in Chapter 5 we get:

$$\frac{R_p}{L} = 860 \Omega / \mu H \text{ at } f = 80 \text{ MHz.}$$

This ratio is hardly dependent on the flux density and therefore it is very useful for defining the number of turns as will be shown by a practical example in Chapter 8.

Applying the above mentioned criterion ensures a sufficiently high reactance in parallel with the input or output terminals at the lowest frequency of operation. So this reactance caused by the inductance of the winding needs no compensation.

Power transformers for the frequency range of 30 – 80 MHz

Technical Publication
ECO7703

7 WINDING LOSSES

In this frequency range conventional transformers can not be used because of their stray-inductance. The only suitable type is the transmission line transformer. For the windings we can choose a.o:

- Twisted enamelled copper wire
- Miniature twin lead
- Coaxial cable with P.T.F.E. isolation, available in several diameters and characteristic resistances.

The first and second are not recommended for high power operation. The third type is e.g. available in 50 Ohms version with diameters of 1.7 and 2.8 mm. Some important properties of these cables at 80 MHz are given in Table 3.


Table 3

Outside diameter	1.7	2.8	mm
Power loss	0.40	0.24	dB/m
Power handling capability	100	200	W

At lower frequencies the power loss is less and the power handling capability higher.

8 PRACTICAL EXAMPLE

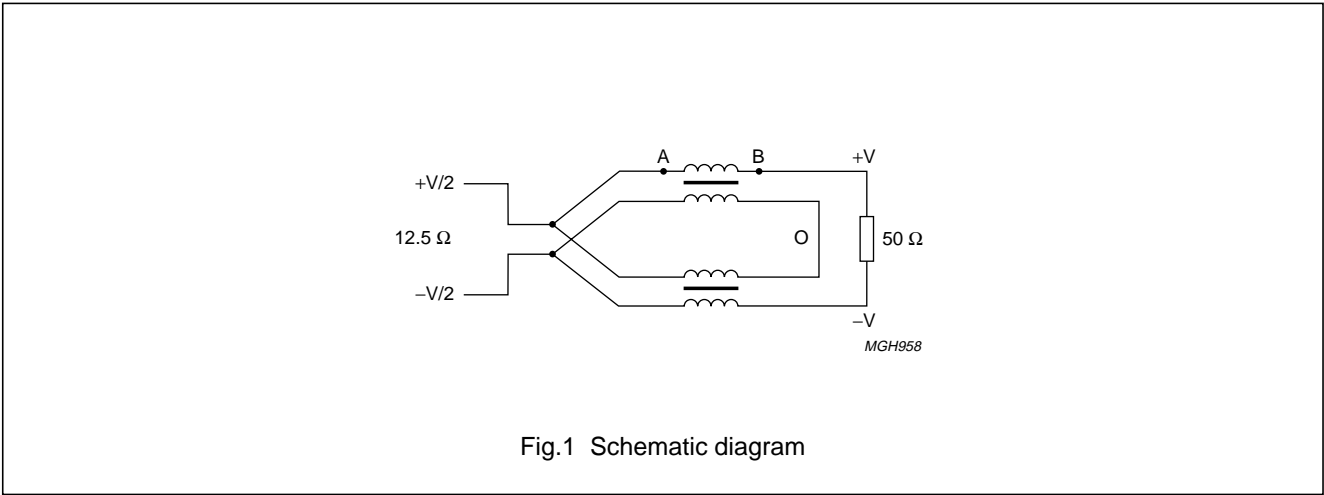Suppose that in a 100 W transmitter the output transistors are connected in push-pull. The optimum load impedance between the collectors is 12.5 Ω and this must be transformed to 50 Ω. Then we need a symmetrical 1 : 4 impedance transformer plus a balun. The first one will be worked out in detail. A schematic diagram is given in Fig.1.



From Table 2 we see that this transformer can be made with one 36 mm toroid but also with two 23 mm toroids, in which case the power handling capability is still 120 W. The latter solution is more attractive because it is smaller.

The optimum characteristic impedance for each winding is 25 Ω which can realized by the parallel connection of two 50 Ω cables of 1.7 mm diameter. As the power is transported through 4 cables, each cable is loaded with 25 W being a quarter of the allowable maximum.

Power transformers for the frequency range of 30 – 80 MHz

Technical Publication
ECO7703

The number of turns will be calculated with the 50 Ω output terminals as a reference point. To keep the core losses below 1% we must keep the parallel loss resistance above 5000 Ω . This means an inductance of: $L = \frac{R_P}{860} = \frac{5000}{860} = 5.81 \mu\text{H}$ (see Chapter 6).

Between the points A and B in Fig.1 the voltage is one quarter of the output voltage. This means that the inductance between these points must be one sixteenth of that across the output terminals, so: $L_{AB} = \frac{L}{16} = \frac{5.81}{16} = 0.363 \mu\text{H}$

Now the number of turns can be calculated with: $n = \sqrt{\frac{L1}{\mu_o \mu_r A}} = 1.48$

In practice we will choose of course 2 turns by which the core losses reduce to: $\left(\frac{1.48}{2}\right)^2 \times 1\% = 0.55\%$

The inductance in parallel with the output terminals rises to: $\left(\frac{2}{1.48}\right)^2 \times 5.81 = 10.6 \mu\text{H}$

This corresponds to a reactance of 2000 Ω at 30 MHz which is high enough to be neglected.

To realize the windings cables are required with a length of appr. 98 mm giving a cable loss of 0.039 dB or 0.91%.

So the total calculated loss of this transformer is:

$$0.55 + 0.91 = 1.46\% \text{ at } f = 80 \text{ MHz.}$$

8.1 Reference:

Application report no. ECO6907 'Design of H.F. Wideband Power Transformers' by A.H. Hilbers, June 17th, 1970.

Power transformers for the frequency range of 30 – 80 MHz

Technical Publication
ECO7703

9 APPENDIX

In the Data Handbook, as given in Chapter 5, curves are given showing the core losses expressed in kW/m³ or mW/cm³ versus the flux density B with the frequency as a parameter. It is often useful to know what this means in terms of an equivalent loss resistance in parallel with the inductance. The power dissipated in this resistance is equal to:

$$P_L = \frac{E_{\max}^2}{2R_p} \quad (1)$$

On the other hand:

$$B_{\max} = \frac{E_{\max}}{\omega A n} \quad (2)$$

Eliminating E_{\max} in (1) and (2) gives:

$$P_L = \frac{\omega^2 B_{\max}^2 A^2 n^2}{2R_p} \quad (3)$$

Further we know that:

$$L = \frac{\mu_o \mu_r n^2 A}{l} \quad (4)$$

So that:

$$n^2 A = \frac{L l}{\mu_o \mu_r} \quad (5)$$

Substituting (5) in (3) we get:

$$P_L = \frac{\omega^2 B_{\max}^2 A l}{2\mu_o \mu_r R_p} \quad (6)$$

The product Al is equal to the volume of the core V , so that:

$$\frac{P_L}{V} = \frac{\omega^2 B_{\max}^2}{2\mu_o \mu_r} \times \frac{L}{R_p} \quad (7)$$

or:

$$\frac{R_p}{L} = \frac{\omega^2 B_{\max}^2}{2\mu_o \mu_r} \times \frac{V}{P_L}$$

Philips Semiconductors – a worldwide company

Argentina: see South America

Australia: 34 Waterloo Road, NORTH RYDE, NSW 2113,
Tel. +61 2 9805 4455, Fax. +61 2 9805 4466

Austria: Computerstr. 6, A-1101 WIEN, P.O. Box 213, Tel. +43 160 1010,
Fax. +43 160 101 1210

Belarus: Hotel Minsk Business Center, Bld. 3, r. 1211, Volodarski Str. 6,
220050 MINSK, Tel. +375 172 200 733, Fax. +375 172 200 773

Belgium: see The Netherlands

Brazil: see South America

Bulgaria: Philips Bulgaria Ltd., Energoprojekt, 15th floor,
51 James Bourchier Blvd., 1407 SOFIA,
Tel. +359 2 689 211, Fax. +359 2 689 102

Canada: PHILIPS SEMICONDUCTORS/COMPONENTS,
Tel. +1 800 234 7381

China/Hong Kong: 501 Hong Kong Industrial Technology Centre,
72 Tat Chee Avenue, Kowloon Tong, HONG KONG,
Tel. +852 2319 7888, Fax. +852 2319 7700

Colombia: see South America

Czech Republic: see Austria

Denmark: Prags Boulevard 80, PB 1919, DK-2300 COPENHAGEN S,
Tel. +45 32 88 2636, Fax. +45 31 57 0044

Finland: Sinikalliontie 3, FIN-02630 ESPOO,
Tel. +358 9 615800, Fax. +358 9 61580920

France: 51 Rue Carnot, BP317, 92156 SURESNES Cedex,
Tel. +33 1 40 99 6161, Fax. +33 1 40 99 6427

Germany: Hammerbrookstraße 69, D-20097 HAMBURG,
Tel. +49 40 23 53 60, Fax. +49 40 23 536 300

Greece: No. 15, 25th March Street, GR 17778 TAVROS/ATHENS,
Tel. +30 1 4894 339/239, Fax. +30 1 4814 240

Hungary: see Austria

India: Philips INDIA Ltd, Band Box Building, 2nd floor,
254-D, Dr. Annie Besant Road, Worli, MUMBAI 400 025,
Tel. +91 22 493 8541, Fax. +91 22 493 0966

Indonesia: see Singapore

Ireland: Newstead, Clonskeagh, DUBLIN 14,
Tel. +353 1 7640 000, Fax. +353 1 7640 200

Israel: RAPAC Electronics, 7 Kehilat Saloniki St, PO Box 18053,
TEL AVIV 61180, Tel. +972 3 645 0444, Fax. +972 3 649 1007

Italy: PHILIPS SEMICONDUCTORS, Piazza IV Novembre 3,
20124 MILANO, Tel. +39 2 6752 2531, Fax. +39 2 6752 2557

Japan: Philips Bldg 13-37, Kohnan 2-chome, Minato-ku, TOKYO 108,
Tel. +81 3 3740 5130, Fax. +81 3 3740 5077

Korea: Philips House, 260-199 Itaewon-dong, Yongsan-ku, SEOUL,
Tel. +82 2 709 1412, Fax. +82 2 709 1415

Malaysia: No. 76 Jalan Universiti, 46200 PETALING JAYA, SELANGOR,
Tel. +60 3 750 5214, Fax. +60 3 757 4880

Mexico: 5900 Gateway East, Suite 200, EL PASO, TEXAS 79905,
Tel. +9-5 800 234 7381

Middle East: see Italy

Netherlands: Postbus 90050, 5600 PB EINDHOVEN, Bldg. VB,
Tel. +31 40 27 82785, Fax. +31 40 27 88399

New Zealand: 2 Wagener Place, C.P.O. Box 1041, AUCKLAND,
Tel. +64 9 849 4160, Fax. +64 9 849 7811

Norway: Box 1, Manglerud 0612, OSLO,
Tel. +47 22 74 8000, Fax. +47 22 74 8341

Philippines: Philips Semiconductors Philippines Inc.,
106 Valero St. Salcedo Village, P.O. Box 2108 MCC, MAKATI,
Metro MANILA, Tel. +63 2 816 6380, Fax. +63 2 817 3474

Poland: Ul. Lukiska 10, PL 04-123 WARSZAWA,
Tel. +48 22 612 2831, Fax. +48 22 612 2327

Portugal: see Spain

Romania: see Italy

Russia: Philips Russia, Ul. Usatcheva 35A, 119048 MOSCOW,
Tel. +7 095 755 6918, Fax. +7 095 755 6919

Singapore: Lorong 1, Toa Payoh, SINGAPORE 1231,
Tel. +65 350 2538, Fax. +65 251 6500

Slovakia: see Austria

Slovenia: see Italy

South Africa: S.A. PHILIPS Pty Ltd., 195-215 Main Road Martindale,
2092 JOHANNESBURG, P.O. Box 7430 Johannesburg 2000,
Tel. +27 11 470 5911, Fax. +27 11 470 5494

South America: Al. Vicente Pinzon, 173, 6th floor,
04547-130 SÃO PAULO, SP, Brazil,
Tel. +55 11 821 2333, Fax. +55 11 821 2382

Spain: Balmes 22, 08007 BARCELONA,
Tel. +34 3 301 6312, Fax. +34 3 301 4107

Sweden: Kottbygatan 7, Akalla, S-16485 STOCKHOLM,
Tel. +46 8 632 2000, Fax. +46 8 632 2745

Switzerland: Allmendstrasse 140, CH-8027 ZÜRICH,
Tel. +41 1 488 2686, Fax. +41 1 488 3263

Taiwan: Philips Semiconductors, 6F, No. 96, Chien Kuo N. Rd., Sec. 1,
TAIPEI, Taiwan Tel. +886 2 2134 2865, Fax. +886 2 2134 2874

Thailand: PHILIPS ELECTRONICS (THAILAND) Ltd.,
209/2 Sanpavuth-Bangna Road Prakanong, BANGKOK 10260,
Tel. +66 2 745 4090, Fax. +66 2 398 0793

Turkey: Talatpasa Cad. No. 5, 80640 GÜLTEPE/ISTANBUL,
Tel. +90 212 279 2770, Fax. +90 212 282 6707

Ukraine: PHILIPS UKRAINE, 4 Patrice Lumumba str., Building B, Floor 7,
252042 KIEV, Tel. +380 44 264 2776, Fax. +380 44 268 0461

United Kingdom: Philips Semiconductors Ltd., 276 Bath Road, Hayes,
MIDDLESEX UB3 5BX, Tel. +44 181 730 5000, Fax. +44 181 754 8421

United States: 811 East Arques Avenue, SUNNYVALE, CA 94088-3409,
Tel. +1 800 234 7381

Uruguay: see South America

Vietnam: see Singapore

Yugoslavia: PHILIPS, Trg N. Pasica 5/v, 11000 BEOGRAD,
Tel. +381 11 625 344, Fax. +381 11 635 777

For all other countries apply to: Philips Semiconductors,
International Marketing & Sales Communications, Building BE-p, P.O. Box 218,
5600 MD EINDHOVEN, The Netherlands, Fax. +31 40 27 24825

Internet: <http://www.semiconductors.philips.com>

© Philips Electronics N.V. 1998

SCA57

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

The information presented in this document does not form part of any quotation or contract, is believed to be accurate and reliable and may be changed without notice. No liability will be accepted by the publisher for any consequence of its use. Publication thereof does not convey nor imply any license under patent- or other industrial or intellectual property rights.

Printed in The Netherlands

Date of release: 1998 Mar 23

Let's make things better.

**Philips
Semiconductors**



PHILIPS