

New Components Simplify Brush DC Motor Drives

By Warren Schultz
 Motorola Discrete Applications

A variety of new components are making brush motor drive design easier. One of these components is a brushless motor control IC that is easily set up to drive brush motors. In addition, multiple power MOSFETs, a new MOS turn-off device and gain stable opto level shifters further simplify high performance DC motor drives. The circuits described here illustrate how these components can be combined to make practical drive circuits. Specifically, topologies which will control speed in both directions and operate from a single power supply are considered.

CONTROL IC

In a brush motor drive, the control ICs primary function is to translate speed and direction inputs into appropriate drive for the power transistors. A very good way to do this is to use the MC33033 Brushless DC controller that is shown in Figure 1.

In a brushless application, two of six output transistors are switched-on in response to Hall sensor inputs H_A , H_B , and H_C . In order to drive a brush motor, all that is required is to select a single Hall code that will drive a

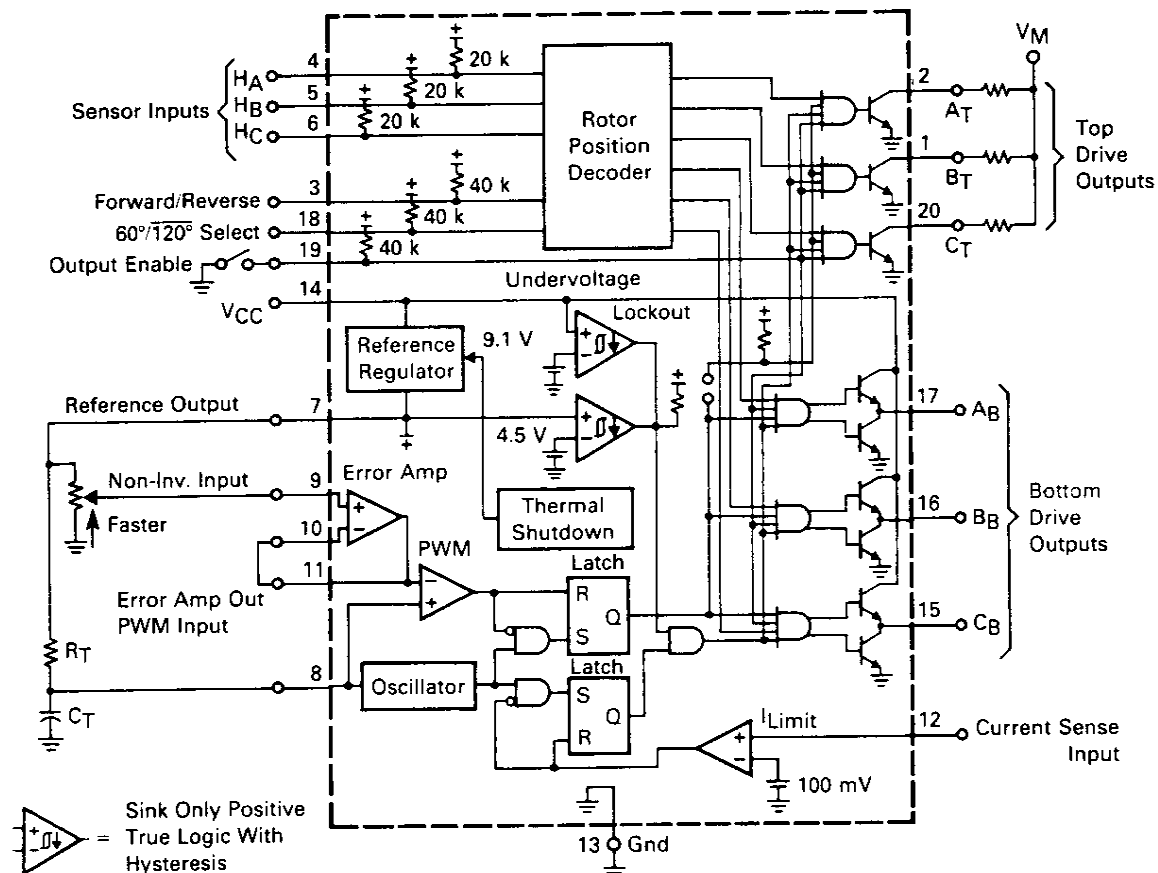


Figure 1. Representative Block Diagram of MC33033 Brushless DC Controller



four transistor H-bridge in a way that is suitable for brush motors. The truth table in Figure 2 provides the coding information that is needed to make this selection. The first line shows that a 100 Hall code turns-on A_{TOP} and C_{BOTTOM} with Forward/Reverse (Pin 3) at logic 1. Going down to line 7, 100 turns-on A_{BOTTOM} and C_{TOP} with Forward/Reverse at logic 0. Therefore, by using phase A and phase C outputs, a 100 Hall code produces the correct drive for brush motors. Note that the top outputs are open collectors, therefore, a logic 0 represents the on state. Conversely, the bottom outputs are totem pole drivers, and a logic 1 turns-on the corresponding output transistor.

Generating the Hall code is easy. Since it is fixed at 100, tying the Hall inputs to DC levels will do the job. Logic 1 is obtained from V_{REF} and logic 0 from ground. The result is the connections for pins 4, 5 and 6 that are shown in Figure 3.

In addition to providing drive to the output transistors, the MC33033 has a current limit function and controls speed by pulse width modulating the lower output transistors. The current limit operates on a 100 mV threshold. Once tripped, it latches the lower transistor drive off until the next clock cycle begins. The latching feature prevents high frequency oscillations which would otherwise overheat the power transistors. Compatibility with SENSEFETs is provided by the 100 mV threshold, and allows the lossless current sensing configuration that is also shown in Figure 3.

LEVEL SHIFTING

For low power, low voltage, motors level shifting is not a problem. Open collector top side outputs in the MC33033 interface directly to P-Channel MOSFETs. All that is required in the way of top side drive circuitry is gate-to-source resistors on the P-Channel transistors, such as R2 and R3 in Figure 3. However, motors that draw more than 5.0 amps are usually driven with all N-Channel bridges. In these applications, level shift and drive for the high side N-Channels can be considerably simplified with two new components, an MOC8102 optoisolator and MDC1000 MOS turn-off device.

In order to illustrate, consider the circuit in Figure 4. This is an extension of the circuit in Figure 3 to an all N-Channel configuration. A charge pump is added to provide above the rail bias for N-Channel gate drive. Level shift and drive for the top transistors is relatively straightforward, but takes four transistors, three resistors and a zener for each one.

In contrast, Figure 5 shows the same motor drive using the new optocoupler and MOS turn-off devices. The reduction in complexity is obvious. Part count is reduced from eight to three. What makes it work may require some explanation.

Historically optoisolators have not been widely used in this type of application because of large variations in current transfer ratio (gain). Common device types such as the 4N26 have large initial tolerances that can be as

Figure 2. Commutation Truth Table

| Inputs (Note 1) | | | | | | | Outputs (Note 2) | | | | | | |
|---------------------------|----------------|----------------|-----|--------|-------|---------------|------------------|----------------|----------------|----------------|----------------|----------------|-------|
| Sensor Electrical Phasing | | | | | | | Top Drives | | | Bottom Drives | | | Fault |
| | | | | | | | | | | | | | |
| S _A | S _B | S _C | F/R | Enable | Brake | Current Sense | A _T | B _T | C _T | A _B | B _B | C _B | |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | X | X | 0 | X | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | X | X | 0 | X | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| X | X | X | X | 0 | 0 | X | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| V | V | V | X | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| X | X | X | X | X | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| X | X | X | X | X | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

NOTES:

1. The digital inputs (Pins 3, 4, 5, 6, 7, 23) are all TTL compatible. The current sense input (Pin 9) has a 100 mV threshold. A logic 0 for this input is defined as < 80 mV, and a logic 1 is < 120 mV.
2. The Fault and top drive outputs are open collectors and are active in the low (0) state.
3. V = any one of the six valid sensor combinations.
X = Don't care.



ClibPDF - www.fastio.com

resistors, and the P-Channels are connected directly to A_T and C_T and tied to the rail through pull up resistors. At higher values of rail voltage, a divider can be used to keep gate voltage on the P-Channels within reasonable limits.

In Figure 3, the mirror outputs of both SENSEFETs are tied together. They are then fed into the MC33033's current limit input through a noise suppression filter consisting of R7 and C3. Since only one SENSEFET is on at any given time, this connection is a logic wired-OR. It provides overcurrent protection for both directions of motor rotation, and does not alter trip points for the individual legs. Trip point is calculated with aid of the following expression.

$$I_{LIMIT} = \frac{V_{SENSE} (R_{SENSE} + r_{m(on)})}{r_{a(on)} \cdot R_{SENSE}}$$

Where:

V_{SENSE} is sense voltage

R_{SENSE} is the mirror to source sense resistor

$r_{m(on)}$ is mirror active resistance = 112 ohms

$r_{a(on)}$ is source active resistance = 0.14 ohms

Since the current limit threshold in the MC33033 is 100 mV, current limiting will occur when V_{SENSE} reaches 100 mV. For the circuit in Figure 3, plugging in 100 mV for V_{SENSE} and $R_{SENSE} = R_6 = 22$ ohms yields:

$$I_{LIMIT} = 0.1(47 + 112)/0.14 \cdot 22 = 5.2 \text{ Amps}$$

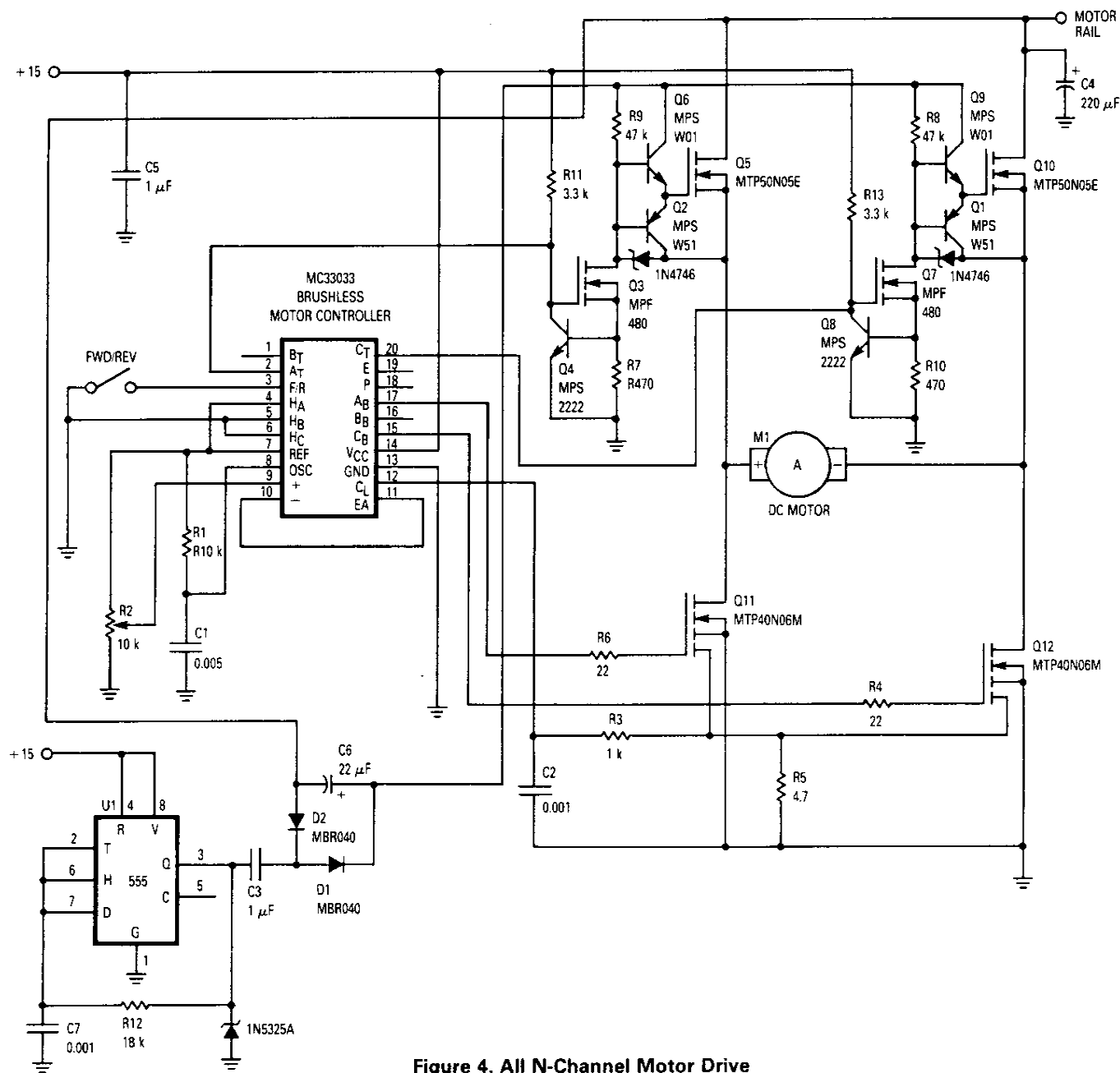


Figure 4. All N-Channel Motor Drive

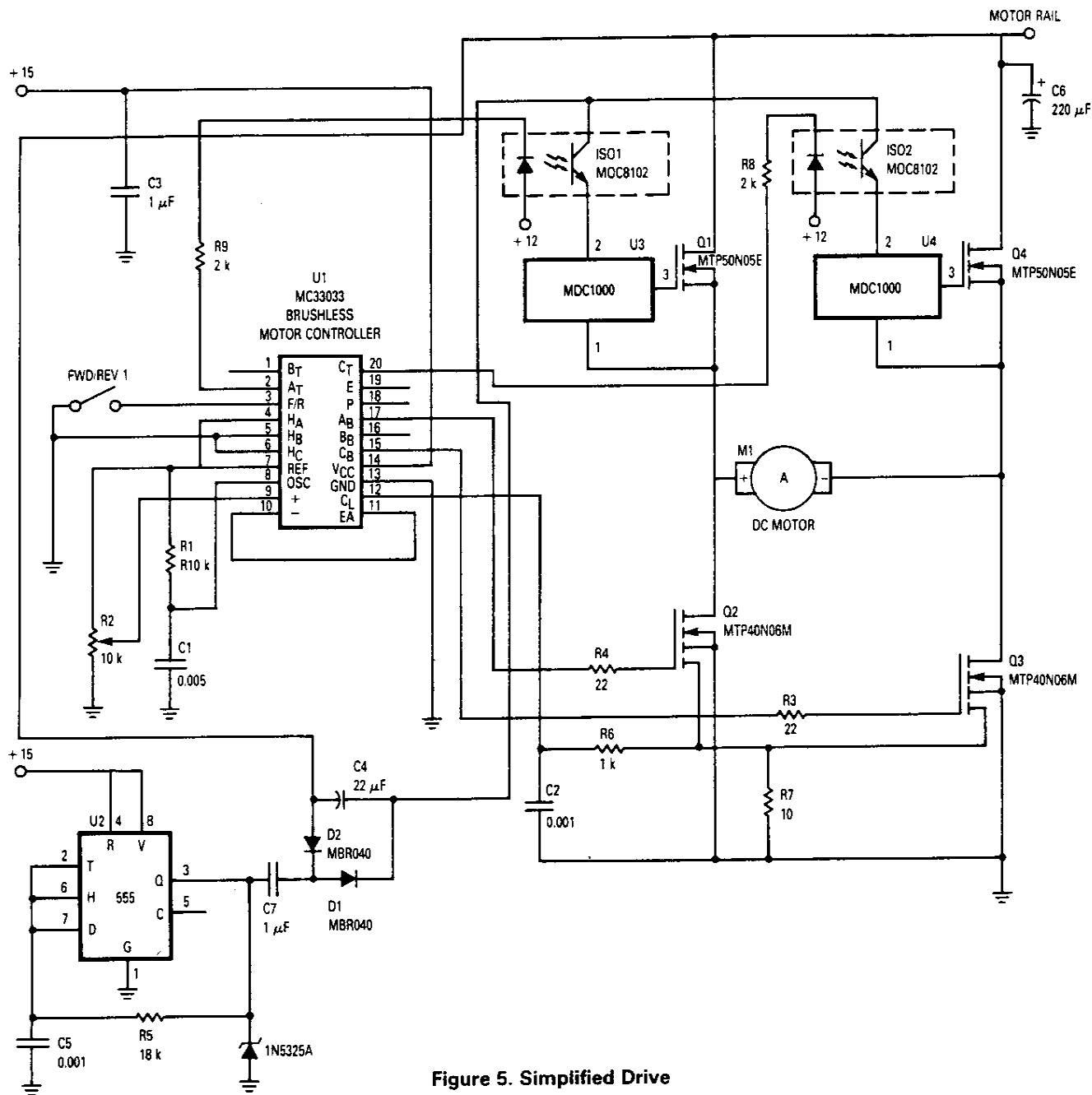


Figure 5. Simplified Drive

Compared to a power sense resistor in series with the motor, 1/2 watt (5.0 A • 0.1 V) of dissipation is saved by using SENSEFETs in the lower half bridge.

The discrete MTP40N06M SENSEFETs that are used in Figure 4 save proportionately more power. For this device, $r_{a(on)}$ and $r_{m(on)}$ are 17 milliohms and 16 ohms respectively. I_{LIMIT} is therefore $0.1(4.7 + 16)/0.017 \cdot 4.7 = 26$ Amps. In this application $26 \text{ A} \cdot 0.1 \text{ V} = 2.6$ watts is saved by using SENSEFETs.

CONCLUSION

The new components that have been described here can be used individually or in combination to make brush motor drives simpler and easier to design. By combining the MC33033's easy to use control capability with an MPM3002 integrated H-Bridge, very simple yet high performance fractional horsepower drives can be built. At higher power levels, N-Channel drive is simplified by gain stable MOC8102 Optocouplers and a new MOS turn-off device.

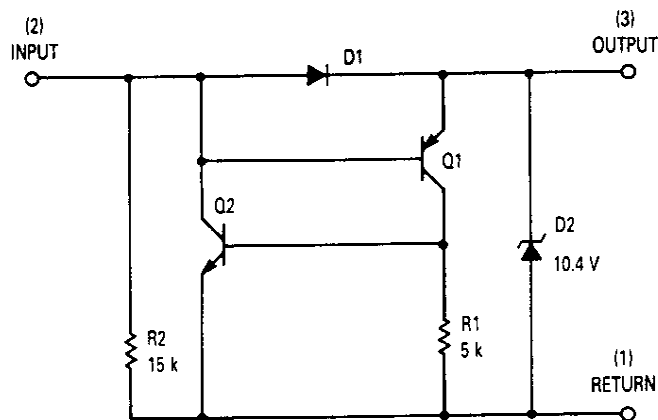


Figure 6. MDC1000

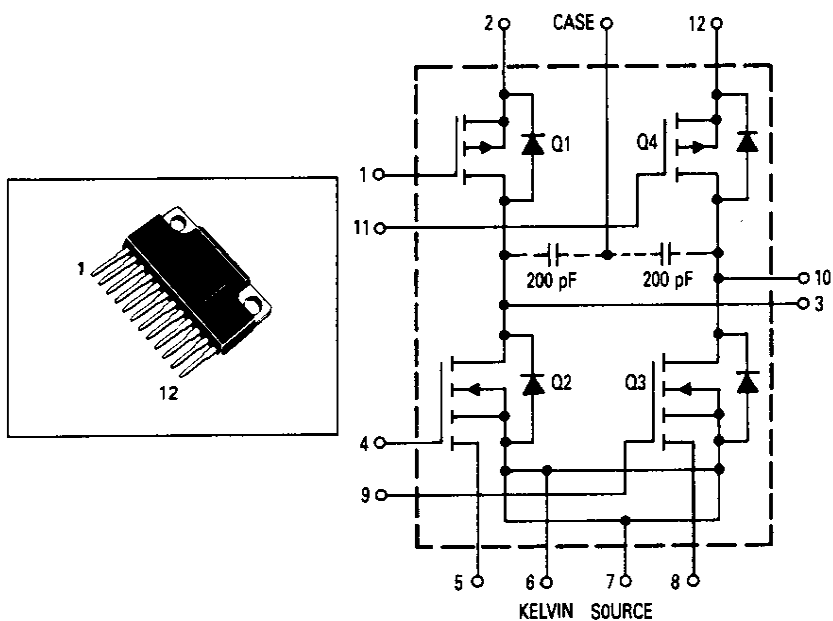



Figure 7. MPM3002

Motorola reserves the right to make changes without further notice to any products herein to improve reliability, function or design. Motorola does not assume any liability arising out of the application or use of any product or circuit described herein; neither does it convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

Literature Distribution Centers:

USA: Motorola Literature Distribution; P.O. Box 20912; Phoenix, Arizona 85036.

EUROPE: Motorola Ltd.; European Literature Center; 88 Tanners Drive, Blakelands, Milton Keynes, MK14 5BP, England.

JAPAN: Nippon Motorola Ltd.; 4-32-1, Nishi-Gotanda, Shinagawa-ku, Tokyo 141 Japan.

ASIA-PACIFIC: Motorola Semiconductors H.K. Ltd.; Silicon Harbour Center, No. 2 Dai King Street, Tai Po Industrial Estate, Tai Po, N.T., Hong Kong.



MOTOROLA

AN1078