

## **50W Current Mode Controlled Offline Switch Mode Power Supply Working over 50% duty cycle using the UC3842A**

Prepared by  
François LHERMITE  
Industrial Applications Engineering

The design of a medium power OFFLINE Switch Mode Power Supply based on the Fly-back architecture has been widely developed for the voltage controlled PWM technique.

This application note describes a way to improve the dynamic characteristics of this power supply using a technique called "Current Controlled PWM". A dedicated bipolar integrated circuit, UC 3842A, has been used to achieve the current control, regulation and safety features.


This paper covers the following aspects:

- Power elements dimensioning for a given specification (power switch/inductor)
- Building the current mode regulation
  - Current sensing loop
  - Feed back loop
- Description of instability occurring at duty cycles greater than 50%
- Description of a compensation network to cancel the instability phenomenon
- Discussion on the compensating network impact on power supply performances



## FLYBACK CURRENT MODE CONTROL STRUCTURE

Current sensing is performed by means of a low value series resistor as shown in Figure 1.

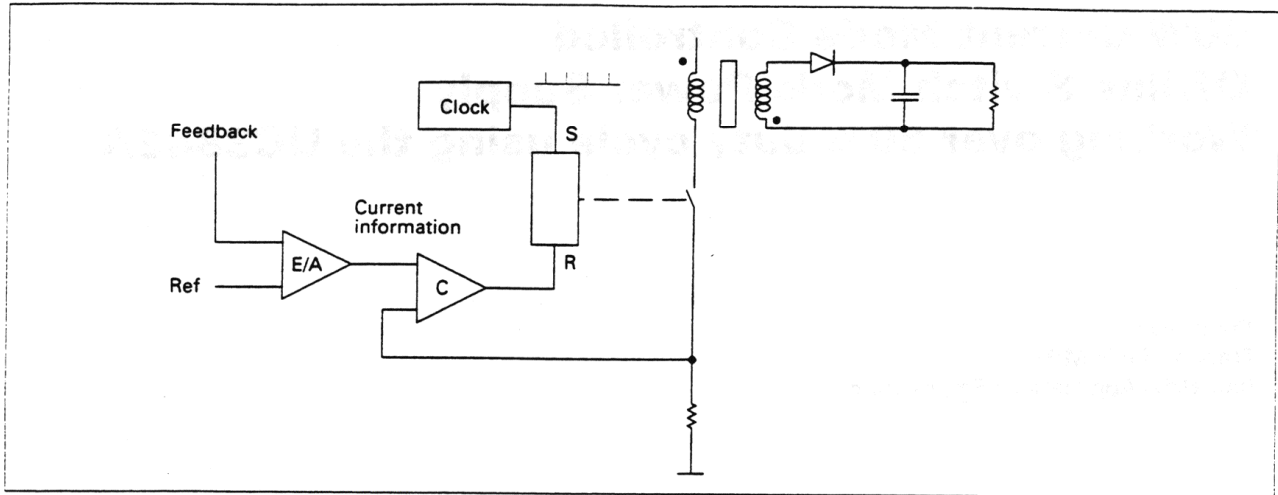

**Figure 1**  
**Flyback Current Mode Control Structure**


The power switch can be a high voltage bipolar transistor or a high voltage N channel MOSFET. The switch choice is a compromise between performances, safety margin and cost. However these three aspects are not discussed in this study. The adopted switch is a MOS transistor. The bipolar NPN transistor could also have been selected.

## POWER ELEMENTS DIMENSIONING

Power supply specification:

$V_{\text{mains}}$	: 85Vac to 245Vac
$P_{\text{out}}$	: 50W nominal 100mW standby mode
$V_{\text{out}}$	: 5V



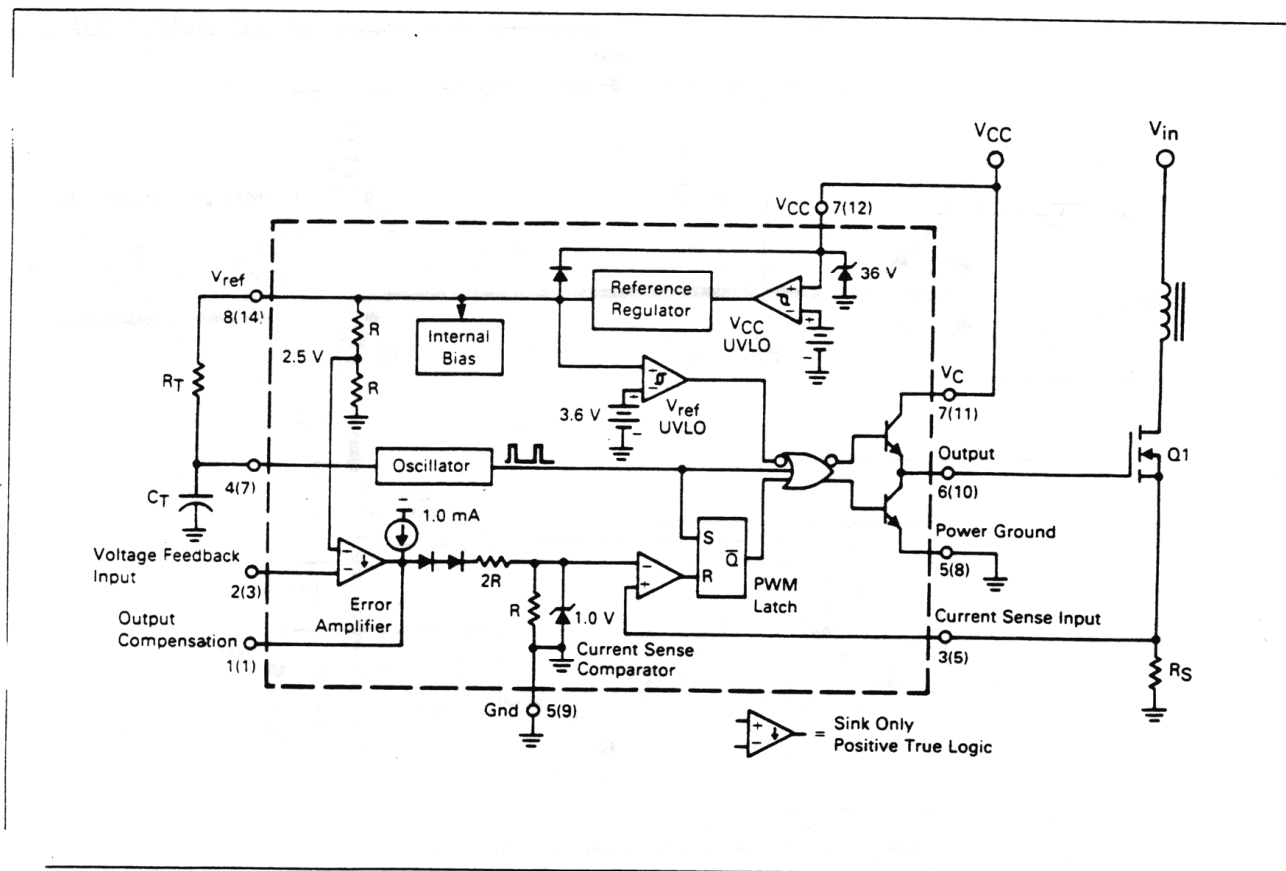


**Figure 3**  
**UC3842A Representative Block Diagram**

The current flowing in the primary winding is represented by Figure 4.

When the power switch achieves the ON state the current starts climbing from a level which represents the valley current value.

The average current ( $I_{av}$ ) represented by the dotted line is related to the following working parameters:

$P_{max}$	maximum output power
$V_{in min}$	minimum rectified mains voltage
$d$	duty cycle
$F$	working frequency
$L_p$	inductance of primary winding

 

**Figure 4**  
**Primary Winding Current Flow**

From the current waveform we can write

eqn. 1 
$$I_{av} = \left( I_{peak} - \frac{\Delta I_p}{2} \right) d$$

where  $\Delta I_p$  represents the current ripple of the primary inductor current.

The current ripple is :

eqn. 2 
$$\Delta I_p = \frac{V_{in} d}{L_p F}$$

The energy stored in the primary inductor during one switching period is given by:

eqn. 3 
$$W_p = \frac{1}{2} L_p (I_{peak})^2$$

This energy can also be expressed as a function of the output power divided by the efficiency of the power supply:

eqn. 4 
$$W_p = \frac{P_{out} T}{\eta}$$

From the equations 2, 3 and 4 we can extract the peak current value:

eqn. 5 
$$I_{peak} = \sqrt{\frac{2 P_{out} \Delta I_p}{\eta V_{in} d}}$$

From the equations 3 and 4 we can extract the required primary inductor value:

eqn. 6

$$L_p = \frac{2 P_{out} T}{\eta (I_{peak})^2}$$

From the magnetic core manufacturer catalogue a core choice can be made as a first approximation. This specific core is identified by the effective core area  $A_e$ .

The chosen material indicates the allowable saturation flux density  $B_{max}$ .

The primary winding now can be computed using:

eqn. 7

$$N_p = \frac{L_p I_{peak max} 10^8}{A_e B_{max}}$$

And the air gap length becomes:

eqn. 8

$$l_g = \frac{0.4 \pi N_p I_{peak max}}{B_{max}}$$

The next step is the primary/secondary winding ratio calculation.

The input and output voltages are governed by the relationship:

eqn. 9

$$N_s = \frac{N_p (V_{out} + V_F) (1 - d_{max})}{V_{in min} d_{max}}$$

In this formula the power transistor saturation voltage has been neglected.

The voltage  $V_{out}$  is relatively low and thus the diode forward voltage drop ( $V_F$ ) cannot be neglected.

The primary/secondary transformer ratio is:


eqn. 10

$$N = \frac{N_p}{N_s}$$

## CALCULATION PROCESS

Figure 5 shows the process to be followed to make the optimum choice for every power element.

As a switchmode power supply is largely a compromise between every working parameter, the designer will first have to establish a requirement priority list.

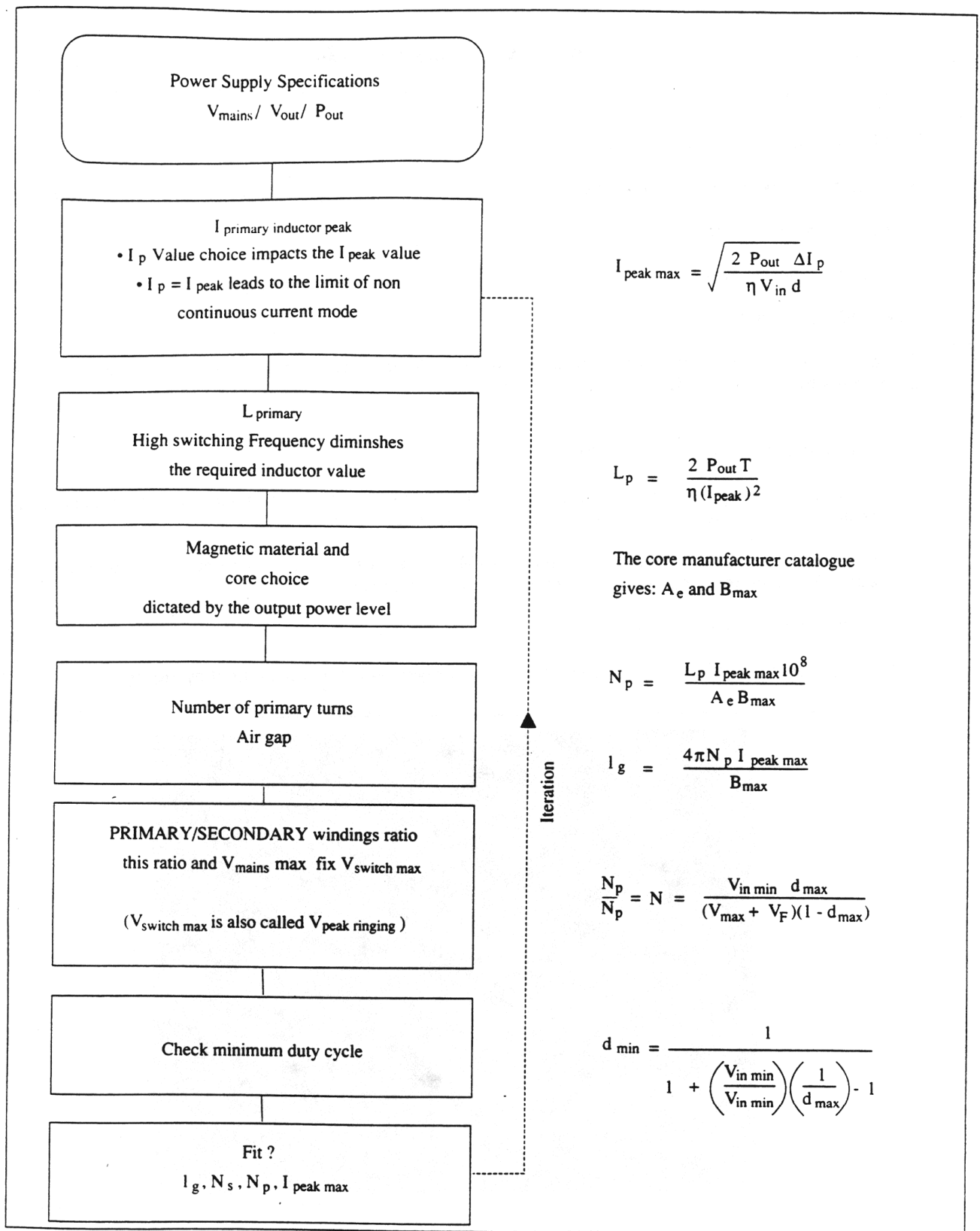

**Figure 5**  
**Calculation and Choice Process Chart**

The main difficulties encountered in a Switch Mode Power Supply are:

- high  $dV/dt$  and  $dI/dt$
- high voltages on the power switch
- rejected interferences on mains line
- conduction and switching losses
- power supply recovery time

#### PARAMETER CHOICE

The above items are related to the working parameters. What follows is a discussion on the way to adapt these parameters to reduce the impact of the listed difficulties.

a) The high  $dI/dt$  can be reduced in two ways:

- diminishing the  $I_{peak}$  value - a large  $L_p$  value will keep the current ripple at a lower level, but consequently a large inductor value will increase the power supply recovery time.
- lowering the switching speed. When using a TMOS, a series resistor in the gate connection will soften the edge. As a counter effect this will increase the switching losses.

b) High voltage on the power switch

The voltage waveform that has to be sustained by the power switch is represented by Figure 6.

 


Figure 6  
High Voltage on Power Switch



Two voltage levels have to be considered:

1. The *settled voltage* whose value is given by:


eqn. 11 
$$V_{\text{settled}} = V_{\text{in}} + N (V_{\text{out}} + V_F)$$

Substituting the ratio  $N$  from equation 9 into equation 11 gives:

eqn. 12 
$$V_{\text{settled max}} = V_{\text{in max}} + V_{\text{in min}} * \frac{d_{\text{max}}}{1 - d_{\text{max}}}$$

 2. The *peak voltage* (ringing peak voltage)

The switch-off sequence is shown enlarged in Figure 7.



- Time 1:** The current flowing through the snubbing capacitor exhibits a shape which is dictated by  $L_p + L_{leakage}$  and  $C_{snubber}$  added to the transformer stray capacitance and transistor heatspreader capacitance (dotted curve in Figure 7).
- Time 2:** The switch is OFF. The secondary diode is not yet conducting. The snubbing capacitor receives the whole inductor current.
- Time 3:** The secondary diode begins conducting.  
 The voltage across  $L_p$  remains constant.  
 The current flowing through the snubbing capacitor is roughly equal to  $I_{peak}$ .  
 An oscillating energy transfer takes place between  $L_{leakage}$  and  $C_{snubber}$ .  
 The ringing decay is controlled by the snubbing resistor (only active during the negative conduction).

The peak ringing voltage is given by:

eqn. 13

$$V_{ringing} = I_{csnub} \sqrt{\frac{L_{leakage}}{C_{snub} + C_{oss} + C_{stray}}}$$

eqn. 14

$$\begin{aligned} \text{with } I_{csnub} &= I_{peak} \\ C_{oss} &= \text{output TMOS capacitance} \\ C_{stray} &= \text{transformer stray capacitance} \end{aligned}$$

It becomes:

eqn. 15

$$V_{peak\ ringing} = V_{settled} + V_{ringing}$$

So the designer can try to lower the peak voltage by choosing a low duty cycle in order to reduce the N ratio. As a counter effect the transistor peak current will be higher.

It is clear that special care in the coupled inductors will reduce the leakage inductance thus reducing the ringing.

**Note:**

Assuming a correct transistor switching behaviour i.e. no current and voltage appearing simultaneously, the  $t_{OFF}$  switching time has no impact on the peak voltage.

**c) Rejected interferences on mains line**

The primary current is flowing in the power network 300V rail and ground rail.

This current is delivered by the rectifying bridge and smoothed by the large value electrolytic smoothing capacitor. This kind of capacitor presents a high ESL (equivalent series inductor) which largely diminishes its high frequency smoothing properties.

Thus the high  $di/dt$  developed by the switch are creating noise voltages which are directly rejected on the mains line.

There are two ways to reduce these interferences :

- lower the  $di/dt$  by decreasing the switching speed.
- insert a symmetrical low pass filter in the mains line.

## POWER COMPONENT CALCULATION

<b>Table 1</b> <b>Units used for Power Components Calculation</b>		
Variable	Unit	Abbreviation
$I_{peak}$	Amperes	A
$P_{out}$	Watts	W
$V_{in}$	Volts	V
T	Microseconds	$\mu S$
$A_e$	Square Centimetres	cm <sup>2</sup>
$B_{max}$	Gauss	G
$N_p$	Number of turns	-
$L_p$	millHenrys	mH
d	decimal notation	-
$\eta$	percent	%

We can adopt an estimated efficiency of 75% and a maximum duty cycle of 0.6.

Let us choose a current ripple of  $\Delta I_p = 0.5A$  and a Period  $T = 10\mu s$

Switch peak current:

eqn. 16 
$$I_{peak\ max} = \sqrt{\frac{2 \times 50\ W \times 0.5A}{75\ \% \times 85V \times \sqrt{2} \times 0.9 \times 0.6}}$$

$$I_{peak\ max} = 1\ A$$

The factor 0.9 gives an estimation of the  $V_{in}$  valley ripple voltage.

Primary inductance:

eqn. 17

$$L_p = \frac{2 \times 50 \text{ W} \times 10 \mu\text{s}}{75 \% \times (1 \text{ A})^2}$$

$$L_p = 1.30 \text{ mH}$$

We choose the ETD34 core in B52 material.

From the manufacturer's catalogue we get:

Effective core area:  $0.97 \text{ cm}^2$

Maximum Flux density: 3200 Gauss

Number of primary turns:

eqn. 18

$$N_p = \frac{1.30 \text{ mH} \times 1 \text{ A} \times 10^8}{0.97 \text{ cm}^2 \times 3200 \text{ G}}$$

$$N_p = 42 \text{ turns}$$

Core air gap:

eqn. 19

$$l_g = \frac{0.4 \times \pi \times 42 \text{ turns} \times 1 \text{ A}}{3200 \text{ G}}$$

$$l_g = 0.17 \text{ mm}$$

Primary/Secondary winding ratio:

eqn. 20

$$N = \frac{85 \text{ V} \times \sqrt{2} \times 0.9 \times 0.6}{(5 \text{ V} + 0.5 \text{ V})(1 - 0.6)}$$

$$N = 30$$

Hence:

eqn. 21

$$N_{5V} = \frac{N_p}{N} = \frac{42}{30} = 1.4 \text{ turns}$$

We can now check if there is no saturation problem for this peak current value. It becomes:

eqn. 22

$$N_p = I_{\text{peak max}} = 42 \text{ turns} \times 1 \text{ A} = 42 \text{ A} \times \text{turns}$$

The ETD34 in B52 material fits our power supply requirements.

## POWER SWITCH CHOICE

From equation 15 we can compute the maximum voltage which will be withstood by the switch in normal and extreme conditions.

$$\text{eqn. 23} \quad V_{\text{peak ringing}} = 245V \times \sqrt{2} + \frac{85V \times \sqrt{2} \times 0.9 \times 0.6}{(1 - 0.6)} + 1 \text{ A} \times \sqrt{\frac{20 \mu\text{H}}{470 \text{ pF} + 150 \text{ pF} + 100 \text{ pF}}}$$

$$V_{\text{peak ringing}} = 722 \text{ V}$$

Thanks to its "easy to drive" capabilities the power MOSFET is a good choice. A high voltage TMOS should be chosen in order to get maximum safety margin. The MTP4N85 fits our requirements.

For this transistor we get :

$$\text{eqn. 24} \quad \begin{aligned} R_{\text{DS(on)}} &= 4 \Omega \\ V_{\text{DSS}} &= 850 \text{ V} \end{aligned}$$

## SECONDARY DIODE CHOICE

The current flowing in the secondary side is directly related to the primary current amplitude and the primary/secondary winding ratio.

The peak value is given as follows:

$$\text{eqn. 25} \quad I_{\text{peak diode}} = I_{\text{primary peak}} N$$

## WIRE SIZE

Let us calculate the skin depth for the considered frequency of 100kHz.

The equation is as follows:

$$\text{eq. 26} \quad \delta = \sqrt{\frac{2\rho}{\omega \mu_0}} \quad \text{with} \quad \omega = 2\pi F \text{ and } F = \frac{1}{T}$$

where  $\rho$  is the copper resistivity in ohm/metre  
 $\mu_0$  is the absolute vacuum permeability  
 $\omega$  is the working radian frequency

$$\text{eqn. 27} \quad \delta = \sqrt{\frac{2 \times 1.7 \cdot 10^{-8} \Omega/\text{m}}{2\pi \times 100 \text{ kHz} \times 4\pi \cdot 10^{-7}}}$$

$$\delta = 0.2 \text{ mm}$$

This skin depth implies the use of multi-layer metal foil or multi-strand Litz wire for the secondary winding.

The winding space for the ETD34 is 20.9mm.

Considering a 0.2mm skin depth we can use a 0.3mm copper foil.

To comply with the isolation norms we have to keep 2mm free space on the two bobbin edges, so the useful winding space becomes:

$$\begin{aligned} W &= 20.9 - (2 * 2\text{mm}) \\ &= 16.9\text{mm} \end{aligned}$$

The corresponding copper area is

$$A_{\text{cu}} = 16.9 \times 0.3 = 5\text{mm}^2$$

For the 10A average output current we get a current density of  $2\text{A/mm}^2$  which is largely acceptable.

Auxiliary winding:

This winding performs two functions:

- Self powering after power supply start-up
- Feedback voltage sensing

The working voltage of the UC3842A is around 15V, so the number of turns is:

$$N_{\text{aux}} = 3 * N_{\text{SV}} = 5 \text{ turns}$$

 


Figure 8  
Power Supply Instability

### Stability considerations

Constant frequency and controlled current mode power supplies used at duty ratios above 50% exhibit instability even in open-loop configuration.

The nature of the instability appears in Figure 8.

The "ON" current has a rising slope  $m_1$ .

The "OFF" current is the secondary current seen from the primary side and scaled with the primary/secondary winding ratio. The OFF slope is  $m_2$  (see equation 35).

The unstable condition is encountered when a short variation in  $V_{in}$  or in the controlled current level arises.

This incident  $\Delta I_0$  is reflected at the end of the ON period and thus the valley current just before the turn ON is increased in amplitude up to  $\Delta I (m_2/m_1)$ .

This variation is also reflected in the next switching cycle and thus the next valley current will be  $[\Delta I (m_2/m_1)](m_2/m_1)$ .

The perturbation is then multiplied on each cycle by  $m_2/m_1$  and alternately increases and decreases the valley inductor current.

After  $n$  cycles the inductor current will reach zero and the process recommences until the feedback loop reacts.

This phenomenon is normally not destructive but produces a switching instability and deteriorates the power supply dynamic performances.

The theory establishes that this instability can be cured for the buck boost and the Fly-back converters by adding to the current sense information a compensating slope  $m_c$  such as:

eqn. 28

$$\Delta I_n = \left( \frac{m_2}{m_1} - \frac{m_c}{m_c} \right) \Delta I_{n-1}$$

Perturbations decrease when the multiplier of  $\Delta I_{n-1}$  is less than one.

We can also write after  $n$  cycles:

eqn. 29


$$\Delta I_n = (-1)^n \left( \frac{m_2}{m_1} - \frac{m_c}{m_c} \right)^n \Delta I_{incident}$$

Two kinds of ramp can be considered:

- Ramp to ensure a marginal open loop stability.
- Ramp to ensure optimal open loop stability.

These two ramps are shown in Figure 9.

( $d > 50\%$ )

 

**Figure 9**  
**Compensating Ramps**

The lowest curve is related to the marginal stability in which the current perturbation remains constant - it neither decreases nor settles down.

We get:

eqn. 30 
$$m_c = \frac{m_2 - m_1}{2}$$

The upper curve eliminates any perturbation within one switching cycle. The optimal compensating ramp gives:

eqn. 31 
$$m_c (\text{opt}) = m_2$$

Note that the optimum compensating ramp has a significant impact on the current limiting characteristic.

( $d > 50\%$ )



## STRUCTURAL INSTABILITY

The working conditions (low mains and high output power) lead to a continuous conduction mode in the core windings. In fact, continuous conduction mode (CCM) in the fly-back structure means that the magnetic field created by the [ampere \* turns] never falls down to zero.

In this configuration and using the current mode control technique to achieve the output regulation an instability takes place when the duty cycle exceeds 50% (see previous " $d > 50\%$ " section). A way to cure this problem is to modify the current information in such a manner that the ON angle becomes as it should be if the duty cycle was less than 50%.

To perform this angle modification we can act on the error amplifier input or on the current sense input. The data sheet UC3842A/D shows two different ways to set up the current compensation. The described application achieves this compensation in a slightly different manner.

This solution requires some additional low cost components to generate a quasi linear sawtooth only during the  $t_{on}$  period. The advantage of this technique is to diminish the  $dV/dt$  seen by the current comparator at turn-on. In this way start-up and output short circuit behaviour is improved.

As shown in Figure 10, the sense voltage is the sum of the voltage developed across the sensing resistor  $R_s$  which represents the actual primary current and the compensating ramp.

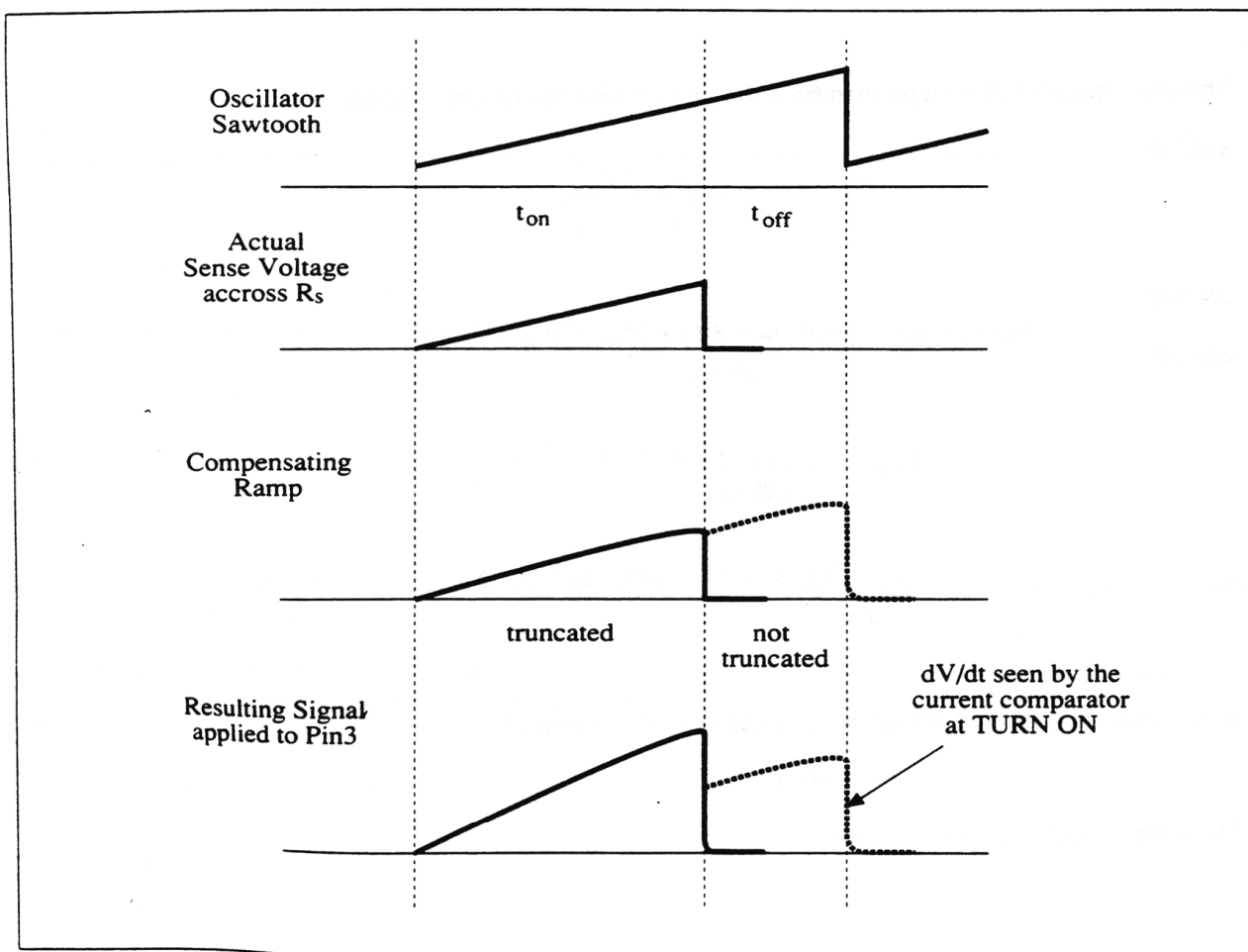


Figure 10  
Compensating Signal

## COMPENSATION SLOPE CHOICE

As already mentioned, the short circuit current is affected by the additional ramp. In order to lower the compensation impact on the short circuit current limitation but still retain a good stability margin we choose:

$$\text{eqn. 32} \quad \frac{m_2 - m_1}{2} \leq m_c \leq m_2$$

$m_2$  is the absolute value of the secondary slope.

The secondary diode current is:

$$\text{eqn. 33} \quad I_{\text{diode}} = I_{\text{diode peak}} - \frac{V_{\text{out}} + V_F}{L_s} t_{\text{OFF}}$$

Seen from the primary side and assuming a tight coupling we can write:

$$\text{eqn. 34} \quad L_s = \frac{L_p}{N^2}$$

The absolute secondary slope seen from the primary side can be expressed as:

$$\text{eqn. 35} \quad m_2 = \frac{(V_{\text{out}} + V_F) N}{L_p}$$

We get:

$$\text{eqn. 36} \quad m_2 = \frac{(5V + 0.5V) \times 30}{1.30 \text{ mH}} = 125 \times 10^3$$


$$m_{1 \text{ min}} = \frac{110 \text{ V}}{1.30 \text{ mH}} = 83 \times 10^3$$

$$\frac{m_2 - m_1}{2} = \frac{(124 - 83)}{2} \times 10^3 = 20 \times 10^3$$

According to equation 32 we can adopt a compensating ramp of:

$$m_c = 80 \times 10^3$$

The adder circuit is shown in Figure 11.

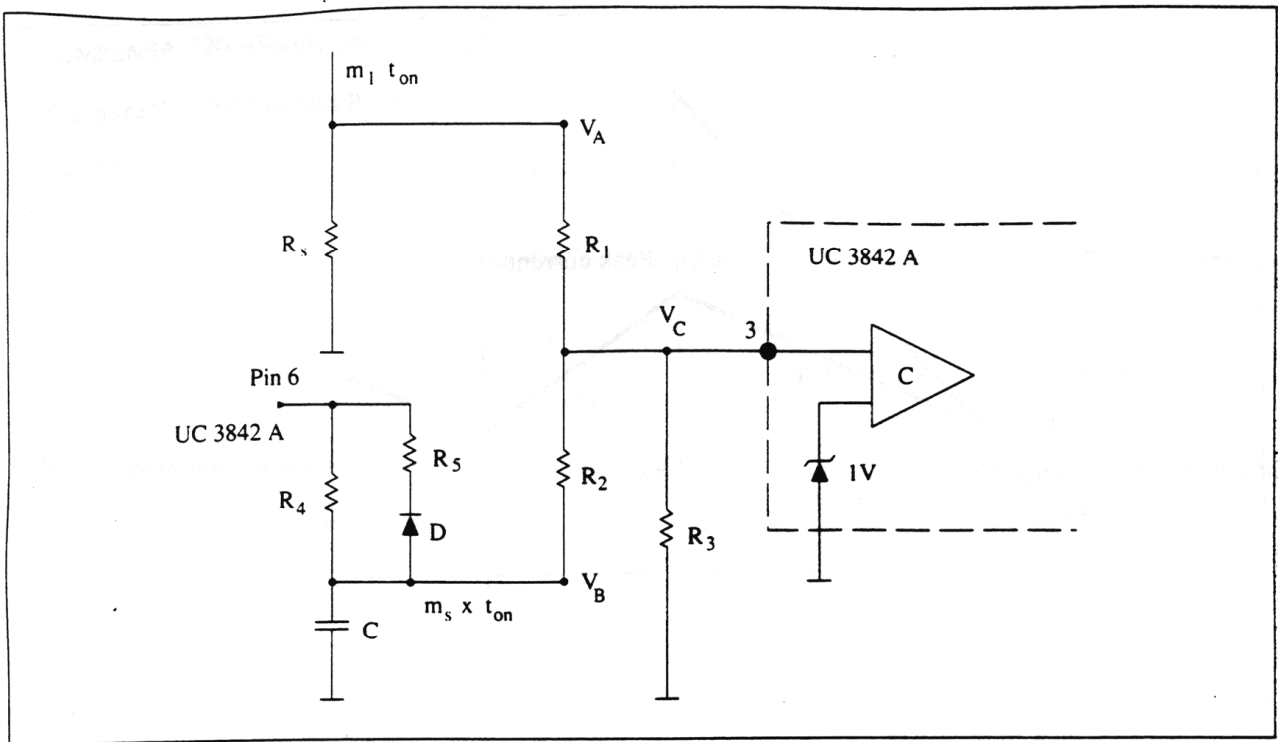

**Figure 11**  
**Adder Circuit**

The resistors  $R_1$ ,  $R_2$  and  $R_3$  perform the actual current signal and the compensating slope addition.



The adder equation is :

eqn. 37

$$V_C = \frac{R_3 (R_1 V_B + R_2 V_A)}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

The network  $R_4$ ,  $R_5$ ,  $C$  and  $D$  connected on the drive output Pin6 build the compensating waveform. Figure 12 shows the resulting quasi sawtooth.

The power supply voltage feedback is made by means of an auxiliary winding working in the fly-back way. Consequently the  $V_{cc}$  voltage is constant and the square wave Pin 6 signal amplitude is constant.

  

**Figure 12**  
**Quasi Sawtooth**

Thus the compensating signal has a constant slope  $m_s$  whose value is:

1. 38

$$m_s = \frac{3.6 \text{ V}}{6\mu s} = 0.6 \text{ V}/\mu s$$

## COMPENSATION ADDER CALCULATION

The current flowing across  $R_S$  is:

$$\text{eqn. 39} \quad I_L = I_{\text{valley}} + m_1 t_{\text{on}}$$

From equations 33 and 37 we can express the "current sense" pin3 voltage as a function of  $R_S$ ,  $I_V$  and the adder network resistors.

$$\text{eqn. 40} \quad V_C = R_S I_V + \left( m_1 R_S R_2 + m_S R_1 \right) \frac{R_3 t_{\text{on}}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

The **compensation factor** is the ratio between the two added expressions between brackets in the above equation.

We can define this K factor as:

$$\text{eqn. 41} \quad K = \frac{m_1}{m_S} = \frac{m_1 R_S R_2}{m_S R_1}$$

The "compensation slope choice" section discussed how to choose  $m_c$  and the  $m_c$  limits.

The compensation slope  $m_c$  enables to compute the current sense resistor value  $R_S$ .

## $R_S$ CALCULATION

Extracting  $R_2$  from equation 41 and solving  $V_C$  in equation 40 we can express  $V_C$  as a function of  $I_V$ ,  $R_1$ ,  $R_3$ ,  $R_S$ ,  $m_1$ ,  $m_S$ , and K.

eqn. 42

$$V_C = R_S^2 \left( -\hat{m}_1 R_3 I_V \right) - R_S \left[ (K+1) m_1 m_S R_3 t_{\text{on}} + K m_S I_V (R_3 + R_1) - m_1 R_3 \right] + K m_S (R_3 + R_1)$$

To simply solve this 2nd order equation the  $R_1$  and  $R_3$  choice can be primarily made.

Let us choose:

$$R_1 = 1 \text{ K}\Omega$$

$$R_3 = 5 \text{ K}\Omega$$

eqn. 43

From the sections "Power component calculation" and "Compensation slope choice" we have :

eqn. 44

$$I_{\text{valley}} = I_{\text{peak}} - I_{\text{ripple}} = 0.5 \text{ A}$$

$$K = 1$$

$$\text{with } m_1 = 80 \cdot 10^3 \text{ A/S}$$

$$\text{and } m_S = 600 \cdot 10^3 \text{ V/S}$$

The roots of the equation 42 are:

$$\text{eqn. 45} \quad R_s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$\text{where: } a = m_1 R_3$$

$$b = (K+1) m_1 m_S R_3 t_{on} + K m_S I_V (R_3 + R_1) - m_1 R_3$$

$$c = K m_S (R_1 + R_3)$$

The sole root is :

$$R_s = 0.81\Omega$$

From equation 41 we get:

$$\text{eqn. 46} \quad R_2 = \frac{K m_S R_1}{m_1 R_s}$$

$$R_2 = \frac{1 * 600 * 10^3 \text{ V}/\mu\text{s} * 1\text{k}\Omega}{80 * 10^3 \text{ A}/\mu\text{s} * .81\Omega}$$

$$R_2 = 9.3\text{k}\Omega$$

For safety and reliability reasons, the power supply short-circuit behaviour is a key point.


Two kinds of short circuit can be considered:

- on the load
- on the secondary diode

## LOAD SHORT CIRCUIT

The first case shows a strong output voltage decrease. The control voltage reacts dictating a high primary current level. The current sense comparator works at the Pin 3 clamped voltage i.e. 1 volt.

The primary inductor current appears in Figure 13.

 

**Figure 13**  
**Primary Inductor Current**

In this configuration the duty cycle is:

eqn. 48 
$$d = \frac{V_F N}{V_{in}}$$

For the minimum mains we get:

eqn. 49 
$$d_{max} = \frac{0.6V \times 30}{85V \times \sqrt{2} \times 0.9} = 0.17$$

which gives:

eqn. 50 
$$t_{on \text{ max load sh. ckt}} = 1.7 \mu s$$


From equation 39 we can get the valley current  $I_V$  and can express the Load Short Circuit peak current as follows:

Load Short Circuit Valley Current:  $I_{VLSC}$   
Load Short Circuit Peak Current:  $I_{PLSC}$

eqn. 51 
$$I_{VLSC} = I_{PLSC} - \frac{V_{in} \sqrt{2} 0.9 t_{on}}{L_m}$$

From equation 40 and taking  $V_{cmax} = 1$  volt with the previously chosen and computed values  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_s$  we get:

eqn. 52 
$$I_{PLSC} = \frac{0.835 + 0.14}{R_s} \text{ Amperes}$$

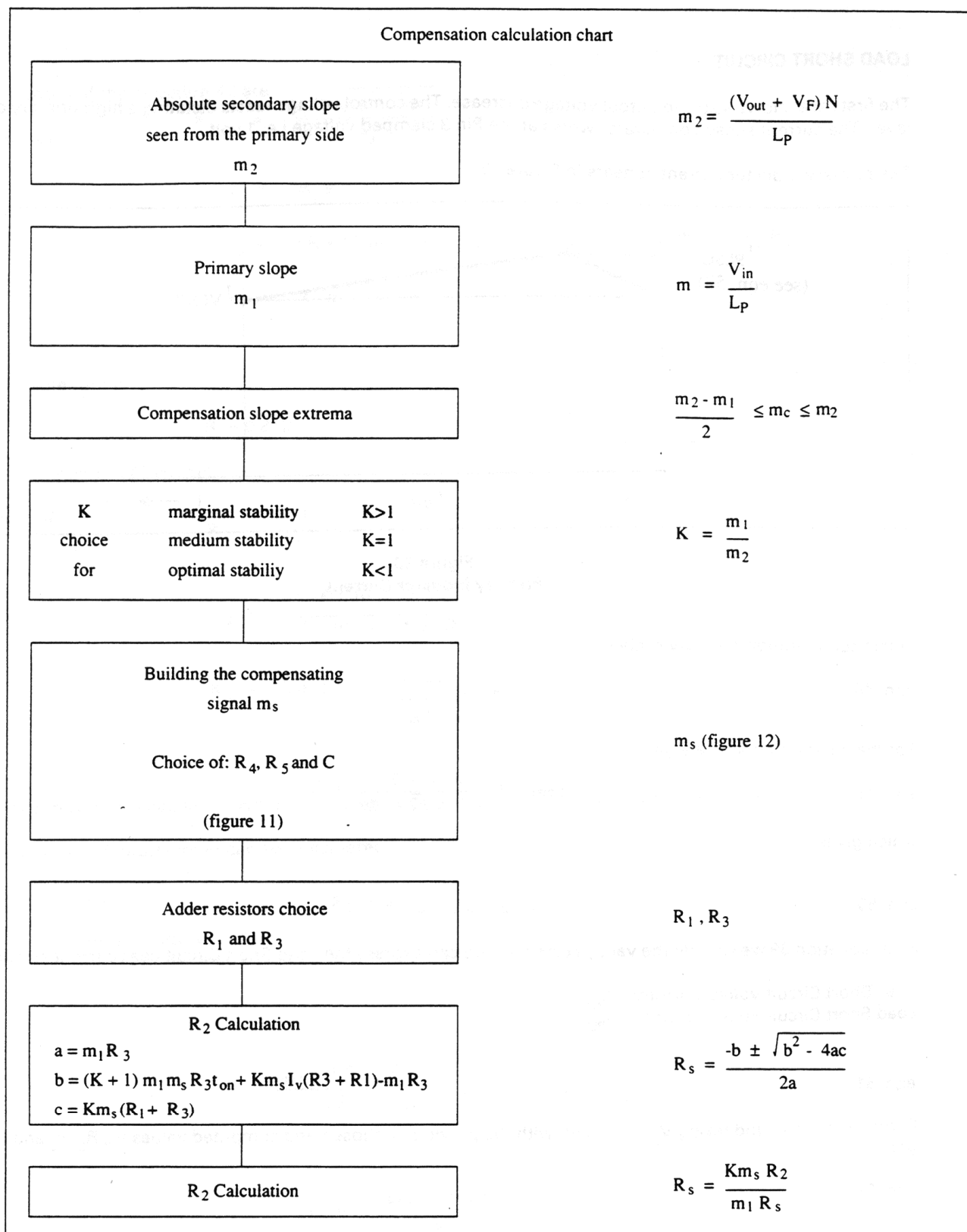

**Figure 14**  
**Compensating Calculation Chart**



## DIODE SHORT CIRCUIT

Diode Short Circuit Peak Current:  $I_{PDSC}$


This particular configuration can be encountered subsequently to a load short circuit in which case the power switch current is mainly dictated by the leakage inductance. The resulting current rising slope is much higher than the compensation slope and we can approximate:

eqn. 53 
$$I_{PDSC} = \frac{(R_1 + R_3 // R_2) V_{cmax}}{(R_1 + R_3 // R_2) R_s}$$

which gives:

eqn. 54 
$$I_{PDSC} = \frac{V_{cmax} (R_1 R_3 + R_1 R_2 + R_3 R_2)}{R_s R_2 R_3}$$

This current slope is shown in Figure 15.

 

**Figure 15**  
**Diode Short Circuit Peak Current**

We can summarize the above results for 3 different K factors :

			For $V_{\text{mains}} = 85 \text{ V}$	
K	$R_s$	$R_2$	$I_{\text{PDSC}}$	$I_{\text{PLSC}}$
Marginal stability $K = 4$	$1 \Omega$	$30 \text{ K}\Omega$	$1.23 \text{ A}$	$0.97 \text{ A}$
Medium stability $K = 1$	$0.8 \Omega$	$9.5 \text{ K}\Omega$	$1.63 \text{ A}$	$1.18 \text{ A}$
Optimal stability $K = 0.64$	$0.7 \Omega$	$7 \text{ K}\Omega$	$1.92 \text{ A}$	$1.33 \text{ A}$

eqn. 55

$$R_1 = 1 \text{ k}\Omega$$

$$R_3 = 5 \text{ k}\Omega$$

$$k = \frac{m_1}{m_c}$$

$$m_1 = 80 \cdot 10^3 \text{ A/s}$$

$$m_s = 600 \cdot 10^3 \text{ V/s} \quad \frac{m_1 - m_2}{2} < m_c \leq m_2$$

## PERFORMANCES

LINE REG	$P_{\text{out}} = 50\text{W}$	$V_{\text{mains}} = 85\text{Vac}$ $V_{\text{mains}} = 245\text{Vac}$	$V_{\text{out}} = 5.16\text{V}$ $V_{\text{out}} = 5\text{V}$
LOAD REG	$V_{\text{mains}} = 220\text{Vac}$	$P_{\text{out}} = 20\text{W}$ $P_{\text{out}} = 40\text{W}$	$V_{\text{out}} = 6\text{V}$ $V_{\text{out}} = 5.6\text{V}$
$d_{\text{max}}$	$P_{\text{out}} = 50\text{W}$	@ $85 \text{ Vac}$	0.6
$d_{\text{min}}$	$P_{\text{out}} = 50\text{W}$	@ $245 \text{ Vac}$	0.34

## CONCLUSION


A complete Switch Mode Power Supply has been described. The aim of this study was not to obtain the best load and line performances and for this reason a very simple feedback network has been adopted. Excellent start-up and short-circuit behaviour have been obtained by the use of the current control mode technique. Unfortunately this high performance technique exhibits a major problem of instability which appears when the duty cycle exceeds 50%. This application note has explained this instability inherent to the current control mode. A compensating network has been implemented and a discussion allows the designer to predict its impact on the power supply general performances.

## BIBLIOGRAPHY

Stability analysis of constant frequency current mode controlled switching regulators operating above 50% duty ratio.

Richard Redl, Istvan Novak  
0275-9305/82/0000-0213\$00.75 1982 IEEE

All products are sold on Motorola's Terms & Conditions of Supply. In ordering a product covered by this document the Customer agrees to be bound by those Terms & Conditions and nothing contained in this document constitutes or forms part of a contract (with the exception of the contents of this Notice). A copy of Motorola's Terms & Conditions of Supply is available on request.

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters can and do vary in different applications. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

The Customer should ensure that it has the most up to date version of the document by contacting its local Motorola office. This document supersedes any earlier documentation relating to the products referred to herein. The information contained in this document is current at the date of publication. It may subsequently be updated, revised or withdrawn.

#### Literature Distribution Centers:

USA: Motorola Literature Distribution; P.O. Box 20912; Phoenix, Arizona 85036.

EUROPE: Motorola Ltd.; European Literature Centre; 88 Tanners Drive, Blakelands, Milton Keynes, MK14 5BP, England.

JAPAN: Nippon Motorola Ltd.; 4-32-1, Nishi-Gotanda, Shinagawa-ku, Tokyo 141, Japan.

ASIA PACIFIC: Motorola Semiconductors H.K. Ltd.; Silicon Harbour Center, No. 2 Dai King Street, Tai Po Industrial Estate, Tai Po, N.T., Hong Kong.



**MOTOROLA**

JIT PRINTED IN THE USA 1993 MPS

ANE424/D

