

Interconnections between the DS2151 or DS2153 parallel port and the Analog Devices ADSP-2181 nonmultiplexed I/O port are shown

in Figure 1. Refer to the "INTERFACING TO A NON-MULTIPLICATED BUS" application note for further information.

TRANSCEIVER – ADSP2181 INTERCONNECTIONS Figure 1

