## Using the LM1204 with **Large Horizontal Sync Widths**

National Semiconductor **Application Note 934** David Westerman March 1994





When the LM1204 was first designed, all known raster standards had a horizontal sync pulse width duty cycle under 10% of the total horizontal line period. The part was designed and is tested in production to work with up to a 10% horizontal sync duty cycle. Recently National has received requests for operating the LM1204 with horizontal sync duty cycles up to 20%. For proper detection of sync (either polarity) it is necessary to AC couple the incoming sync signal to pin 23. This enables the LM1204 to detect sync with a peakto-peak signal as low as 1.2V. Normally pin 23 receives a TTL signal. For negative going pulses there is a natural diode clamp through the substrate diode. There is no equivalent clamp for positive syncs. This causes a loss of sensitivity at pin 23 as the sync pulses become wider. An external clamp must be added to pin 23 for horizontal sync duty cycles over 10%.

The first circuit shown in Figure 1 gives an accurate clamp at 5V. With this circuit the LM1204 can operate up to a 23% duty cycle for the horizontal sync. The operation of this circuit is quite simple. The base of the 2N3906 is biased to about 4.4V. With the diode drop from pin 23, this transistor clamps the positive going pulses to 5V. By clamping the input signal at pin 23, the integrator for pulse detection will operate in its optimum range.

If the user has a system where the duty cycle of the horizontal pulse is 15% or less, then the simple diode clamp shown in Figure 2 can be used. This clamps the input pulse to pin 23 to about 5.7V. This is not quite optimum for the integrator, but is close enough to operate with 15% duty cycles for the horizontal pulse.

Some of the users of the LM1204 have added a resistor from pin 25, the integrator cap connection, to ground. Other users have tried adding a resistor from pin 23 to ground. In both cases the idea is to pull down the level for positive going pulses with large duty cycles. EITHER RESISTOR WILL RESULT IN IMPROPER OPERATION OF THE LM1204! The only acceptable method to use the LM1204 with larger horizontal sync duty cycles is to add a clamp to the incoming signal at pin 23 as covered in this application

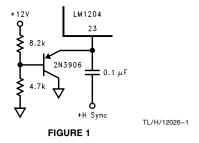

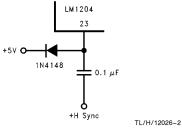

## LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

- 1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
- 2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

National Semiconductor Corporation 1111 West Bardin Road Arlington, TX 76017 Tel: 1(800) 272-9959 Fax: 1(800) 737-7018

**National Semiconductor** Europe

Fax: (+49) 0-180-530 85 86 Fax: (+49) 0-180-530 8b so Email: cnjwge@tevm2.nsc.com Deutsch Tel: (+49) 0-180-530 85 85 English Tel: (+49) 0-180-532 78 32 Français Tel: (+49) 0-180-532 8 8 8 Italiano Tel: (+49) 0-180-534 16 80

**National Semiconductor** National Semiconductor Hong Kong Ltd. 13th Floor, Straight Block, Ocean Centre, 5 Canton Rd. Tsimshatsui, Kowloon Hong Kong Tel: (852) 2737-1600 Fax: (852) 2736-9960 National Semiconductor Japan Ltd.
Tel: 81-043-299-2309
Fax: 81-043-299-2408