

## Introduction

This revision obsoletes the previous revision of this App Note, and covers additional material.

This App Note shows a simple component pre-distortion method that works for many popular Sallen-Key (also called KRC or VCVS [voltage-controlled, voltage-source]) filter sections. This method compensates for voltage-feedback and current-feedback op amps. Several examples illustrate this method.

KRC active filter sections use an op amp and two resistors to set a non-inverting gain of K. Resistors and capacitors placed around this amplifier provide the desired transfer function. The op amp's finite bandwidth causes K to be a function of frequency. For this reason, KRC filters typically operate at frequencies well below the op amp's bandwidth ( $f \ll f_{3dB}$ ).

"Pre-distortion" compensates for the op amp's finite bandwidth by modifying the nominal resistor and capacitor values. The pre-distortion method in this App Note compensates for the op amp's group delay, which is approximately constant when  $f \ll f_{3dB}$ .

One possible design sequence for KRC filters is:

1. Design the filter assuming an ideal op amp (K is assumed constant over frequency)
  - Select components for low sensitivities
  - Do a worst case analysis
  - Do a temperature analysis
2. Pre-distort the resistors and capacitors to compensate for the op amp's group delay
3. Compensate for parasitic elements

## Filter Component Pre-distortion

This section outlines a simple pre-distortion method that works for many popular Sallen-Key filters using current-feedback or voltage-feedback op amps. Other more general pre-distortion methods are available (see Reference [4]) which require more design effort.

To pre-distort your filter components:

1. Calculate the op amp's delay:

$$\tau_{oa} \approx -\frac{1}{f_c} \cdot \frac{\phi(f_c)}{360^\circ}$$

where  $\phi(f)$  is the op amp phase response in degrees, and  $f_c$  is the cutoff frequency (passband edge frequency) of your filter.

- Subtract the phase shift caused by your measurement jig from any measured value of  $\phi(f_c)$
  - The group delay is specified at  $f_c$  because it has the greatest impact on the filter response near that frequency
  - Other less accurate estimates of the op amp delay at  $f_c$  are:
    - Step response propagation delay
    - $1/(2\pi f_{3dB})$
2. The time delay around the filter feedback loop ("electrical loop delay") adds to the op amp delay. For this reason,
    - Make the filter feedback loop as physically short as possible
    - If you need greater accuracy in the following calculations, use the electrical loop delay ( $\tau_{eld}$ ) instead of the op amp delay ( $\tau_{oa}$ ):

$$\tau_{eld} \leftarrow \tau_{oa}$$

See *Appendix B* for information on calculating

$$\tau_{eld}$$

3. Replace K in the filter transfer function with a simple approximation to the op amp's frequency response
  - Start with a simple, single pole approximation:
 
$$K \leftarrow K/(1 + \tau_{oa}s), \quad s = j\omega$$
  - Alter the approximation to K and simplify:
    - *Do not create new terms* (a coefficient times a new power of s) in the transfer function *after simplifying*
    - Convert  $(1 + \tau_{oa}s)$  to the exponential form (a pure time delay) when it multiplies, or divides, the entire transfer function
    - Do not change the gain at  $\omega \approx \omega_p$  in allpass sections
    - The most useful alterations to K are:

$$\begin{aligned} \frac{K}{1 + \tau_{oa}s} &\approx K \cdot \frac{1 - (\tau_{oa}/2)s}{1 + (\tau_{oa}/2)s} \\ &\approx K(1 - \tau_{oa}s) \\ &\approx Ke^{-\tau_{oa}s} \end{aligned}$$

All of these approximations are valid when:

$$\omega \ll 1/\tau_{oa}$$

4. Use an op amp with adequate bandwidth ( $f_{3dB}$ ) and slew rate (SR):

$$f_{3dB} \geq 10f_H$$

$$SR > 5f_H V_{peak}$$

where  $f_H$  is the highest frequency in the passband of the filter, and  $V_{peak}$  is the largest peak voltage. This increases the accuracy of the pre-distortion algorithm. It also reduces the filter's sensitivity to op amp performance changes over temperature and process. Make sure the op amp is stable at a gain of  $A_v = K$ .

Appendix A contains examples using transfer functions. The next section will apply the results from Appendix A.

### KRC Lowpass Biquad

The biquad shown in Figure 1 is a Sallen-Key lowpass biquad.  $V_{in}$  needs to be a voltage source with low output impedance.  $R_1$  and  $R_2$  attenuate  $V_{in}$  to keep the signal within the op amp's dynamic range. Using Example 3 in Appendix A, we can show:

$$\frac{V_o}{V_{in}} \approx \frac{H_o}{1 + \left( \frac{1}{\omega_p Q_p} \right) s + \left( \frac{1}{\omega_p^2} \right) s^2} \cdot e^{-\tau_{oa} s}$$

$$\omega, \omega_p \ll 1/\tau_{oa}$$

where:

$$\alpha = R_2 / (R_1 + R_2)$$

$$K = 1 + R_f / R_g$$

$$H_o = \alpha K$$

$$R_{12} = (R_1 \parallel R_2)$$

$$1/(\omega_p Q_p) = R_{12} C_5 (1 - K) + R_3 C_4 + R_{12} C_4$$

$$1/\omega_p^2 = R_{12} R_3 C_4 C_5 + K \tau_{oa} R_{12} C_5$$

After selecting  $\alpha$  and  $R_{12}$ , calculate  $R_1$  and  $R_2$  as:

$$R_1 = R_{12} / \alpha$$

$$R_2 = R_{12} / (1 - \alpha)$$

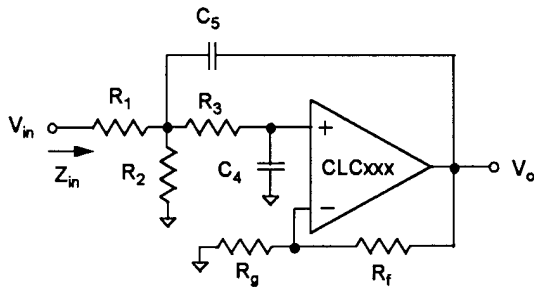


Figure 1: Lowpass Biquad

To pre-distort this filter:

- Design the filter assuming  $K$  constant ( $\tau_{oa} = 0$ ). Use low values for  $K$  so that:
  - $\tau_{oa}$  will have less impact on the biquad's response
  - For voltage-feedback op amps,  $\tau_{oa}$  will be smaller ( $\tau_{oa} \approx K$  divided by the gain-bandwidth product)

- Recalculate the resistors and capacitors using the pre-distorted values of  $\omega_p$  and  $Q_p$  ( $\omega_{p(pd)}$  and  $Q_{p(pd)}$ ) that will compensate for  $\tau_{oa}$ :

$$1/\omega_{p(pd)}^2 = 1/\omega_{p(nom)}^2 - K \tau_{oa} R_{12} C_5$$

$$= R_{12} R_3 C_4 C_5$$

$$1/(\omega_{p(pd)} Q_{p(pd)}) = 1/(\omega_{p(nom)} Q_{p(nom)})$$

$$= R_{12} C_5 (1 - K) + R_3 C_4 + R_{12} C_4$$

where  $\omega_{p(nom)}$  and  $Q_{p(nom)}$  are the nominal values of  $\omega_p$  and  $Q_p$

- Repeat step 2 until  $\omega_p \approx \omega_{p(nom)}$  and  $Q_p \approx Q_{p(nom)}$ , where:

$$1/\omega_p^2 = 1/\omega_{p(pd)}^2 + K \tau_{oa} R_{12} C_5$$

$$1/(\omega_p Q_p) = 1/(\omega_{p(pd)} Q_{p(pd)})$$

### Design Example

The circuit shown in Figure 2 is a 3rd-order Chebyshev lowpass filter. Section A is a buffered single pole section, and Section B is a lowpass biquad. Use a voltage source with low output impedance, such as the CLC111 buffer, for  $V_{in}$ .

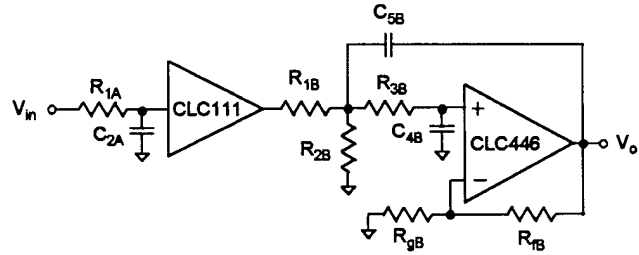


Figure 2: Lowpass Filter

The nominal filter specifications are:

$$f_c = 50\text{MHz} \quad (\text{passband edge frequency})$$

$$f_s = 100\text{MHz} \quad (\text{stopband edge frequency})$$

$$A_p = 0.5\text{dB} \quad (\text{maximum passband ripple})$$

$$A_s = 19\text{dB} \quad (\text{minimum stopband attenuation})$$

$$H_o = 0\text{dB} \quad (\text{DC voltage gain})$$

The 3rd-order Chebyshev filter meets our specifications (see References [1-4]). The resulting -3dB frequency is 58.4MHz. The pole frequencies and quality factors are:

Section	A	B
$\omega_p/2\pi$ [MHz]	53.45	31.30
$Q_p$ [ ]	1.706	—

Overall Design:

- Use the CLC111 for section A. This is a closed-loop buffer
  - $f_{3dB} = 800\text{MHz} > 10f_c = 500\text{MHz}$
  - $SR = 3500\text{V}/\mu\text{s}$ , while a 50MHz, 2V<sub>pp</sub> sinusoid requires more than 250V/ $\mu\text{s}$
  - $\tau_{oa} \approx 0.28\text{ns}$  at 50MHz
  - $C_{ni(111)} = 1.3\text{pF}$  (input capacitance)

- Use the CLC446 for section B. This is a current-feedback op amp
  - $f_{3dB} = 400\text{MHz} \approx 10f_c = 500\text{MHz}$
  - $SR = 2000\text{V}/\mu\text{s} > 250\text{V}/\mu\text{s}$  (see Item #1)
  - $\tau_{oa} \approx 0.56\text{ns}$  at 50MHz
  - $C_{ni(446)} = 1.0\text{pF}$  (non-inverting input capacitance)
- Use 1% resistors (chip metal film, 1206 SMD, 25ppm/°C)
- Use 1% capacitors (ceramic chip, 1206 SMD, 100ppm/°C)
- Use standard resistor and capacitor values
- See Reference [6] for the low-sensitivity design of this biquad.

#### Section A Pre-distortion:

We selected  $R_{1A}$  for noise, distortion and to properly isolate the CLC111's output and  $C_{2A}$ . The pole is then set by  $C_{2A}$ . The pre-distorted value of  $R_{1A}$ , that also compensates for  $C_{ni(111)}$ , is (see Example 1 in Appendix A):

$$R_{1A} = (1/\omega_p - \tau_{oa}) / (C_{2A} + C_{ni(111)})$$

The resulting components are in the table below:

- The Initial Value column shows the values before pre-distortion
- The Adjusted Value column shows the values after pre-distortion, and adjusting  $C_{2A}$  for  $C_{ni(111)}$
- The Standard Value column shows the nearest available standard 1% resistor and capacitor values

Component	Value		
	Initial	Adjusted	Standard
$R_{1A}$	108Ω	100Ω	100Ω
$C_{2A}$	47pF	47pF	47pF
$C_{ni(111)}$	—	1.3pF	1.3pF

#### Section B Pre-distortion:

- The design started with these values:
  - $\omega_{p(nom)} = 2\pi(53.45\text{MHz})$
  - $Q_{p(nom)} = 1.706$
  - $K_B = 1.50$
  - $\alpha_B = 0.667$
  - $C_{4B} + C_{ni(446)} = 4.7\text{pF}$
  - $C_{5B} = 47\text{pF}$
- Iteration 0 shows the initial design results. Iterations 1-3 pre-distort  $R_{12B}$  and  $R_{3B}$  to compensate for the CLC446's group delay:

Iteration	0	1	2	3
$\omega_{p(pd)} / 2\pi$ [MHz]	53.45	63.21	60.65	61.21
$Q_{p(pd)}$ [ ]	1.706	1.443	1.503	1.490
$R_{12B}$ [Ω]	64.00	50.17	53.32	52.63
$R_{3B}$ [Ω]	627.0	571.9	584.9	581.9

Iteration	0	1	2	3
$K\tau_{oa}R_{12B}C_{5B}$ [ns <sup>2</sup> ]	2.527	1.981	2.105	2.078
$\omega_p / 2\pi$ [MHz]	47.15	55.18	53.08	53.53
$Q_p$ [ ]	1.934	1.653	1.718	1.703

- The resulting components are:

Component	Value		
	Initial	Adjusted	Standard
$R_{1B}$	96.0Ω	78.9Ω	78.7Ω
$R_{2B}$	192Ω	158Ω	158Ω
$R_{3B}$	627Ω	582Ω	576Ω
$C_{4B}$	4.7pF	3.7pF	3.6pF
$C_{ni(446)}$	—	1.0pF	1.0pF
$C_{5B}$	47pF	47pF	47pF
$R_{fB}$	348Ω	348Ω	348Ω
$R_{gB}$	696Ω	696Ω	698Ω

Figures 3 and 4 show simulated gains for the following conditions:

- Ideal (Initial Values,  $\tau_{oa} = 0$ )
- Without Pre-distortion (Initial Values,  $\tau_{oa} \neq 0$ )
- With Pre-distortion (Standard Values,  $\tau_{oa} \neq 0$ )

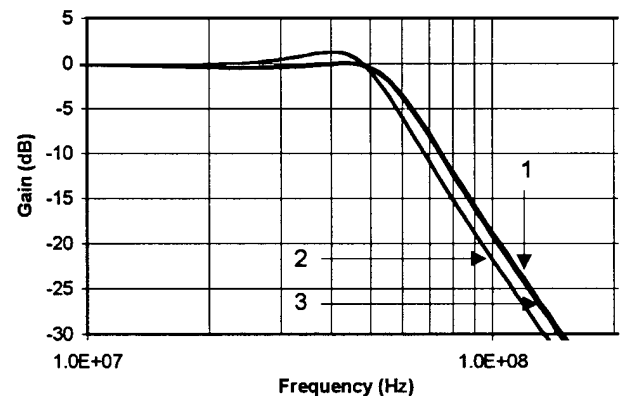


Figure 3: Simulated Filter Magnitude Response

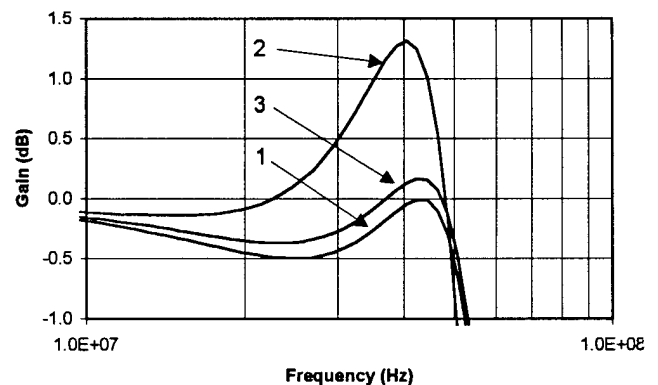


Figure 4: Simulated Filter Magnitude Response in the Passband

## SPICE Models

SPICE models are available for most of Comlinear's amplifiers. These models support nominal DC, AC, AC noise and transient simulations at room temperature.

We recommend simulating with Comlinear's SPICE models to:

- Predict the op amp's influence on filter response
  - Support quicker design cycles
- Include board and component parasitics to obtain a more accurate prediction of the filter's response, and to further improve your design.

To verify your simulations, we recommend breadboarding your circuit.

## Summary

This App Note demonstrates a component pre-distortion method that:

- Works for popular Sallen-Key filter sections
- Is quick and simple to use
- Shows the op amp's effect on the filter response
- Gives reasonable op amp selection criteria

Appendix A and the *Design Example* section contain illustrations of this method.

## Appendix A- Transfer Function Examples

Example 1:

Single pole section, K in the numerator:

$$\frac{V_o}{V_{in}} \approx \frac{K}{1 + (1/\omega_p)s}$$

$$1/\omega_p = \tau_1$$

where  $\tau_1$  is a time constant set by resistors and capacitors.

To include the op amp's group delay, substitute for K and simplify:

$$\frac{V_o}{V_{in}} \approx \frac{1}{1 + (\tau_1)s} \cdot \frac{K}{1 + \tau_{oa}s}$$

$$\approx \frac{K}{1 + (1/\omega_p)s} \quad ; \quad \omega, \omega_p \ll 1/\tau_{oa}$$

$$1/\omega_p = \tau_1 + \tau_{oa}$$

Notice that:

- There are no new powers of s in the transfer function
- Changing the resistor and capacitor values can compensate for  $\tau_{oa}$
- The approximation is reasonably accurate when  $f \ll f_{3dB}$

To pre-distort this filter section, recalculate the resistors and capacitors using the equation:

$$\tau_1 = 1/\omega_p - \tau_{oa}$$

Example 2:

Single pole allpass section, K times the numerator:

$$\frac{V_o}{V_{in}} \approx \frac{1 - (1/\omega_z)s}{1 + (1/\omega_p)s} \cdot K$$

$$1/\omega_p = \tau_1$$

$$1/\omega_z = \tau_2$$

where  $\tau_1$  and  $\tau_2$  are time constants set by resistors and capacitors. This section operates as an allpass filter when:

$$\tau_1 = \tau_2$$

To include the op amp's group delay, substitute for K and simplify. Since this is an allpass transfer function, the approximation to K does not change gain at  $\omega = \omega_p$ :

$$\frac{V_o}{V_{in}} \approx \frac{1 - (\tau_2)s}{1 + (\tau_1)s} \cdot \frac{1 - (\tau_{oa}/2)s}{1 + (\tau_{oa}/2)s} \cdot K$$

$$\approx \frac{1 - (1/\omega_z)s}{1 + (1/\omega_p)s} \cdot K$$

$$\omega, \omega_p, \omega_z \ll 1/\tau_{oa}$$

$$1/\omega_z = \tau_2 + \tau_{oa}/2$$

$$1/\omega_p = \tau_1 + \tau_{oa}/2$$

Notice that:

- There are no new powers of s in the transfer function
- The gain at  $\omega_p$  does not change (this is an allpass section)
- Changing the resistor and capacitor values can compensate for  $\tau_{oa}$
- The approximation is reasonably accurate when  $f \ll f_{3dB}$

To pre-distort this filter, recalculate the resistors and capacitors using the equations:

$$\tau_2 = 1/\omega_z - \tau_{oa}/2$$

$$\tau_1 = 1/\omega_p - \tau_{oa}/2$$

Example 3:

Biquad section, s term in the denominator that includes K:

$$\frac{V_o}{V_{in}} \approx \frac{1}{1 + (1/(\omega_p Q_p))s + (1/\omega_p^2)s^2}$$

$$1/(\omega_p Q_p) = \tau_1 + K\tau_2$$

$$1/\omega_p^2 = \tau_3^2$$

where  $\tau_1$ ,  $\tau_2$  and  $\tau_3$  are time constants set by resistors and capacitors.

To include the op amp's group delay, substitute for K and simplify:

$$\frac{V_o}{V_{in}} \approx \frac{1}{1 + (\tau_1 + K(1 - \tau_{oa}s) \cdot \tau_2)s + (\tau_3^2)s^2}$$

$$\approx \frac{1}{1 + (1/(\omega_p Q_p))s + (1/\omega_p^2)s^2}$$

$$\omega, \omega_p \ll 1/\tau_{oa}$$

$$1/(\omega_p Q_p) = \tau_1 + K\tau_2$$

$$1/\omega_p^2 = \tau_3^2 - K\tau_2\tau_{oa}$$

Notice that:

- There are no new powers of s in the transfer function
- Changing the resistor and capacitor values can compensate for  $\tau_{oa}$
- The approximation is reasonably accurate when  $f \ll f_{3dB}$

To pre-distort this filter:

1. Design the filter assuming K constant ( $\tau_{oa} = 0$ ).
2. Recalculate the resistors and capacitors using the pre-distorted values of  $\omega_p$  and  $Q_p$  ( $\omega_{p(pd)}$  and  $Q_{p(pd)}$ ) that will compensate for  $\tau_{oa}$ :

$$1/\omega_{p(pd)}^2 = 1/\omega_{p(nom)}^2 + K\tau_2\tau_{oa}$$

$$= \tau_3^2$$

$$1/(\omega_{p(pd)} Q_{p(pd)}) = 1/(\omega_{p(nom)} Q_{p(nom)})$$

$$= \tau_1 + K\tau_2$$

where  $\omega_{p(nom)}$  and  $Q_{p(nom)}$  are the nominal values of  $\omega_p$  and  $Q_p$

3. Repeat step 2 until  $\omega_p \approx \omega_{p(nom)}$  and  $Q_p \approx Q_{p(nom)}$ , where:

$$1/\omega_p^2 = 1/\omega_{p(pd)}^2 - K\tau_2\tau_{oa}$$

$$1/(\omega_p Q_p) = 1/(\omega_{p(pd)} Q_{p(pd)})$$

Example 4:

Biquad section,  $s^2$  term in the denominator multiplied by K:

$$\frac{V_o}{V_{in}} \approx \frac{1}{1 + (1/(\omega_p Q_p))s + (1/\omega_p^2)s^2}$$

$$1/(\omega_p Q_p) = \tau_1$$

$$1/\omega_p^2 = K\tau_2^2$$

where  $\tau_1$  and  $\tau_2$  are time constants set by resistors and capacitors.

To include the op amp's group delay, substitute for K and simplify:

$$\frac{V_o}{V_{in}} \approx \frac{1}{1 + (\tau_1)s + (\tau_2^2 \cdot K/(1 + \tau_{oa}s))s^2}$$

$$\approx \frac{e^{\tau_{oa}s}}{1 + (1/(\omega_p Q_p))s + (1/\omega_p^2)s^2}$$

$$\omega, \omega_p \ll 1/\tau_{oa}$$

$$1/(\omega_p Q_p) = \tau_1 + \tau_{oa}$$

$$1/\omega_p^2 = K\tau_2^2 + \tau_1\tau_{oa}$$

Notice that:

- The  $(1 + \tau_{oa}s)$  factor in the numerator was converted to the exponential form, which represents a constant group delay
- There are no new powers of s in the transfer function
- Changing the resistor and capacitor values can compensate for  $\tau_{oa}$
- The approximation is reasonably accurate when  $f \ll f_{3dB}$

To pre-distort this filter:

1. Design the filter assuming K constant ( $\tau_{oa} = 0$ ).
2. Recalculate the resistors and capacitors using the pre-distorted values of  $\omega_p$  and  $Q_p$  ( $\omega_{p(pd)}$  and  $Q_{p(pd)}$ ) that will compensate for  $\tau_{oa}$ :

$$1/\omega_{p(pd)}^2 = 1/\omega_{p(nom)}^2 - \tau_1\tau_{oa}$$

$$= K\tau_2^2$$

$$1/(\omega_{p(pd)} Q_{p(pd)}) = 1/(\omega_{p(nom)} Q_{p(nom)}) - \tau_{oa}$$

$$= \tau_1$$

where  $\omega_{p(nom)}$  and  $Q_{p(nom)}$  are the nominal values of  $\omega_p$  and  $Q_p$

3. Repeat step 2 until  $\omega_p \approx \omega_{p(nom)}$  and  $Q_p \approx Q_{p(nom)}$ , where:

$$1/\omega_p^2 = 1/\omega_{p(pd)}^2 + \tau_1\tau_{oa}$$

$$1/(\omega_p Q_p) = 1/(\omega_{p(pd)} Q_{p(pd)}) + \tau_{oa}$$

## Appendix B- Electrical Loop Delay

$\tau_{eld}$  can be calculated as:

$$\tau_{eld} = x \cdot \sqrt{\epsilon_r \mu_r} / c + \tau_{oa}$$

where:

- x is the distance around the filter feedback loop, excluding the op amp
- $\epsilon_r$  is the equivalent relative permittivity of the PCB trace
- $\mu_r$  is the equivalent relative permeability of the PCB trace
- c is the speed of light in free space ( $3.00 \times 10^8$  m/s)
- $\tau_{oa}$  is the op amp group delay at  $f_c$

For a typical printed circuit board,  $\sqrt{\epsilon_r \mu_r} \approx 2.0$ . This gives:

$$\tau_{eld} \approx x \cdot (0.067 \text{ ns / cm}) + \tau_{oa}$$

where x is in centimeters, and  $\tau_{oa}$  is in nanoseconds.

## Appendix C- Bibliography

- [1] R. Schaumann, M. Ghausi and K. Laker, *Design of Analog Filters: Passive, Active RC, and Switched Capacitor*. New Jersey: Prentice Hall, 1990.
- [2] A. Zverev, *Handbook of FILTER SYNTHESIS*. John Wiley & Sons, 1967.
- [3] A. Williams and F. Taylor, *Electronic Filter Design Handbook*. McGraw Hill, 1995.
- [4] S. Natarajan, *Theory and Design of Linear Active Networks*. Macmillan, 1987.
- [5] M. Steffes, 'Simplified Component Value Pre-distortion for High Speed Active Filters,' Comlinear Application Note, OA-21, Rev. A, March 1993 (no longer available).
- [6] K. Blake, 'Low-Sensitivity, Lowpass Filter Design,' Comlinear Application Note, OA-27, July 1996.

**This page intentionally left blank.**

---

## Customer Design Applications Support

National Semiconductor is committed to design excellence. For sales, literature and technical support, call the National Semiconductor Customer Response Group at **1-800-272-9959** or fax **1-800-737-7018**.

### Life Support Policy

National's products are not authorized for use as critical components in life support devices or systems without the express written approval of the president of National Semiconductor Corporation. As used herein:

1. Life support devices or systems are devices or systems which, a) are intended for surgical implant into the body, or b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



#### National Semiconductor Corporation

1111 West Bardin Road  
Arlington, TX 76017  
Tel: 1(800) 272-9959  
Fax: 1(800) 737-7018

#### National Semiconductor Europe

Fax: (+49) 0-180-530 85 86  
E-mail: europe.support@nsc.com  
Deutsch Tel: (+49) 0-180-530 85 85  
English Tel: (+49) 0-180-532 78 32  
Francais Tel: (+49) 0-180-532 93 58  
Italiano Tel: (+49) 0-180-534 16 80

#### National Semiconductor Hong Kong Ltd.

13th Floor, Straight Block  
Ocean Centre, 5 Canton Road  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

#### National Semiconductor Japan Ltd.

Tel: 81-043-299-2309  
Fax: 81-043-299-2408

---

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.