

### Introduction

This Application Note covers the design of a Sallen-Key bandpass biquad. It gives a design with low component and op amp sensitivities. Then it gives a filter tuning method to compensate for parasitics. A design example illustrates these methods. These biquads are also called KRC or VCVS [voltage-controlled, voltage-source].

Changes in component values over process, environment and time affect the performance of a filter. To achieve a greater production yield, the filter needs to be insensitive to these changes. This Application Note presents a design algorithm that results in low sensitivity to component variation. See [6] for information on evaluating the sensitivity performance of your filter.

To achieve the best production yield, the nominal filter design must also compensate for component and board parasitics. This App Note gives a method to empirically tune your filter. See [5, 7] for the background theory.

### Filter Tuning Overview

This section shows a simple tuning method that compensates for the parasitic elements in your filter.

To minimize the impact of parasitics:

- Keep signal paths as short as possible
- Minimize the length of all feedback loops
- Use components with small parasitics
- Use good PCB layout techniques
- Use an op amp with adequate bandwidth ( $f_{3dB}$ ) and slew rate (SR):

$$f_{3dB} \geq 10f_H$$

$$SR > 5f_H V_{peak}$$

where  $f_H$  is the highest frequency in the passband of the filter, and  $V_{peak}$  is the largest peak voltage. Make sure the op amp is stable at the chosen gain.

To compensate for the parasitic elements:

1. Start with a low sensitivity, low parasitic design
2. Calculate the sensitivities of the filter response parameters to the resistors and capacitors [6]
3. Measure the filter's response. The important parameters to extract are:
  - Maximum passband gain ( $H_p$ )
  - Pole frequency ( $\omega_p$ )
  - Pole quality ( $Q_p$ )


The *Design Example* section gives a simple extraction method. Use accurate component values for the prototype filter so that the nominal design

point will be near the center of the possible component values

4. Use the information in steps 2 and 3 to adjust the resistor and capacitor values:
  - Set up the linear equations relating the relative change in filter response parameters ( $\Delta H_p/H_p$ ,  $\Delta \omega_p/\omega_p$  and  $\Delta Q_p/Q_p$ ) to the relative change in the components to be adjusted
  - The number of components to change is the same as the number of filter response parameters
  - The coefficients of these linear equations are the component sensitivities [6]
5. Repeat steps 3 and 4 until the nominal response is close enough to the desired response.

### KRC Bandpass Biquad Design

The biquad shown in Figure 1 is a Sallen-Key bandpass biquad.  $V_{in}$  needs to be a voltage source with low output impedance.

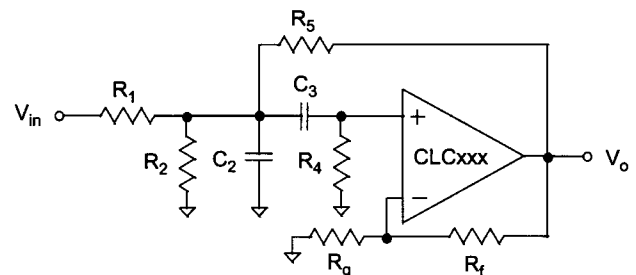

**Figure 1: Bandpass Biquad**

$R_2$  attenuates the input signal for low gains.  $V_{in}$ ,  $R_1$  and  $R_2$  can be replaced with their Thévenin equivalent voltage ( $\alpha V_{in}$ ) and impedance ( $R_{12}$ ):

$$\alpha = R_2 / (R_1 + R_2)$$

$$R_{12} = R_1 || R_2$$

The transfer function is:

$$\frac{V_o}{V_{in}} \approx \frac{H_p (\omega_p / Q_p) s}{s^2 + (\omega_p / Q_p) s + (\omega_p^2)} \quad , \quad s = j\omega$$

where:

$$\omega_p / Q_p = \left( \frac{1}{R_{12}} + \frac{1}{R_4} - \frac{K-1}{R_5} \right) \cdot \frac{1}{C_2} + \frac{1}{R_4 C_3}$$

$$\omega_p^2 = \frac{1}{R_4 C_2 C_3} \left( \frac{1}{R_{12}} + \frac{1}{R_5} \right)$$

$$K = 1 + R_f / R_g$$

$$H_p = \frac{\alpha K}{R_{12} C_2} \cdot \frac{Q_p}{\omega_p}$$

To achieve low sensitivities, use this design algorithm:

1. Use this biquad when:

$$0.5 \leq Q_p < 5.0$$

Steps 2 and 3 assume this condition to be true.

2. Partition the gain:

- Use a low noise amplifier before this biquad if you need a large gain
- Initialize the peak passband gain in 1 of 3 ways:
  - For the best sensitivity performance, use:
 
$$H_p \approx 1.0$$
  - For reasonable sensitivity performance and reduced component spreads, use:
 
$$H_p \approx \max\{1.0, Q_p\}$$
  - For dynamic range performance, scale  $H_p$  as needed. Limit the peak gain to:
 
$$H_p < 10.0$$

3. Set the input attenuation:

$$\alpha = \min\{1.0, H_p\}$$

4. Initialize one of the resistor spreads ( $r^2 = R_{12}/R_4$ ) and the op amp gain (K):

$$A_1 = 0.0381 Q_p^{1.51} (H_p / \alpha)^{-1.27}$$

$$A_2 = 0.00206 Q_p^{-1.92} (H_p / \alpha)^{1.39}$$

$$r^2 \approx \max\{0.1, A_1 + A_2\}$$

$$B_1 = 0.456 (\max\{1, Q_p\})^{-1.22} (H_p / \alpha)^{1.22}$$

$$B_2 = 0.0260 (\max\{1, Q_p\})^{1.76} (H_p / \alpha)^{-1.51}$$

$$K \approx 1.0 + \max\{0.1, B_1 + B_2\}$$

5. Select an op amp with adequate bandwidth ( $f_{3dB}$ ) and slew rate (SR):

$$f_{3dB} \geq 10f_H$$

$$SR > 5f_H V_{peak}$$

where  $f_H$  is the highest frequency in the passband, and  $V_{peak}$  is the largest peak voltage. Make sure the op amp is stable at a gain of  $A_v = K$ .

6. For current-feedback op amps, use the recommended value of  $R_f$  for a gain of  $A_v = K$ . For voltage-feedback op amps, select  $R_f$  for noise and distortion performance. Then set  $R_g$  for the correct gain:

$$R_g = R_f / (K - 1)$$

7. Calculate the capacitor spread ( $c^2 = C_2/C_3$ ), and the other resistor spread ( $\beta^2 = R_{12}/R_5$ ):

$$A_0 = (K - 1) (\alpha K Q_p / H_p)^2$$

$$A_1 = r^2 + K(1 - \alpha/H_p)$$

$$c^2 = \frac{1}{r^2} \cdot \frac{2A_0}{A_1 + \sqrt{A_1^2 + 4A_0}}$$

$$\beta^2 = \left( \frac{\alpha K Q_p}{H_p} \right)^2 \left( \frac{1}{c^2 r^2} \right) - 1$$

8. Initialize the resistance level ( $R = \sqrt{R_{12} R_4}$ ). Increasing R will:

- Increase the output noise
- Improve the distortion performance
- Improve the isolation between the op amp outputs and  $C_2$  and  $C_3$
- Make the parasitic capacitances a larger fraction of  $C_2$  and  $C_3$

9. Calculate the capacitance level ( $C = \sqrt{C_2 C_3}$ ):

$$C = \sqrt{1 + \beta^2} / (\omega_p R)$$

10. Calculate the resistors and capacitors:

$$R_{12} = rR$$

$$R_1 = R_{12} / \alpha$$

$$R_2 = R_{12} / (1 - \alpha)$$

$$R_4 = R/r$$

$$R_5 = R_{12} / \beta^2$$

$$C_2 = cC$$

$$C_3 = C/c$$

11. Set the resistors and capacitors to the nearest standard values.

The component sensitivity formulas are in the table below. The sensitivities to  $\alpha_i = K$  are a measure of this biquad's sensitivity to the op amp group delay [5]. To evaluate this biquad's sensitivity performance, see [6]. To manually pre-distort this filter, and compensate for parasitic capacitances, see [5] and [7].

$\alpha_i$	$S_{\alpha_i}^{H_p}$	$S_{\alpha_i}^{\omega_p}$	$S_{\alpha_i}^{Q_p}$
$R_1$	$\frac{H_p}{K} - 1$	$\frac{-\alpha}{2(1+\beta^2)}$	$S_{R_1}^{H_p} + S_{R_1}^{\omega_p} + 1$
$R_2$	$\frac{(1-\alpha)H_p}{\alpha K}$	$\frac{-(1-\alpha)}{2(1+\beta^2)}$	$S_{R_2}^{H_p} + S_{R_2}^{\omega_p}$
$R_4$	$\frac{H_p(1+c^2)r^2}{\alpha K}$	$-\frac{1}{2}$	$S_{R_4}^{H_p} + S_{R_4}^{\omega_p}$
$R_5$	$\frac{-H_p(K-1)\beta^2}{\alpha K}$	$\frac{-\beta^2}{2(1+\beta^2)}$	$S_{R_5}^{H_p} + S_{R_5}^{\omega_p}$
$C_2$	$\frac{-H_p c^2 r^2}{\alpha K}$	$-\frac{1}{2}$	$S_{C_2}^{H_p} + S_{C_2}^{\omega_p} + 1$

$C_3$	$-S_{C_2}^{H_p}$	$-\frac{1}{2}$	$-S_{C_2}^{Q_p}$
$R_f$	$\left(\frac{H_p \beta^2}{\alpha} + 1\right) \cdot \frac{K-1}{K}$	0	$\frac{H_p}{S_{R_f}^{\omega_p}} + S_{R_f}^{\omega_p} - \frac{K-1}{K}$
$R_g$	$-S_{R_f}^{H_p}$	0	$-S_{R_f}^{Q_p}$
$K$	1	0	$\frac{H_p \beta^2}{\alpha}$

### KRC Bandpass Biquad Tuning Method

To tune this filter, use this algorithm:

1. Start with a low-sensitivity design.
2. Calculate the sensitivities of  $H_p$ ,  $\omega_p$  and  $Q_p$  to the components.
3. Set up the linear equations:
  - Choose the 3 components  $\alpha_i$  that will be changed to adjust  $H_p$ ,  $\omega_p$  and  $Q_p$
  - Create this sensitivity matrix using the formulas (see Appendix A for a simple method that uses measurement or simulation results):

$$\mathbf{M}_3 = \begin{bmatrix} S_{\alpha_1}^{H_p} & S_{\alpha_2}^{H_p} & S_{\alpha_3}^{H_p} \\ S_{\alpha_1}^{\omega_p} & S_{\alpha_2}^{\omega_p} & S_{\alpha_3}^{\omega_p} \\ S_{\alpha_1}^{Q_p} & S_{\alpha_2}^{Q_p} & S_{\alpha_3}^{Q_p} \end{bmatrix}$$

4. Measure the filter response, and then extract  $H_p$ ,  $\omega_p$  and  $Q_p$ :
  - Find the maximum gain magnitude:

$$H_p = \max\{|H(j\omega)|\}$$

- Find the -3dB corner frequencies  $f_1$  and  $f_2$ , where  $f_2 > f_1$
- Calculate  $\omega_p$  and  $Q_p$ :

$$\omega_p = 2\pi\sqrt{f_1 f_2}$$

$$Q_p = \sqrt{f_1 f_2} / (f_2 - f_1)$$

5. Calculate the needed changes in  $H_p$ ,  $\omega_p$  and  $Q_p$  (X):

$$\Delta X/X = 1 - X_{\text{meas}}/X_{\text{nom}}$$

where  $X_{\text{nom}}$  and  $X_{\text{meas}}$  are the nominal and measured values of X. Limit the relative changes in X:

$$\Delta X/X \leftarrow \max\{-0.5, \min\{1.0, \Delta X/X\}\}$$

6. Calculate the needed component values:

- Estimate the relative changes in  $\alpha_i$ , and then limit them:

$$\begin{bmatrix} \Delta\alpha_1/\alpha_1 \\ \Delta\alpha_2/\alpha_2 \\ \Delta\alpha_3/\alpha_3 \end{bmatrix} = \mathbf{M}_3^{-1} \cdot \begin{bmatrix} \Delta H_p/H_p \\ \Delta\omega_p/\omega_p \\ \Delta Q_p/Q_p \end{bmatrix}$$

$$\frac{\Delta\alpha_i}{\alpha_i} \leftarrow \max\left\{-0.5, \min\left\{1.0, \frac{\Delta\alpha_i}{\alpha_i}\right\}\right\}$$

- Calculate the new  $\alpha_i$ :

$$\alpha_i \leftarrow \alpha_i(1 + \Delta\alpha_i/\alpha_i)$$

- Change the filter components to these new values; use accurate component values when building the prototype filter so that the nominal design point will be near the center of the possible component values

7. Repeat steps 4-6 until the nominal response is close enough to the desired response.

### Design Example

The circuit shown in Figure 2 is a 4th-order bandpass filter. This filter cascades two bandpass biquads: sections A and B. Use a voltage source with low output impedance, such as the CLC111 buffer, for  $V_{in}$ .

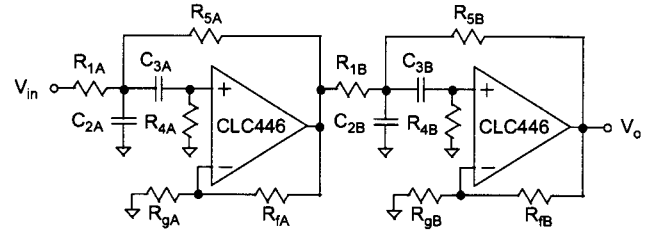


Figure 2: Bandpass Filter

The nominal filter specifications are:

- $f_{sl} = 15\text{MHz}$  (lower stopband edge frequency)
- $f_{cl} = 40\text{MHz}$  (lower passband edge frequency)
- $f_{cu} = 60\text{MHz}$  (upper passband edge frequency)
- $f_{su} = 135\text{MHz}$  (upper stopband edge frequency)
- $A_p = 3.0\text{dB}$  (maximum passband ripple)
- $A_s = 30\text{dB}$  (minimum stopband attenuation)
- $H_p = 0\text{dB}$  (passband voltage gain)

The 2nd-order Butterworth lowpass prototype filter meets these specifications [1-4]. The  $H_p$  values shown below give a maximum gain of 1.00 from  $V_{in}$  to each biquad output. The transformed filter is:

Section	A	B
$\omega_p/2\pi$ [MHz]	42.36	56.65
$Q_p$ [ ]	3.501	3.501
$H_p$ [V/V]	1.000	2.043

Overall Design:

1. Restrict the resistor and capacitor ratios to:
 
$$0.1 \leq c^2, r^2, \beta^2 \leq 10$$
2. Use 1% resistors (chip metal film, 1206 SMD)
3. Use 5% capacitors (ceramic chip, 1206 SMD)
4. Use standard resistor and capacitor values
5. Use the same  $H_p$  in both sections to simplify the design. Also set the overall gain to 1.00:

$$H_p = \sqrt{(1.000)(2.043)} = 1.429$$

Section A Design:

1.  $Q_p$  (3.501) meets the required limits
2.  $H_p$  (1.429) is between the first two criteria in step 2 of the design algorithm; the sensitivity performance and component spreads should be reasonable

3. Initialize  $\alpha$  to 1.00;  $R_{2A}$  is an open circuit
4. Initialize  $r^2$  &  $K$ :  
 $A_1 = 0.1606$      $A_2 = 0.0003$   
 $r^2 = 0.1609$   
 $B_1 = 0.1528$      $B_2 = 0.1376$   
 $K = 1.290$
5. The CLC446 is a current-feedback op amp:
  - $f_{3dB} = 400\text{MHz} < 10f_H = 600\text{MHz}$  ( $f_H = f_{cu}$ ); the op amp strongly affects the filter
  - $SR = 2000\text{V}/\mu\text{s}$ , while a  $60\text{MHz}$ ,  $2\text{V}_{pp}$  sinusoid requires more than  $300\text{V}/\mu\text{s}$
6. Set  $R_{fA}$  to the CLC446's recommended  $R_f$  at  $A_v = +1.290$ , then calculate  $R_{gA}$ :  
 $R_{fA} = 392\Omega$   
 $R_{gA} = R_{fA} / (K - 1) = 1352\Omega$
7. Calculate  $c^2$  and  $\beta^2$ :  
 $A_0 = 2.897$      $A_1 = 0.5482$   
 $c^2 = 9.011$   
 $\beta^2 = 5.889$
8. Initialize  $R = 300\Omega$
9. Calculate  $C$ :  

$$C = \frac{\sqrt{1 + 5.889}}{2\pi(42.36\text{MHz}) \cdot (300\Omega)} = 32.87\text{pF}$$
10. The initial values are in the table below

$\alpha_i$	$S_{\alpha_i}^{H_p}$	$S_{\alpha_i}^{\omega_p}$	$S_{\alpha_i}^{Q_p}$
$R_1$	0.11	-0.07	1.04
$R_4$	1.78	-0.50	1.28
$R_5$	-1.89	-0.43	-2.32
$C_2$	-1.61	-0.50	-1.11
$C_3$	1.61	-0.50	1.11
$R_f$	2.12	0.00	1.89
$R_g$	-2.12	0.00	-1.89
$K$	1.00	0.00	8.42

2. To tune the filter, change  $R_1$ ,  $R_4$  and  $R_g$ :

$$\begin{bmatrix} \Delta R_1/R_1 \\ \Delta R_4/R_4 \\ \Delta R_g/R_g \end{bmatrix} = \mathbf{M}_3^{-1} \cdot \begin{bmatrix} \Delta H_p/H_p \\ \Delta \omega_p/\omega_p \\ \Delta Q_p/Q_p \end{bmatrix}$$

where:

$$\mathbf{M}_3 = \begin{bmatrix} 0.11 & 1.78 & -2.12 \\ -0.07 & -0.50 & 0.00 \\ 1.04 & 1.28 & -1.89 \end{bmatrix}$$

$$\mathbf{M}_3^{-1} = \begin{bmatrix} -0.91 & -0.62 & 1.02 \\ 0.13 & -1.91 & -0.14 \\ -0.41 & -1.64 & -0.07 \end{bmatrix}$$

3. The results of tuning section A are:

Iteration #	1	2	3	4
$R_1$ [ $\Omega$ ]	120	98.7	89.3	90.8
$R_4$ [ $\Omega$ ]	748	496	488	492
$R_g$ [ $\Omega$ ]	1352	676	708	700
$H_p$ [V/V]	0.736	1.625	1.373	1.433
$\omega_p/2\pi$ [MHz]	34.62	41.76	42.57	42.32
$Q_p$ [ ]	2.212	4.226	3.335	3.504
$\Delta H_p/H_p$ [%]	48.5	-13.7	3.92	-0.28
$\Delta \omega_p/\omega_p$ [%]	18.3	1.42	-0.50	0.09
$\Delta Q_p/Q_p$ [%]	36.8	-20.7	4.74	-0.09
$\Delta R_1/R_1$ [%]	-17.9	-9.52	1.58	—
$\Delta R_4/R_4$ [%]	-33.8	-1.59	0.79	—
$\Delta R_g/R_g$ [%]	-50.0	4.75	-1.13	—

4. The results of tuning section B are:

Iteration #	1	2	3	4
$R_1$ [ $\Omega$ ]	90.0	66.5	62.9	63.3
$R_4$ [ $\Omega$ ]	559	363	357	360
$R_g$ [ $\Omega$ ]	1352	740	784	779
$H_p$ [V/V]	0.993	1.663	1.384	1.428
$\omega_p/2\pi$ [MHz]	45.66	55.94	56.95	56.62
$Q_p$ [ ]	3.029	4.174	3.391	3.496
$\Delta H_p/H_p$ [%]	30.5	-16.4	3.15	0.07
$\Delta \omega_p/\omega_p$ [%]	19.4	1.25	-0.53	0.05
$\Delta Q_p/Q_p$ [%]	13.5	-19.2	3.14	0.14
$\Delta R_1/R_1$ [%]	-26.1	-5.48	0.67	—
$\Delta R_4/R_4$ [%]	-35.0	-1.83	0.98	—
$\Delta R_g/R_g$ [%]	-45.3	6.00	-0.64	—

#### Section B Design:

$H_p$  and  $Q_p$  are the same as in section A, but  $\omega_p$  is different. To change the pole frequency, scale the resistors  $R_{1B}$ ,  $R_{4B}$  and  $R_{5B}$ :

$$R_{xB} \leftarrow R_{xA} \cdot (\omega_{pA} / \omega_{pB}) = R_{xA} \cdot 0.7477$$

The initial component values are:

Component	Initial Value	
	Section A	Section B
$R_1$ [ $\Omega$ ]	120	90.0
$R_4$ [ $\Omega$ ]	748	559
$R_5$ [ $\Omega$ ]	20.4	15.3
$C_2$ [pF]	98.7	98.7
$C_3$ [pF]	11.0	11.0
$R_f$ [ $\Omega$ ]	392	392
$R_g$ [ $\Omega$ ]	1352	1352

#### Filter Tuning:


This section uses simulated results; different layout and component parasitics will change the tuning results. Simulations used the following parasitics:

- 0.2pF across all resistors
- 1.0pF to ground at CLC446 non-inverting inputs
- A group delay of 0.56ns for the CLC446 at 50MHz, using a good simulation model


1. The sensitivities for sections A and B are equal since they are not functions of  $\omega_p$ . They are:

Figures 3 and 4 show the simulated filter gain. The curve numbers are:

1. The ideal gain
2. The gain for the initial design (Iteration 1)
3. The gain for the tuned filter (Iteration 4)

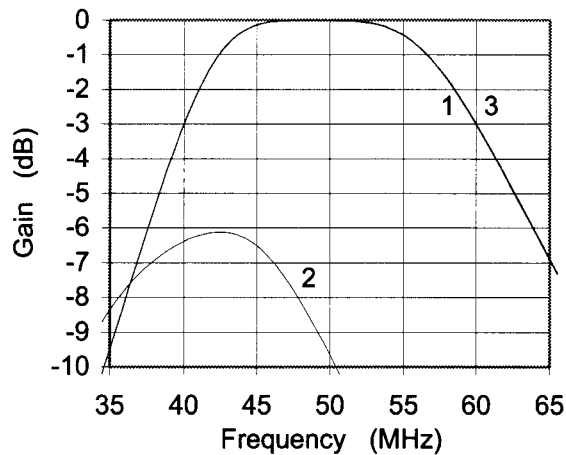

**Figure 3: Simulated Filter Magnitude Response**

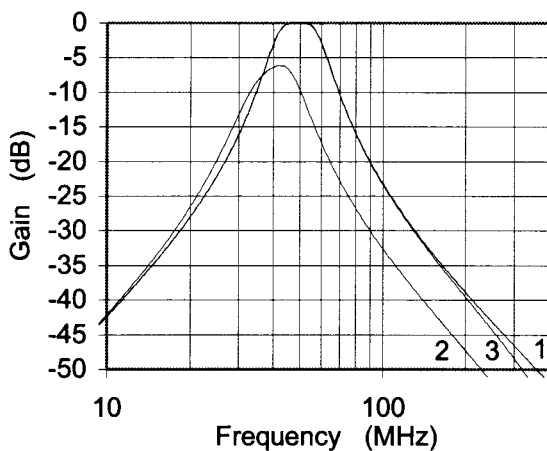

**Figure 4: Simulated Filter Magnitude Response**

The final standard component values are:

Component		Standard Tuned Value	
		Section A	Section B
R <sub>1</sub>	[Ω]	90.9	63.4
R <sub>4</sub>	[Ω]	487	357
R <sub>5</sub>	[Ω]	20.5	15.4
C <sub>2</sub>	[pF]	100	100
C <sub>3</sub>	[pF]	11	11
R <sub>f</sub>	[Ω]	392	392
R <sub>g</sub>	[Ω]	698	787

## SPICE Models

SPICE models are available for most of Comlinear's amplifiers. These models support nominal DC, AC, AC noise and transient simulations at room temperature.

We recommend simulating with Comlinear's SPICE models to:

- Predict the op amp's influence on filter response
- Support quicker design cycles

Include board and component parasitic models to obtain a more accurate prediction of the filter's response.

To verify your simulations, we recommend bread-boarding your circuit.

## Summary

This App Note contains an easy to use design algorithm for a low sensitivity, Sallen-Key bandpass biquad. Designing for low H<sub>p</sub>, ω<sub>p</sub> and Q<sub>p</sub> sensitivities gives:

- Reduced filter variation over process, temperature and time
- Higher manufacturing yield
- Lower component cost

A low sensitivity design is not enough to produce high manufacturing yields. This Application Note shows how to tune the filter to compensate for parasitics; no assumptions about the parasitics are necessary. The components must also have low tolerance, small parasitics and low temperature coefficients.

## Appendix A - Estimating the Sensitivity Matrix

For filters where the sensitivity formulas are not readily available, this appendix gives a simple method to estimate the entries in the sensitivity matrix.

To estimate the sensitivity matrix entries using measurement or simulation results, use this algorithm:

1. Choose the 3 components α<sub>i</sub> that will be changed to adjust H<sub>p</sub>, ω<sub>p</sub> and Q<sub>p</sub> (X)
2. Calculate the sensitivities of H<sub>p</sub>, ω<sub>p</sub> and Q<sub>p</sub> to the chosen components:

- Extract the parameters H<sub>p</sub>, ω<sub>p</sub> and Q<sub>p</sub> at the nominal values of α<sub>i</sub>
- Extract the parameters H<sub>p</sub>, ω<sub>p</sub> and Q<sub>p</sub> when only one α<sub>i</sub> is different from its nominal value; this results in 3 sets of 3 modified performance parameters
- Estimate the sensitivities (X is H<sub>p</sub>, ω<sub>p</sub> or Q<sub>p</sub>):

$$S_{\alpha_1}^X \approx \frac{\Delta X}{X} \cdot \frac{\alpha_1}{\Delta \alpha_1} \bigg|_{\Delta \alpha_2 = \Delta \alpha_3 = 0}$$

$$S_{\alpha_2}^X \approx \frac{\Delta X}{X} \cdot \frac{\alpha_2}{\Delta \alpha_2} \bigg|_{\Delta \alpha_1 = \Delta \alpha_3 = 0}$$

$$S_{\alpha_3}^X \approx \frac{\Delta X}{X} \cdot \frac{\alpha_3}{\Delta \alpha_3} \bigg|_{\Delta \alpha_1 = \Delta \alpha_2 = 0}$$

3. Form the sensitivity matrix:

$$\mathbf{M}_3 = \begin{bmatrix} S_{\alpha_1}^{H_p} & S_{\alpha_2}^{H_p} & S_{\alpha_3}^{H_p} \\ S_{\alpha_1}^{\omega_p} & S_{\alpha_2}^{\omega_p} & S_{\alpha_3}^{\omega_p} \\ S_{\alpha_1}^{Q_p} & S_{\alpha_2}^{Q_p} & S_{\alpha_3}^{Q_p} \end{bmatrix}$$

4. Invert the sensitivity matrix ( $\mathbf{M}_3^{-1}$ )

Example:

As an example, suppose that the following measurements result from the 4 conditions in Step 2 (italicized numbers are changed from nominal):

Condition #	1	2	3	4
$R_1$ [ $\Omega$ ]	120	115	120	120
$R_4$ [ $\Omega$ ]	748	748	715	748
$R_9$ [ $\Omega$ ]	1352	1352	1352	1300
$H_p$ [V/V]	0.736	0.729	0.681	0.792
$\omega_p/2\pi$ [MHz]	34.62	34.84	35.51	34.54
$Q_p$ [ ]	2.212	2.110	2.096	2.368

where the Condition # means:

1. Nominal values
2.  $\Delta R_1 \neq 0$ , and  $\Delta R_2 = \Delta R_3 = 0$
3.  $\Delta R_2 \neq 0$ , and  $\Delta R_1 = \Delta R_3 = 0$
4.  $\Delta R_3 \neq 0$ , and  $\Delta R_1 = \Delta R_2 = 0$

The sensitivity of  $H_p$  to  $R_1$  is estimated as:

$$S_{R_1}^{H_p} = \frac{0.729 - 0.736}{0.736} \cdot \frac{120}{115 - 120} \approx 0.23$$

Estimating the other sensitivities produces these sensitivity matrices:

$$\mathbf{M}_3 \approx \begin{bmatrix} 0.23 & 1.69 & -1.98 \\ -0.15 & -0.58 & 0.06 \\ 1.11 & 1.19 & -1.83 \end{bmatrix}$$

$$\mathbf{M}_3^{-1} \approx \begin{bmatrix} -0.95 & -0.70 & 1.00 \\ 0.20 & -1.70 & -0.27 \\ -0.45 & -1.53 & -0.11 \end{bmatrix}$$

## Appendix B - Bibliography

- [1] R. Schaumann, M. Ghausi and K. Laker, *Design of Analog Filters: Passive, Active RC, and Switched Capacitor*. New Jersey: Prentice Hall, 1990.
- [2] A. Zverev, *Handbook of FILTER SYNTHESIS*. John Wiley & Sons, 1967.
- [3] A. Williams and F. Taylor, *Electronic Filter Design Handbook*. McGraw Hill, 1995.
- [4] S. Natarajan, *Theory and Design of Linear Active Networks*. Macmillan, 1987.
- [5] K. Blake, "Component Pre-distortion for Sallen-Key Filters," *Comlinear Application Note*, OA-21, Rev. B, July 1996.
- [6] K. Blake, "Low-Sensitivity, Lowpass Filter Design," *Comlinear Application Note*, OA-27, July 1996.
- [7] K. Blake, "Low-Sensitivity, Highpass Filter Design With Parasitic Compensation," *Comlinear Application Note*, OA-29, Oct. 1996.

## Customer Design Applications Support

National Semiconductor is committed to design excellence. For sales, literature and technical support, call the National Semiconductor Customer Response Group at 1-800-272-9959 or fax 1-800-737-7018.

## Life Support Policy

National's products are not authorized for use as critical components in life support devices or systems without the express written approval of the president of National Semiconductor Corporation. As used herein:

1. Life support devices or systems are devices or systems which, a) are intended for surgical implant into the body, or b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



**National Semiconductor Corporation**  
1111 West Bardin Road  
Arlington, TX 76017  
Tel: 1(800) 272-9959  
Fax: 1(800) 737-7018

**National Semiconductor Europe**  
Fax: (+49) 0-180-530 85 86  
E-mail: europe.support@nsc.com  
Deutsch Tel: (+49) 0-180-530 85 85  
English Tel: (+49) 0-180-532 78 32  
Francais Tel: (+49) 0-180-532 93 58  
Italiano Tel: (+49) 0-180-534 16 80

**National Semiconductor Hong Kong Ltd.**  
13th Floor, Straight Block  
Ocean Centre, 5 Canton Road  
Tsimshatsui, Kowloon  
Hong Kong  
Tel: (852) 2737-1600  
Fax: (852) 2736-9960

**National Semiconductor Japan Ltd.**  
Tel: 81-043-299-2309  
Fax: 81-043-299-2408

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.