

## Low Cost, Low Noise VCO Biasing Circuit for Cable/TV tuners

Ravindra Ambatipudi

National Semiconductor Corporation

Phase-locked loops (PLL) are used in a variety of applications, most notably in Cable and TV tuners. In these, the PLL synchronizes an output signal (typically generated by a Voltage Controlled Oscillator, VCO) with a reference or input signal in frequency as well as in phase. The VCO used in these PLLs requires a biasing circuit. Depending on the VCO used, this biasing circuit is required to provide an output voltage between 24 and 32 Volts from an input voltage of typically 5V, 9V or 12V. Figure 1 shows the circuit diagram of a low cost VCO biasing circuit. This circuit converts a 5V input to an output of 27V, in order to bias the VCO.

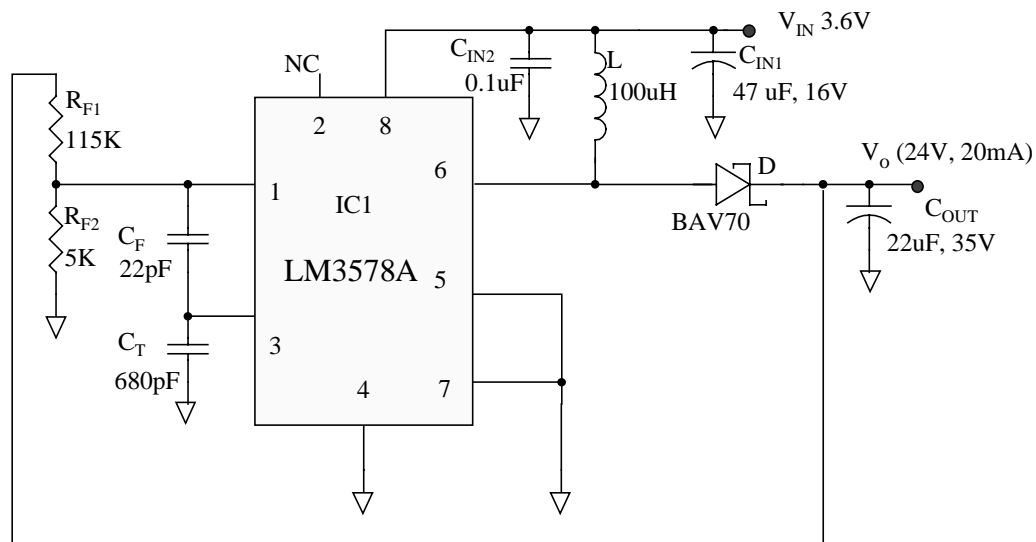


Figure 1

### Converter Specifications:

Input Voltage,  $V_{IN} = 5V$

Output Voltage  $V_{OUT} = 27V$

Load Current  $I_L = 10mA$  (max.)

Switching Frequency,  $f_s = 100kHz$ .

Since the load current requirements are very low, this converter is chosen to operate in discontinuous conduction mode. The output voltage is maintained at 27V by the feedback network consisting of the resistors,  $R_{F1}$  and  $R_{F2}$ . Pins 1 and 2 are set to 1V internally. The output voltage level can be adjusted to the desired value by changing the feedback resistors,  $R_{F1}$  and  $R_{F2}$ , using the equation-

$$V_{out} = 1 + \frac{R_{f1}}{R_{f2}}$$

The switching frequency is set by using the timing capacitor  $C_T$ . Choosing a value of 680pF for  $C_T$  sets the switching frequency at 100kHz. Capacitor  $C_F$  (typically between 10-25 pF), together with the feedback resistors ( $R_{F1}$  and  $R_{F2}$ ), is used for compensation. For more details on the choice of the above components, please refer to the data sheet for LM3578A.

The same circuit will work for 9V or 12V input, with a slight modification. A higher voltage input capacitor will be required. Also, a higher value inductor should be used. Since the current requirements are so low, it is possible to use inexpensive inductor and capacitors in the application. The capacitor  $C_{IN2}$  is enough to suppress the switching noise. An inexpensive input filter can be used to further suppress the noise. The noise is dependent on the ESR of the input and output capacitors. Hence, low-ESR capacitors should be used in this application. This circuit offers advantages of low cost and low noise (figure 2) over other commonly used circuits, such as switched capacitors.

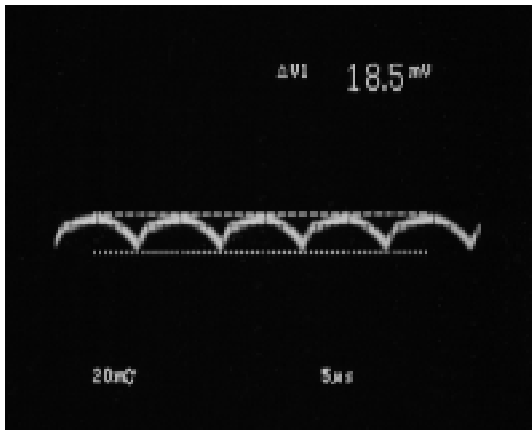


Figure 2(a) Input voltage Ripple  
(18.5mVp-p)


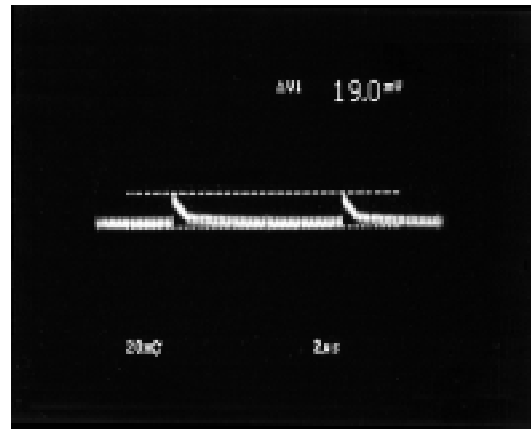


Figure 2(b) Output voltage ripple  
(19.0mV p-p)

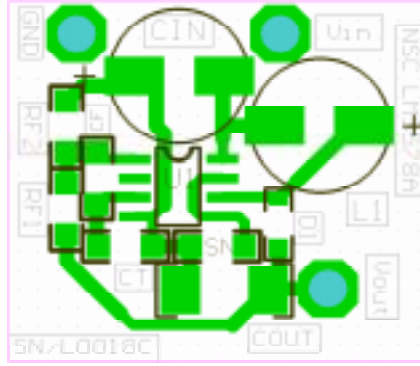

Typical Layout (Scale- 2:1)

### Parts List:

| <i>Designator</i>  | <i>Value</i> | <i>Description</i>                              | <i>Manufacturer</i>    | <i>Part No.</i>  |
|--------------------|--------------|---|------------------------|------------------|
| IC1                | -            | Switching Regulator                             | National Semiconductor | LM3578AM         |
| D                  | 40V, 250mA   | Output diode                                    | Fairchild              | BAV70            |
| L*                 | 100μH, 0.1A  | Boost Inductor                                  | Coilcraft              | DT1608-104       |
| C <sub>IN1</sub>   | 47μF, 16V    | Input Capacitor, surface mount tantalum         | Sprague                | 595C4760016D2W   |
| C <sub>IN2</sub>   | 0.1μF, 50V   | Input capacitor- Required for suppressing noise | Novacap                | 1206N104H250N    |
| C <sub>OUT</sub> * | 22μF, 35V    | Output Capacitor, surface mount tantalum        | AVX                    | TPSE226M035R0300 |
| R <sub>F1</sub>    | 115KΩ        | Feedback resistor                               | Panasonic              | ERJ-8GCRYJ134M   |
| R <sub>F2</sub>    | 5K           | Feedback Resistor                               | Panasonic              | ERJ-8GCRYJ512M   |
| C <sub>F</sub>     | 22pF         | Feedback Capacitor                              | Novacap                | 1206N220H250N    |
| C <sub>T</sub>     | 680pF        | Timing Capacitor, Sets the switching frequency  | Novacap                | 1206B681J250N    |

\* Any inductor with the given rating can be used for this application. Any 22μF,35V low esr capacitor can be used for C<sub>OUT</sub>.