

Design Idea DI-19

LinkSwitch™ Low Cost 1.5 W CV/CC Charger or Adapter



Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Charger/Adapter	LNK501	1.5 W	85-265 VAC	5.5 V	Flyback

Design Highlights

- Replaces a linear transformer based supply at the same or lower cost but with much higher performance
- <0.3 W consumption at zero load meets worldwide guidelines (EC's 0.3 W, USA's 1 W for example)
- Extremely simple circuit – only 15 components for production-worthy design
- Primary based CV/CC output – no secondary sense components required
- $\pm 10\%$ output voltage and $\pm 22\%$ output current tolerances at peak power point
- Fully protected for thermal, short circuit and open loop faults
- >62% efficiency (>70% with R1 replaced by an inductor)
- Meets CISPR22B/EN55022B EMI limits with low cost resistive input filter
- Ultra-low leakage current design <5 μA
- EE13 core for low cost and small size

Operation

The AC input is rectified and filtered by D1, D2, C1 and C2. Conducted EMI filtering is provided both by a π filter (C1, R1 and C2) and a differential filter (RF1 and C1). Together with a shield in the transformer (formed from part of the primary) the design meets conducted EMI limits with no Y-capacitor between primary and secondary. Resistor R1 also functions as a fuse.

LinkSwitch derives all feedback information from the primary. During output diode conduction, the output voltage transformed through the turns ratio is sampled and held by C4. The feedback voltage across C4 (V_{OR}) is converted into feedback current by R2 and fed into the CONTROL pin. This feedback current regulates the output by PWM control during CV operation, and by reducing the internal current limit during CC operation. Below an output voltage of ~ 2 V, LinkSwitch enters auto-restart, limiting average output current to <50 mA. The nominal transition from CV to CC occurs at 5.5 V, 0.27 A. The output envelope characteristic and specification limits are shown in Figure 2.

Together with D3, C4 and R2 are also part of the primary clamp, limiting the peak drain to source voltage due to leakage inductance. Resistor R3 filters the leading edge leakage inductance spike, reducing the error in the feedback voltage. The CONTROL pin capacitor C3 provides energy storage for supply start-up and sets auto-restart timing during fault conditions.

Key Design Points

- Select transformer turns ratio to give a V_{OR} of 40 V to 60 V. Lower values reduce power capability; higher values increase no-load consumption.
- R2 provides 2.3 mA into the CONTROL pin at the peak power point at 85 VAC. The value can be adjusted to center the output voltage.

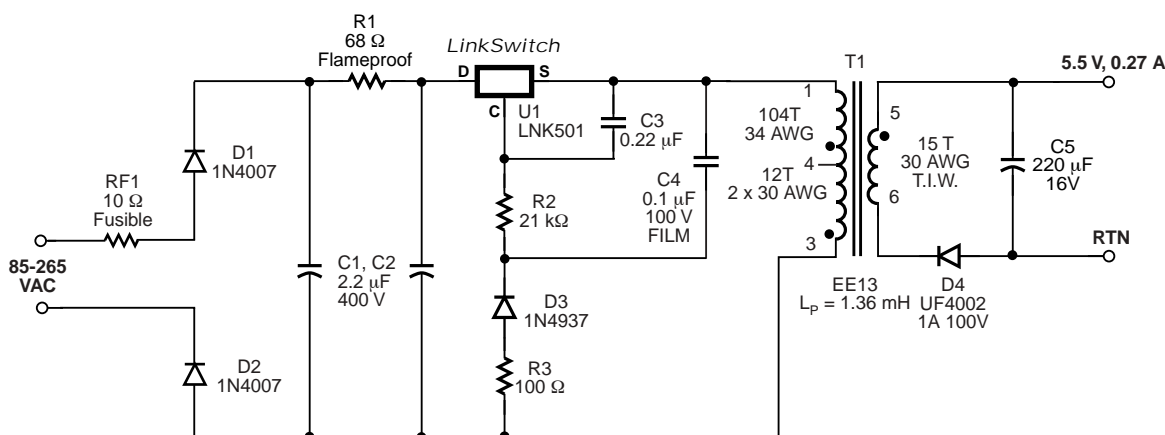


Figure 1. LinkSwitch 1.5 W Charger Power Supply: 85 VAC to 265 VAC Input, 5.5 V, 0.27 A Output

PI-3367-091602

- To maintain the $\pm 22\%$ CC tolerance the primary inductance tolerance should be tighter than $\pm 10\%$.
- Minimize zero load consumption by reducing drain node capacitance: Use double coated/grade 2 wire for primary and do not vacuum impregnate. Avoid using an RC snubber across the output diode.
- For resistive loads, increase C3 to 1 μF (electrolytic) to allow adequate time for start-up at full load.
- For battery loads, an output π filter is typically not required but can be added for resistive loads to reduce switching ripple.
- R1 can be replaced with an inductor for higher efficiency ($\sim 10\%$ increase).
- Adding a 1 mA to 2 mA pre-load reduces zero load voltage by ~ 1 V but increases power consumption by ~ 10 mW.
- Diode D4 can be replaced with a Schottky for higher efficiency.
- See AN-35 for more information.

TRANSFORMER PARAMETERS	
Core	TDK PC40 EE13, $A_L = 101 \text{ nH/T}^2$
Bobbin	EE13 Horizontal 8 pin
Winding Details	Primary: 104T, 34 AWG Shield: 12T, 2 x 30 AWG Secondary: 15T, 30 AWG T.I.W. Flux Band: 1T, 6 mm Cu foil (T.I.W.: Triple Insulated Wire)
Winding Order (pin numbers)	Secondary (5-6), tape, Shield (3-4), tape, Primary (4-1), tape, Flux band (3-NC)
Inductance	Primary: 1.36 mH $\pm 10\%$, Leakage: 50 μH (max.)
Primary Resonant Frequency	300 kHz (minimum)

Table 1. Transformer Construction Information.

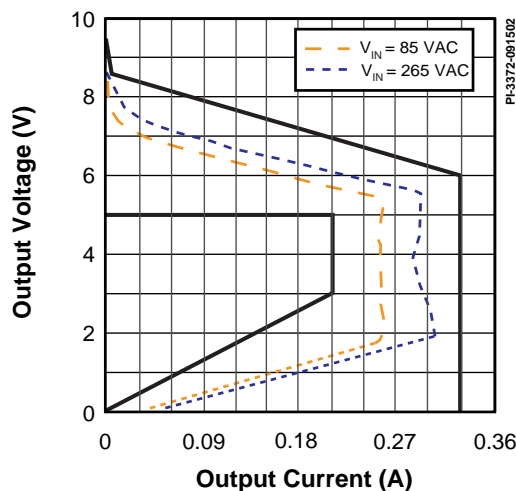


Figure 2. Load Regulation - CV/CC Characteristics with Limits.

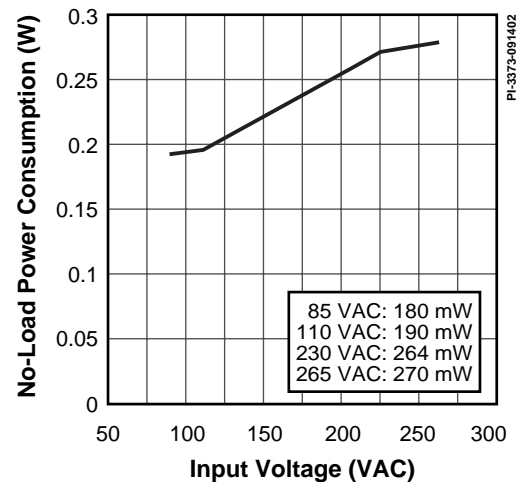


Figure 3. No-load Input Power Consumption.

For the latest updates, visit our Web site: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others. The products and applications illustrated herein may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI Logo, TOPSwitch, TinySwitch and EcoSmart are registered trademarks of Power Integrations, Inc. PI Expert is a trademark of Power Integrations, Inc. ©Copyright 2002, Power Integrations, Inc.

WORLD HEADQUARTERS

AMERICAS

Power Integrations, Inc.
San Jose, CA 95138 USA
Customer Service:
Phone: +1 408-414-9665
Fax: +1 408-414-9765
e-mail: usasales@powerint.com

CHINA

Power Integrations International
Holdings, Inc.
China
Phone: +86-755-8367-5143
Fax: +86-755-8377-9610
e-mail: chinasales@powerint.com

EUROPE & AFRICA

Power Integrations (Europe) Ltd.
United Kingdom
Phone: +44-1344-462-300
Fax: +44-1344-311-732
e-mail: eurosales@powerint.com

KOREA

Power Integrations
International Holdings, Inc.
Seoul, Korea
Phone: +82-2-782-2840
Fax: +82-2-782-4427
e-mail: koreasales@powerint.com

SINGAPORE

Power Integrations, Singapore
Republic of Singapore 308900
Phone: +65-6358-2160
Fax: +65-6358-2015
e-mail: singaporesales@powerint.com

JAPAN

Power Integrations, K.K.
Keihin-Tatemono 1st Bldg.
Japan
Phone: +81-45-471-1021
Fax: +81-45-471-3717
e-mail: japansales@powerint.com

APPLICATIONS HOTLINE

World Wide +1-408-414-9660

TAIWAN

Power Integrations
International Holdings, Inc.
Taipei, Taiwan
Phone: +886-2-2727-1221
Fax: +886-2-2727-1223
e-mail: taiwansales@powerint.com

INDIA (Technical Support)

Innovatech
Bangalore, India
Phone: +91-80-226-6023
Fax: +91-80-228-9727
e-mail: indiasales@powerint.com

APPLICATIONS FAX

World Wide +1-408-414-9760