

# Design Idea DI-29

## **DPA-Switch**<sup>™</sup>

### 25 W Flyback DC-DC Converter



Application	Device	Power Output	Input Voltage	Output Voltage	Topology
DC-DC Converter	DPA425R	25 W	36 - 75 VDC	7 V	Flyback

### Design Highlights

- Extremely low component count
- High efficiency – 85% using Schottky rectifiers
- No current sense resistor or transformer required
- Accurate input under/over voltage meets ETSI standards
- Operates to zero load with no pre-load required
- Output overload, open loop and thermally protected
- 400 kHz operation minimizes size of magnetics


### Operation

*DPA-Switch* greatly simplifies the design compared to a discrete implementation. Resistor R1 programs the input under/over voltages to 33 V and 86 V, respectively. These thresholds have tolerances that guarantee the converter is operational at 36 V, without the cost of additional line sense components.

Resistor R3 programs the internal current limit of the DPA425R to 50% of nominal. The larger *DPA-Switch* selection reduces conduction losses, raising efficiency without circuit changes or increased overload power.

Zener VR1 clamps leakage inductance spikes, keeping the DRAIN voltage below  $BV_{DSS}$ . The bias supply for U1 is provided from an auxiliary flyback transformer winding.

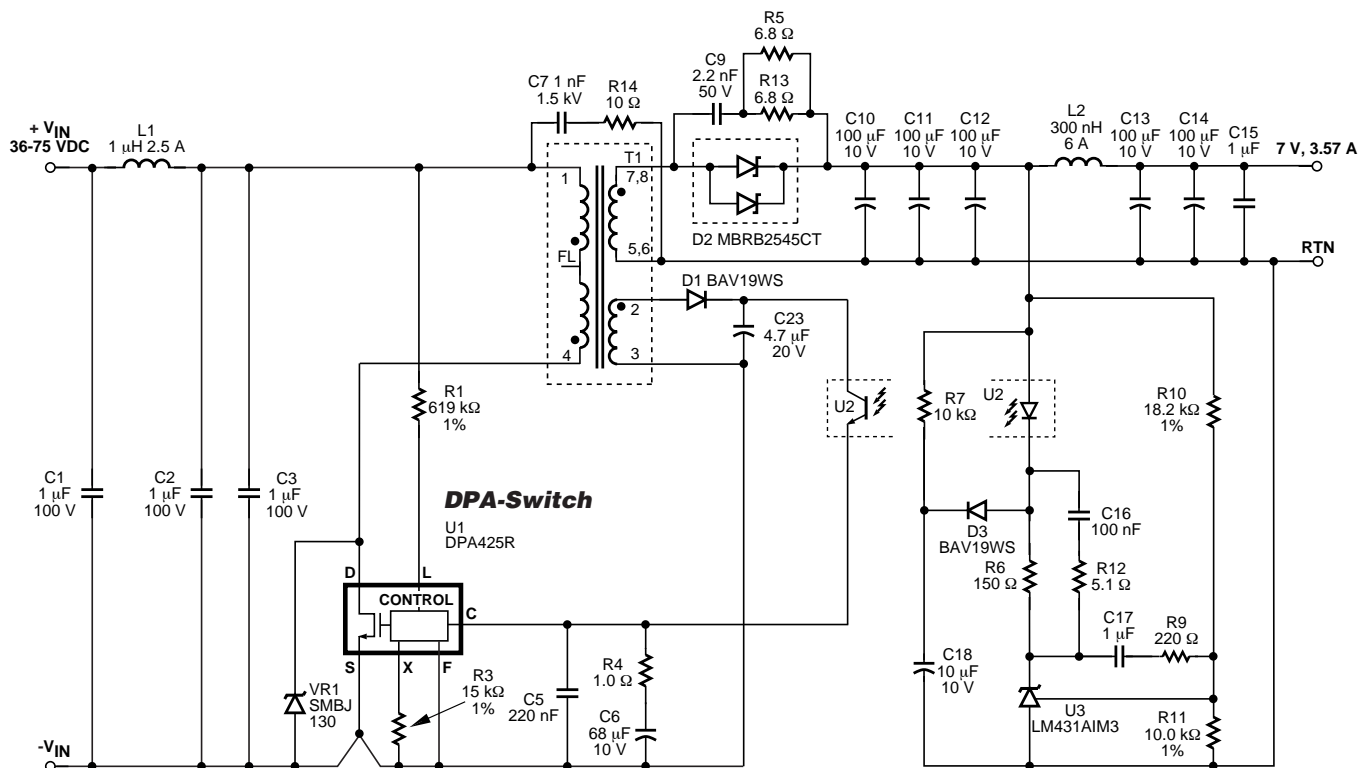On the secondary, a snubber across D2 (C9, R5 and R13) limits the secondary leakage inductance spikes generated by diode reverse recovery. Inductor L2, C13 and C14 form a post-filter to reduce high frequency output switching ripple. A soft-finish network, C18, D3 and R7, eliminates output turn-on overshoot. The remaining components provide output voltage regulation and loop compensation.



PI-3012-091602

Figure 1. *DPA-Switch* Flyback DC-DC Converter Schematic.

## Key Design Points

- For nominal under-voltage set point  $V_{UV}$ :  
 $R1 = (V_{UV} - 2.35 \text{ V}) / 50 \mu\text{A}$ .  $V_{OV} = (R1 \times 135 \mu\text{A}) + 2.5 \text{ V}$ .
- Zener VR1 voltage is 130 V to safely limit the DRAIN voltage below  $V_{DSS}$  of 200 V.
- Opto U2 should have a CTR of between 100% and 200% for optimum loop stability.
- Set resonance of L2 and C13 + C14 to beyond loop crossover frequency (typically 5% to 10% of switching frequency).
- Good layout practices should be followed:
  - Locate C5, C6 and R4 close to U1, with grounds returned to the SOURCE pin.
  - Primary return should be connected to the *DPA-Switch* tab, not the SOURCE pin.
  - Minimize the primary and secondary loop areas to reduce parasitic leakage inductance.

Transformer Parameters	
Core Material	PR1408 Siemens N87 Gap for 340 nH/T <sup>2</sup>
Bobbin	P1408 8 pin (B&B B-096 or equivalent)
Winding Details	Primary: 6T + 6T, 2 x 27 AWG Secondary: 3T, 4 x 25 AWG Bias: 6T, 32 AWG
Winding Order (pin numbers)	Primary (4-FL), tape, Bias (2-3), tape, Secondary (5,6-7,8), tape, Primary (FL-1), tape
Inductance	Primary: 49 $\mu\text{H} \pm 10\%$ , Leakage: 1 $\mu\text{H}$ (max)
Primary Resonant Frequency	3.8 MHz (minimum)

Table 1. Transformer Construction Information.

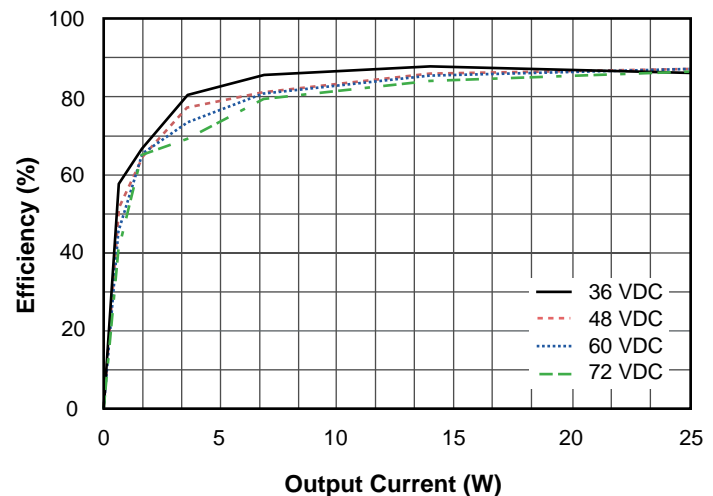


Figure 2. Efficiency vs. Output Power.

For the latest updates, visit our Web site: [www.powerint.com](http://www.powerint.com)

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others. The products and applications illustrated herein may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at [www.powerint.com](http://www.powerint.com).

The PI Logo, **TOPSwitch**, **TinySwitch** and **EcoSmart** are registered trademarks of Power Integrations, Inc. **PI Expert** is a trademark of Power Integrations Inc. ©Copyright 2002, Power Integrations, Inc.

### WORLD HEADQUARTERS AMERICAS

Power Integrations, Inc.  
San Jose, CA 95138 USA  
Customer Service:  
Phone: +1 408-414-9665  
Fax: +1 408-414-9765  
e-mail: [usasales@powerint.com](mailto:usasales@powerint.com)

### CHINA

Power Integrations International  
Holdings, Inc.  
China  
Phone: +86-755-8367-5143  
Fax: +86-755-8377-9610  
e-mail: [chinasales@powerint.com](mailto:chinasales@powerint.com)

### EUROPE & AFRICA

Power Integrations (Europe) Ltd.  
United Kingdom  
Phone: +44-1344-462-300  
Fax: +44-1344-311-732  
e-mail: [eurosales@powerint.com](mailto:eurosales@powerint.com)

### KOREA

Power Integrations  
International Holdings, Inc.  
Seoul, Korea  
Phone: +82-2-782-2840  
Fax: +82-2-782-4427  
e-mail: [koreasales@powerint.com](mailto:koreasales@powerint.com)

### SINGAPORE

Power Integrations, Singapore  
Republic of Singapore 308900  
Phone: +65-6358-2160  
Fax: +65-6358-2015  
e-mail: [singaporesales@powerint.com](mailto:singaporesales@powerint.com)

### JAPAN

Power Integrations, K.K.  
Keihin-Tatemono 1st Bldg.  
Japan  
Phone: +81-45-471-1021  
Fax: +81-45-471-3717  
e-mail: [japansales@powerint.com](mailto:japansales@powerint.com)

### APPLICATIONS HOTLINE

World Wide +1-408-414-9660

### TAIWAN

Power Integrations  
International Holdings, Inc.  
Taipei, Taiwan  
Phone: +886-2-2727-1221  
Fax: +886-2-2727-1223  
e-mail: [taiwansales@powerint.com](mailto:taiwansales@powerint.com)

### INDIA (Technical Support)

Innovatech  
Bangalore, India  
Phone: +91-80-226-6023  
Fax: +91-80-228-9727  
e-mail: [indiasales@powerint.com](mailto:indiasales@powerint.com)

### APPLICATIONS FAX

World Wide +1-408-414-9760