

LNB SUPPLY AND CONTROL VOLTAGE REGULATOR (PARALLEL INTERFACE)


F. Lentini - G. Benenati

1. ABSTRACT

LNB is the integrated solution for supplying/interfacing satellite LNB modules. It gives good performances in a simple and economical way, with a minimum use of external components. It is comprised of functions that realize LNB supplying/interfacing in accordance to the international standards.

2. INTRODUCTION.

Figure 1: Basic Satellite Installation

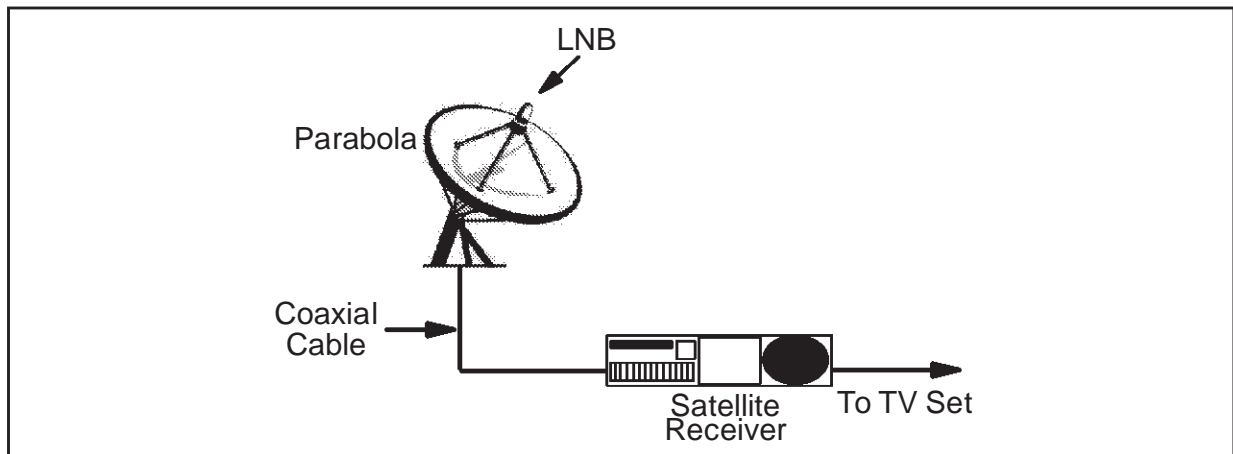

A typical satellite receiver system is formed by these blocks (reported in figure 1):

1. The **parabola** is the antenna of the system and focuses the satellite signal to the LNB;
2. The **LNB** (low noise block) is placed on the focus of the parabola and converts the incoming signal in the 10GHz range to a lower frequency signal (in the 1-2GHz range) called "first conversion signal". This allows the signal to be carried by an inexpensive coaxial cable towards the receiver. Additionally, it improves the first conversion signal level by a built-in low noise amplifier. A universal LNB can change the type of polarization (horizontal or vertical) or operative band by command signals sent by the receiver;
3. The **coaxial cable** joins the LNB to the receiver and carries out 3 functions:
 - a) to transfer the first conversion signal from the LNB to the receiver;
 - b) to transfer the command signals from the receiver to the LNB to change polarization or signal band;
 - c) to carry the DC voltage to supply the LNB.
4. The **receiver** converts the first conversion signal into signals for the TV system. The receiver provides for that provides for two important features:


- a) to supply the LNB block;
 - b) to generate all the signals/voltages that LNB needs to operate correctly.
5. The **supply/interface block** is placed inside the receiver. It must perform the following functions:
- a) be ready to accept future digital standards with an external modulation input and fast oscillator start-up;
 - b) implement the loop-through function in slave condition for single dish, multiple receiver system;
 - c) accept the paralleling of 2 or more receivers and, in this condition, avoid the flow of reverse current from the output to the GND;
 - d) give accurate, thermal compensated outputs with the possibility to compensate the DC voltage drop caused by long coaxial cables;
 - e) be reliable;
 - f) provide overload (better if dynamic) and thermal protection with diagnostic;
 - g) avoid every type of trimming;
 - h) provide the possibility to be driven by a microcontroller or a simple digital logic to implement all these functions;
 - i) Finally, it must be cheap and get a small area in the board.

All these functions are hard to be implemented with discrete components, but are greatly made easier by using an integrated device, like LNBP, that has been specially designed for this purpose.

3. FUNCTIONAL BLOCKS.


LNBP comprises the following operative blocks (see figure 2):

Figure 2: Internal Block Diagram

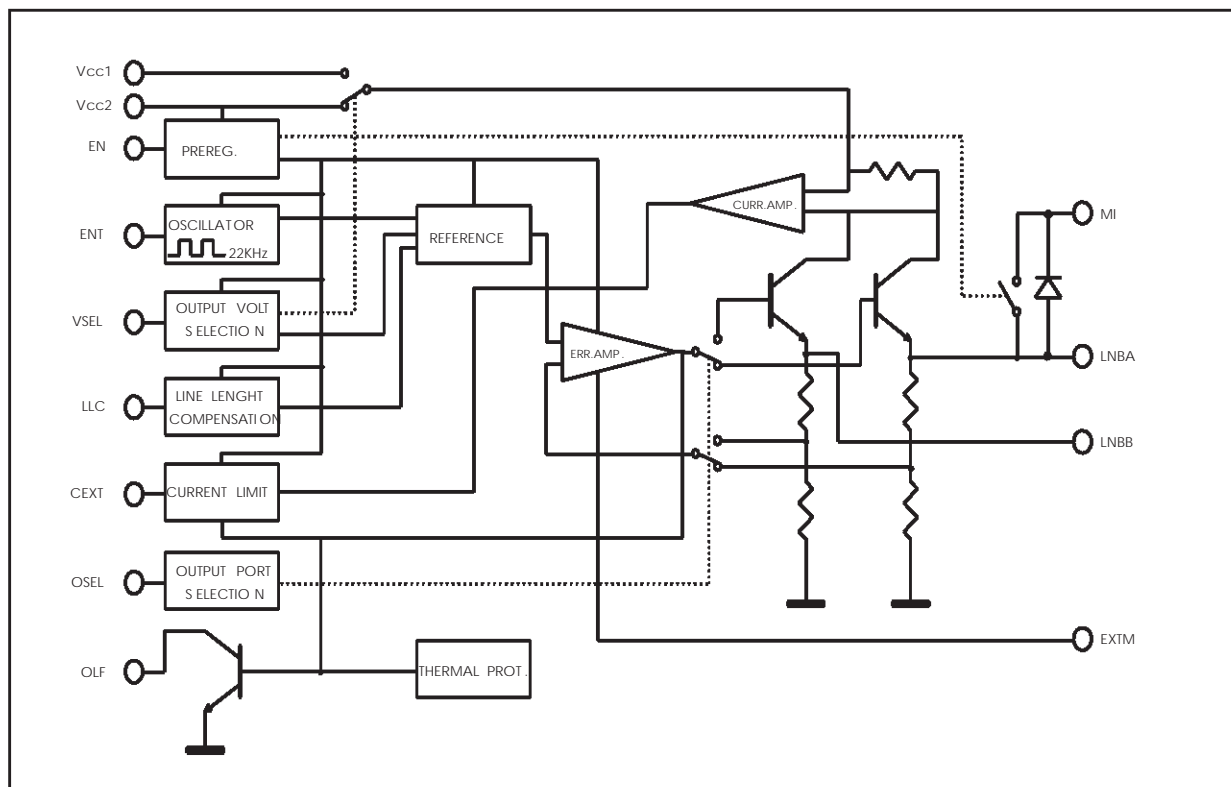

1. The **oscillator** is activated by putting the ENT pin (Enable Tone) = H and is factory trimmed at 22KHz \pm 2KHz, avoiding the need to use external trimming. The rise and fall edges are controlled to be in the 5 to 15 μ s range, 10 μ s typ., to avoid RF pollution towards the receiver. The Duty Cycle is 50% typ. It modulates the DC output with a \pm 0.3V amplitude and 0V average. The presence of this signal usually gives the LNB information about the band to be received.
2. The **OSEL (OUTPUT PORT SELECTION)** selects the two outputs of the LNB (LNBA and LNBB), in order to drive a dual-dish system, depending on its present state. When OSEL is L, the LNBA port is selected. When OSEL is H, the LNBB port is selected. The LNBA and LNBB outputs supply either 13V or 18V. If VSEL is low (VSEL = L) 13V is selected, otherwise, if VSEL is high (VSEL = H) 18V is selected. This kind of feature changes the LNB polarization type. The LNB switches horizontal or vertical polarization depending on the supply voltage it gets from the receiver.
3. In order to keep the power dissipation of the device low, the **input selector** automatically selects Vcc1, that is the lowest input voltage, when 13 V out is selected (i.e. VSEL is L). If 18V out is selected (i.e. VSEL is H), Vcc2 input is selected. So power dissipation at Iout=500mA is: $P_d = (22-18) \cdot 0.5 = 2W$ (with Vcc2=22V and Vout=18V) or $(15-13) \cdot 0.5 = 1W$ (with Vcc1=15V and Vout=13V). Without input selection we should have $P_d = (22-13) \cdot 0.5 = 4.5W$, which is much higher. Moreover, an internal switch selects the **MI (MASTER INPUT)** to be transferred to the LNBA when the EN pin is low. This case occurs when two receivers are connected in series and the slave receiver (the nearest to the antenna) is disabled. The master receiver supplies the LNB by means of the MI input of the slave receiver.
4. The **line length compensation** function is useful when the antenna is connected to the receiver by a long coaxial cable that adds a considerable DC voltage drop. When the LCC pin is H, the output voltage selected is increased by about 1V.
5. The **reference** drives all the internal blocks that require a high precision thermal compensated voltage source.
6. The LNB has two different **protection** features, and both turn off the outputs. The first one acts in overload conditions (i.e. for output current $\geq 500mA$), and the second for overheating (i.e. for $T_{amb} \geq 150^\circ C$).
 - a) The overload protection case occurs when output current request is $\geq 500mA$. In this condition the device limits the output current at 500mA for a time T_{on} depending on the Cext value. When T_{on} has elapsed, output goes low for a time of $T_{off} = 15 \cdot T_{on}$. This keeps the power dissipated by the device low in overload conditions, and avoids to oversize the heatsink in such a condition.
 - b) In the thermal protection case the output is disabled until the chip temperature has fallen. After that the LNB restarts working properly. The LNBA bypass switch is not protected, so the MI input must be driven by a current limited voltage source.

Figure 3: LNB Pin Grouping

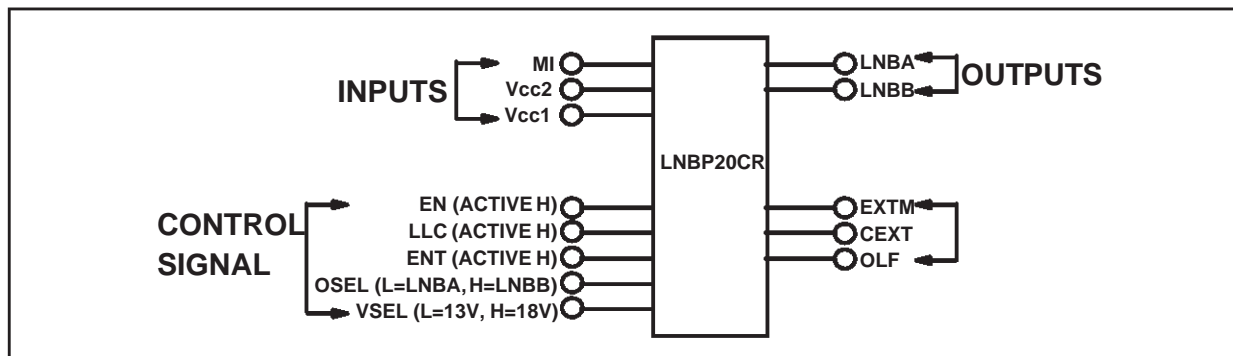

In figure 3 the LNBP pins are grouped by functions. The 5 control signals are logic inputs that control the IC function, and it is recommended that the V_{IH} not exceed 7V.

C_{ext} controls the restore timing of the overload protection. If an overload protection is present, output goes low for a time imposed by the C_{ext} value. At the same time the OLF pin, an open collector output, goes low.

In figure 4 and figure 5 the behavior of T_{on} and T_{off} times vs. C_{ext} is respectively shown. When T_{off} has elapsed, the output returns active for a time $T_{on}=T_{off}/15$. Then, OLF returns a high impedance output. If the overload is still present the cycle is repeated. This behavior greatly reduces the dissipation in the device. In fact, in short circuit conditions with $V_{cc2}=25\text{ V}$, considering I_{out} internally limited at 650mA and $T_{off}=15*T_{on}$ we obtain: $P_d \text{ average} = V_{in} * I_{out} * T_{on} / (T_{on} + T_{off}) = 25 * 0.65 * 1 / (1 + 15) = 1.02\text{ W}$, that is lower than the power dissipated in normal conditions.

Figure 4: Overload Protection On Time versus C_{ext}


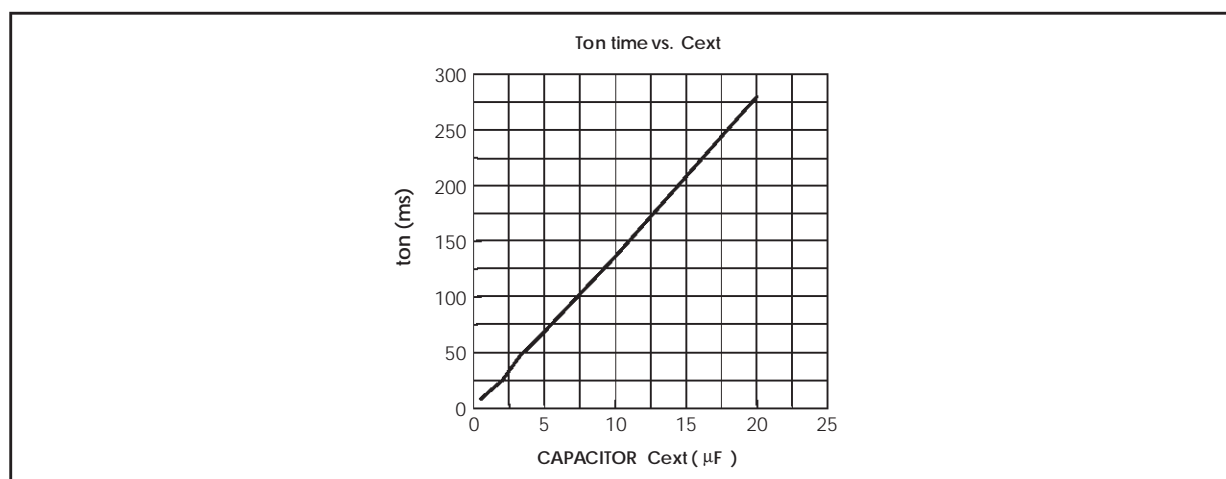


Figure 5: Overload Protection Off Time versus C_{ext}

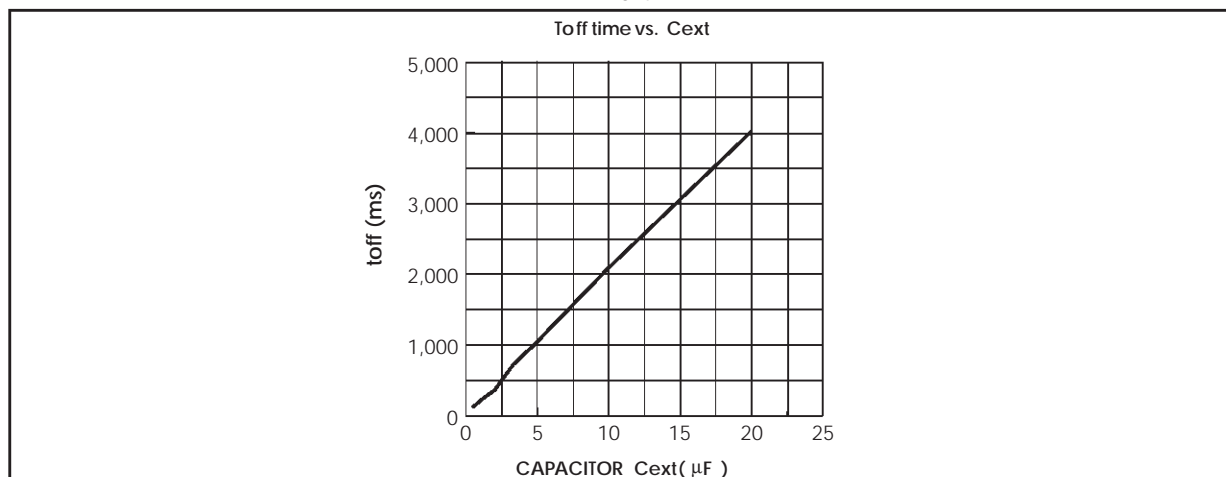

The C_{ext} must be properly chosen. It is related to the I_{out} and C_{out} (total capacitor connected to the LNBA or LNBB output) values. Large C_{out} values at start-up give high current peak for a long time, and consequently, an overload condition for a time that could be greater than the T_{on} imposed by C_{ext} . So the output will be forced low, completely discharge and will not start. For proper use it is necessary that

$C_{out}/C_{ext} \leq 20$. The OLF also gives information about the thermal protection status. If the thermal protection is triggered, the output is disabled and the OLF goes low. When the chip temperature has fallen, the output returns active and the OLF returns to its 3-state condition.

By sensing the ON/OFF ratio of the OLF signal, a microcontroller can discriminate if an overload or a thermal protection is present.

EXTM modulates the V_{out} by a capacitor connected in series (see figure 6). In this case:

$V_{out\ a.c.} = V_{in\ a.c.} \cdot V_{out\ d.c.} / 3$ where, respectively, $V_{out\ a.c.}$ and $V_{in\ a.c.}$ are alternate components of V_{out} and V_{in} , and $V_{out\ d.c.}$ is the direct component of V_{out} . For example, if an a.c. signal of 600mV p.p. must be imposed to the 13V d.c. out, the formula is as follows:

$V_{in\ a.c.} = 3 \cdot V_{out\ a.c.} / V_{out\ d.c.} = 3 \cdot 600 / 13 \approx 140\ mV\ p.p.$ If we dispose a 0-5V square wave signal to modulate output voltage, it is necessary to lower this signal amplitude. In accordance to figure 7 we have: $R1 = R2 \cdot (V1/V_{in} - 1)$.

Figure 6: How to Use EXTM Input


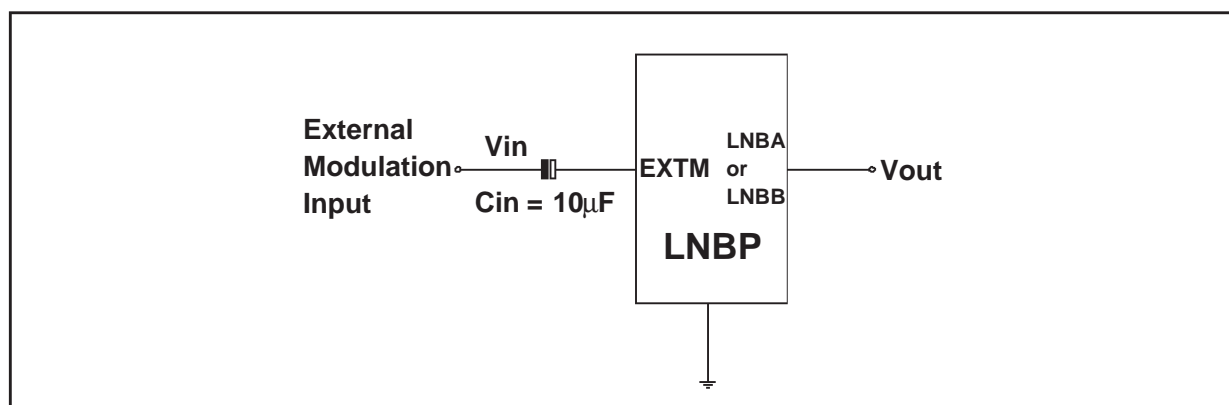


Figure 7: How to Adjust the External Modulation Level

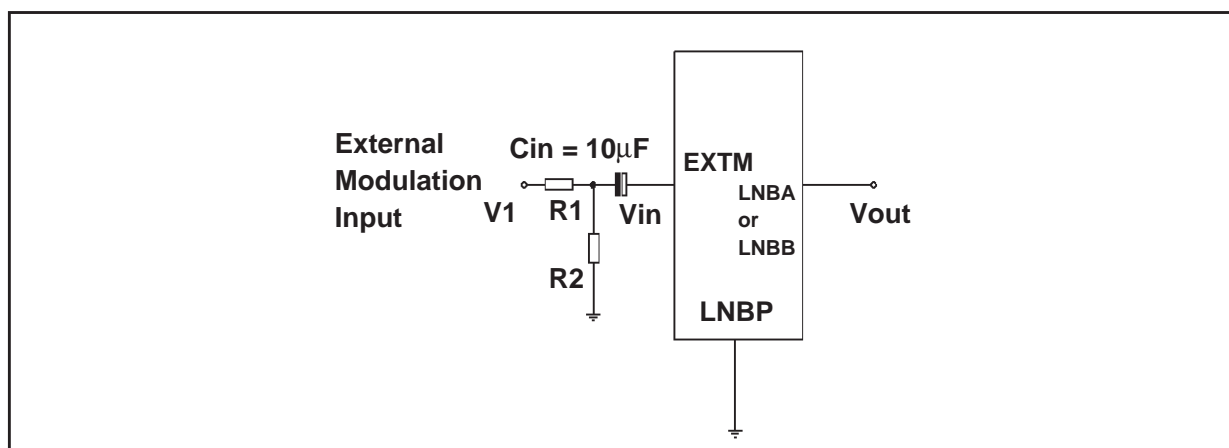

$R2$ must be in the 50Ohm range to minimize the effects of the EXTM input resistance variations. In our example we obtain:

$$R1 = 50 \cdot (5/0.14 - 1) = 1.7k\Omega$$

As a side effect, the EXTM modifies the V_{out} by a resistor connected between this input and the GND. Figure 8 and 9 report the V_{out} value vs. R .

Figure 8: Vout Value vs. Resistance on the EXTM pin at VSEL = L

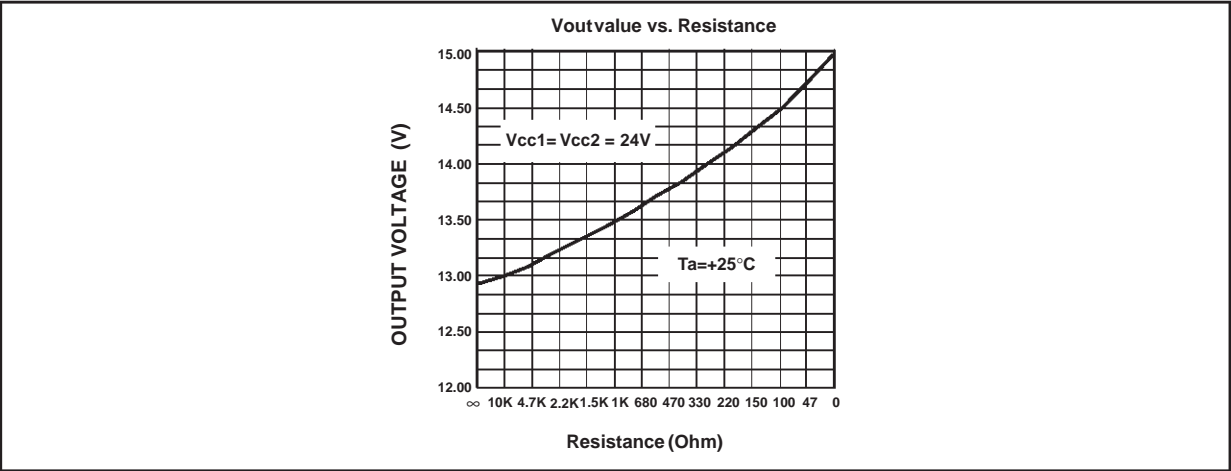


Figure 9: Vout Value vs. Resistance on the EXTM pin at VSEL = H


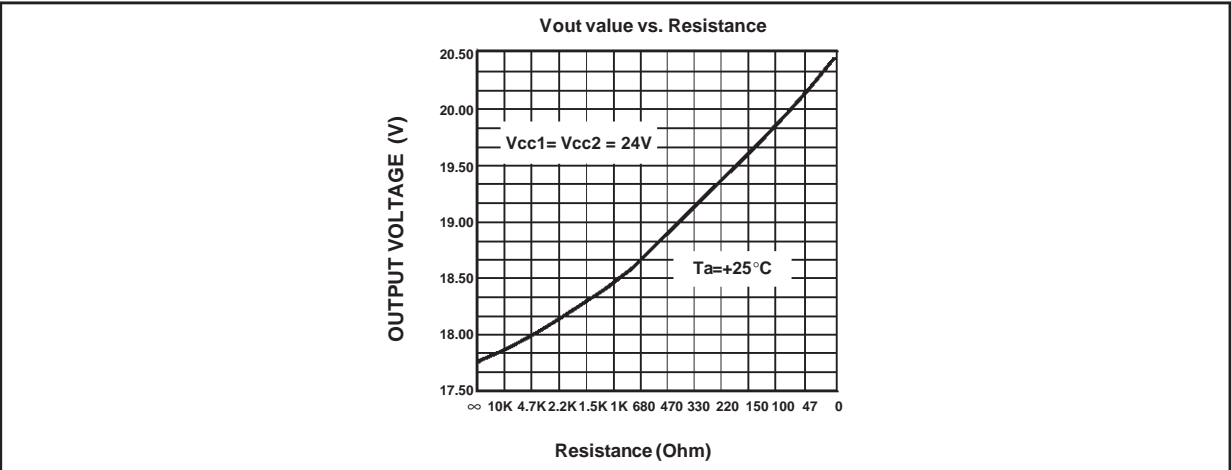


Figure 10: LNBP Output Stages

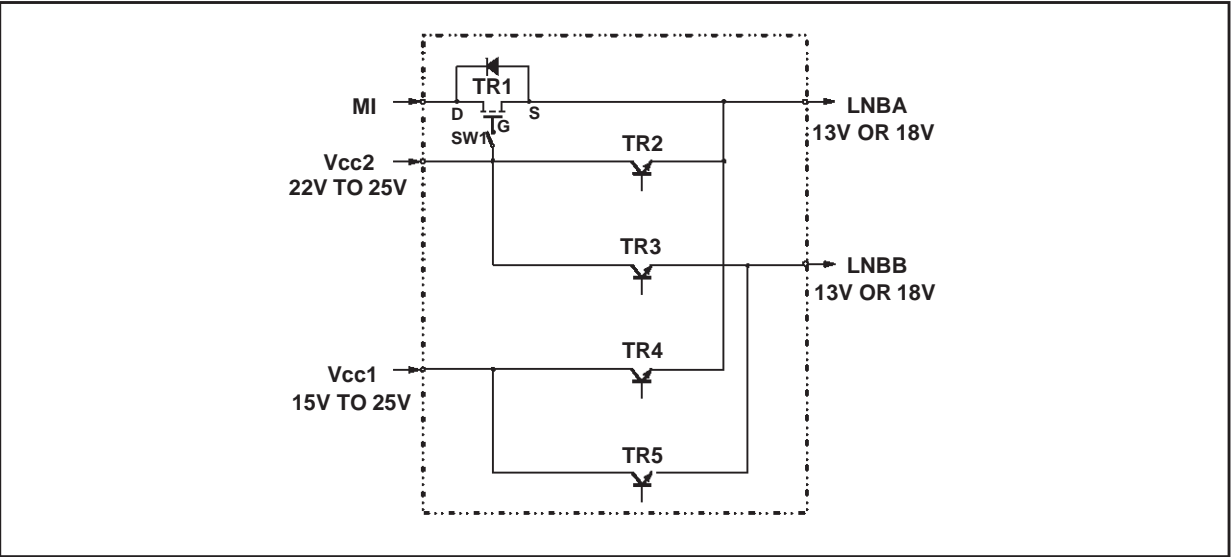

4. OPERATING MODE.

LNBP has 3 power inputs (V_{cc1} , V_{cc2} and MI) and two outputs (LNBA, LNBB) internally connected in accordance to the scheme reported in figure 10. By analyzing this scheme we can make out the following results:


1. TR1 is an N-channel Power MOSFET with its source connected to the LNBA. It is driven by SW1, that joins the gate to V_{cc2} . The drop between MI and LNBA is due to the R_{on} of TR1, but in some conditions it is increased by inadequate driving. In fact we have:
 $V_{drop} = V_{drain} - V_{source} = V_{MI} - (V_{cc2} - V_{gs}) = V_{gs} - (V_{cc2} - V_{MI})$.

We can see that the drop can be minimized increasing the $(V_{cc2} - V_{MI})$ value. For example, if V_{cc2} increases, the effect of inadequate driving is cancelled.



V_{gs} depends on the TR1 and I_{out} characteristics. Figure 11 gives the V_{gs} vs. I_{out} plot, with $V_{cc2} - V_{MI}$ as the parameter. Therefore, given I_{out} , V_{cc2} and V_{MI} we can calculate the V_{drop} . If $V_{cc2} = 22V$, $MI = 21V$ and $I_{out} = 500mA$ the formula is as follows: $V_{drop} = V_{gs} - 1V$. In figure 11 it results that $V_{gs} = 3.1V$ at $I_{LOAD} = 500mA$ and $V_{cc2} - V_{MI} = 1V$ and in such conditions $V_{drop} = 3.1V - 1V = 2.1V$.

If we increase V_{cc2} at 26V we obtain: $V_{drop} = 5.65V - 5V = 0.65V$, which is much lower.

Figure 11: Loop-Through Switch Gate Voltage

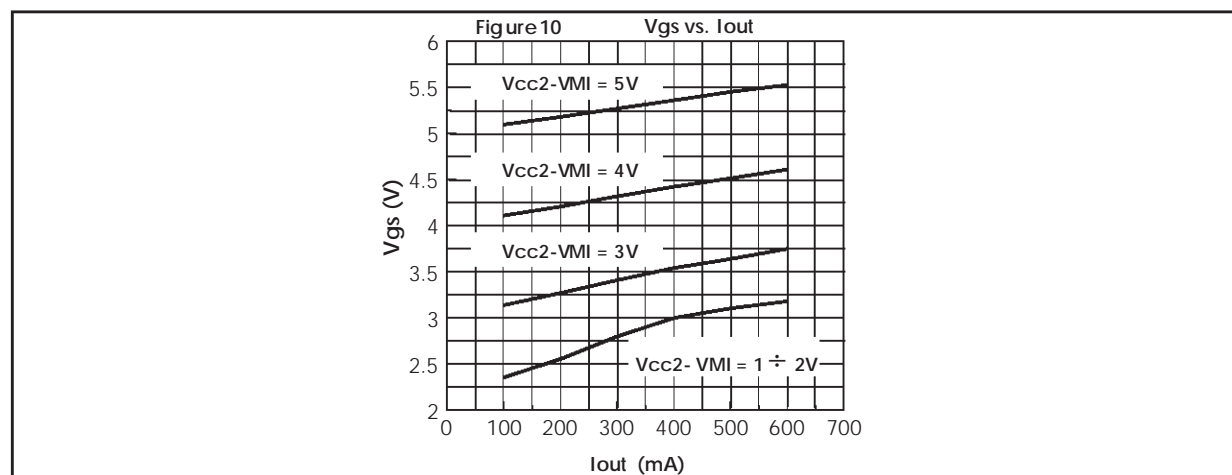

2. In some cases it happens that two or more receivers share the same coaxial cable making their output hard paralleled, so the same voltage is present at the outputs of the receivers. If a receiver is not disconnected at the mains, it will flow a current from the LNBA to the MI by means of the parasitic D-S TR1 diode. Moreover, the TR2 (or TR4) $B_{V_{b-e}}$ could be exceeded, so a reverse current could flow from the LNBA to V_{cc2} (or V_{cc1}) or from the LNBB to V_{cc2} (or V_{cc1}), with possible destruction of the relative transistor. To overcome this drawback it is enough to add one or two diodes, depending on how many outputs are used, in series at the LNBA or LNBB pins (see figure 12). In this case we have to consider the voltage drop across the diode that is load and temperature dependent. These effects can be minimized by using Schottky diodes and activating the LLC function.

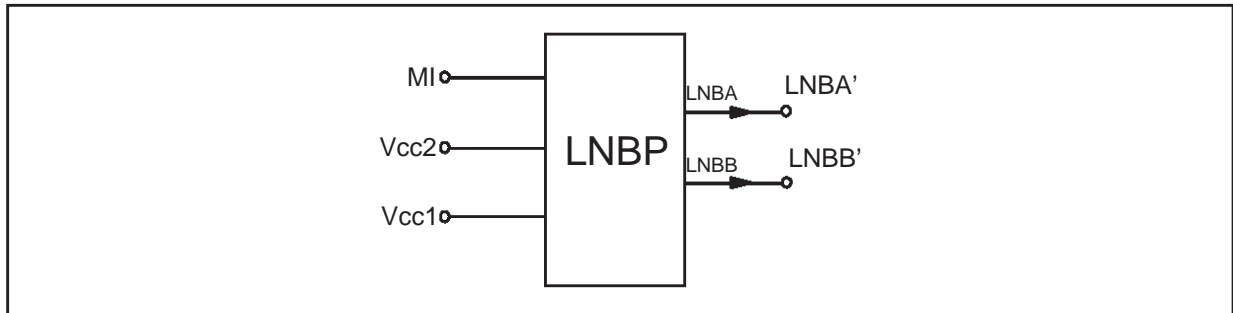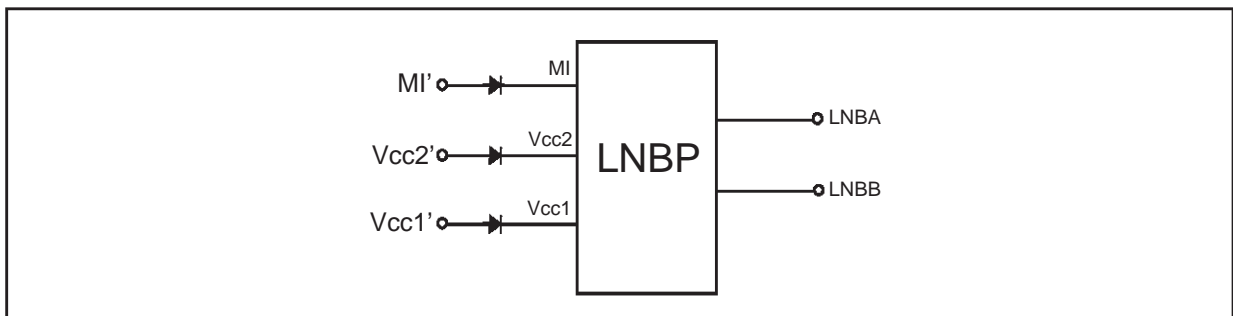Figure 12: Reverse Current Protection Using Diodes on the Outputs

Figure 13: Reverse Current Protection Using Diodes on the Inputs


3. In alternative we can add one, two or three diodes, depending on how many inputs are used, in series at the MI, Vcc1 and Vcc2 input pins (see figure 13). In this case diodes do not cause a change at Vout, but only worsen the voltage drop, which can be minimized by using Schottky diodes. Diodes used in figures 12 and 13 must withstand a continuous current of almost 1A and a breakdown voltage of 30V (suggested type is BYV10-30).

5. APPLICATION HINTS.

1. LNBP has an LLC pin to compensate the voltage drop across the cable. This pin adds a discrete 1V value at the selected output voltage when it is active. It is also possible to obtain a continuous variation of the LNBA or LNBB voltage by using EXTM input.
2. If only a single 22V source is suitable, at the cost of higher power losses in the device and higher heatsink surface, it is possible to power the Vcc1 and Vcc2 pins by the same 22V source without affecting any other circuit performance. In order to reduce power dissipation in the device, it can be useful to insert an adequate resistor in series to the Vcc1 pin (see figure14). This resistor must be dimensioned considering that the minimum voltage on the Vcc1 pin must be ≥ 16 V, with a supply current $I_{SUPPLY} = 500$ mA.
This means: $R \leq (22-16) / 500 \cdot 10^{-3} \cong 12$ Ohm.
Power dissipated in this resistor is:
 $P_d = R \cdot I_{out}^2 = 12 \cdot (500 \cdot 10^{-3})^2 = 3W$.
It is recommended to bypass the Vcc1 and Vcc2 pins by 2.2μF electrolytic capacitors.

3W is the power dissipated saved by the device.

3. If Vcc2 is not inserted (i.e. the receiver is not connected to the mains) the TR1 can not bypass MI to the LNBA, because the gate is not driven (see figure 10). It is possible to overcome this drawback by using the scheme reported in figure 15.

Figure 14: How to Get Vcc1 Using a Drop Resistor


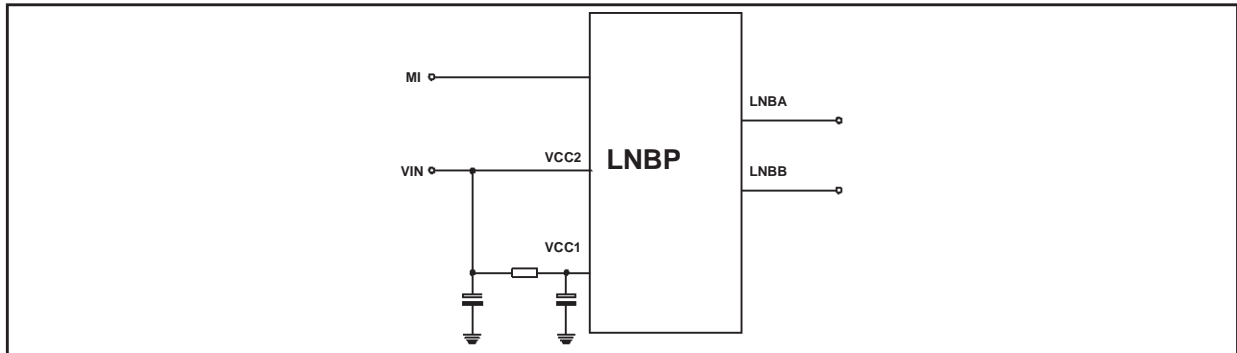



Figure 15: A Loop-Through Switch That Works Without Vcc2

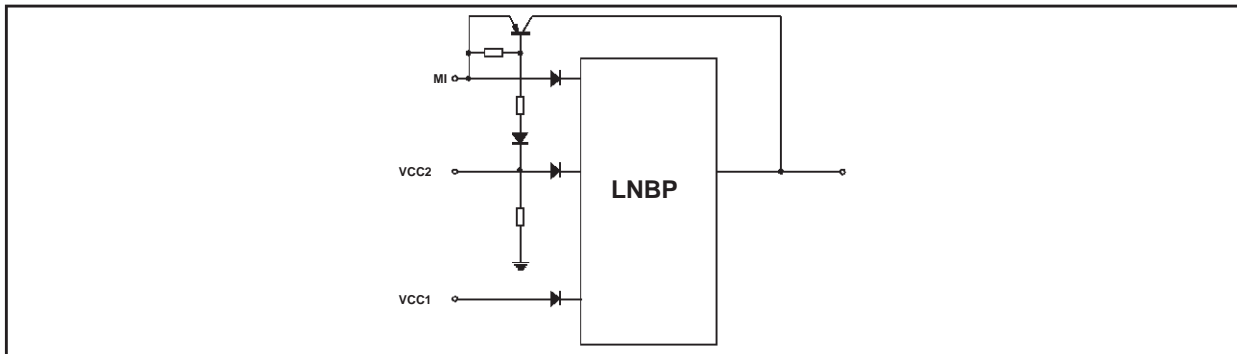

6. SINGLE SUPPLY APPLICATION.


In some applications (TV receivers, PC cards, etc.) a 12V power supply is available. It is possible to use this voltage to supply the LNBP. Figure 16 reports the schematic of the application proposed. It uses an MC34063 to step-up the 12V input at a value of 16V or 23V, depending on the Vsel status. If Vsel is H (i.e. the LNBP gives 18V at out LNBA), a 23V voltage is available at point A. If Vsel is L (i.e. the LNBP gives 13V at out LNBA), a 16V voltage is available at point A. This keeps the power dissipated by LNBP low and gives good efficiency because the LNBP is supplied with a minimum drop. Diode D2 protects the LNBP by reverse current. If the LNBP is disabled (i.e. En is L), the 23V voltage is selected at point A, regardless of the Vsel status. The changing voltage at point A is actuated by HC03, which is an open-drain quad 2-input nand gate.

Figure 16: Single Supply Application Using MC34063A Plus LNBPxx

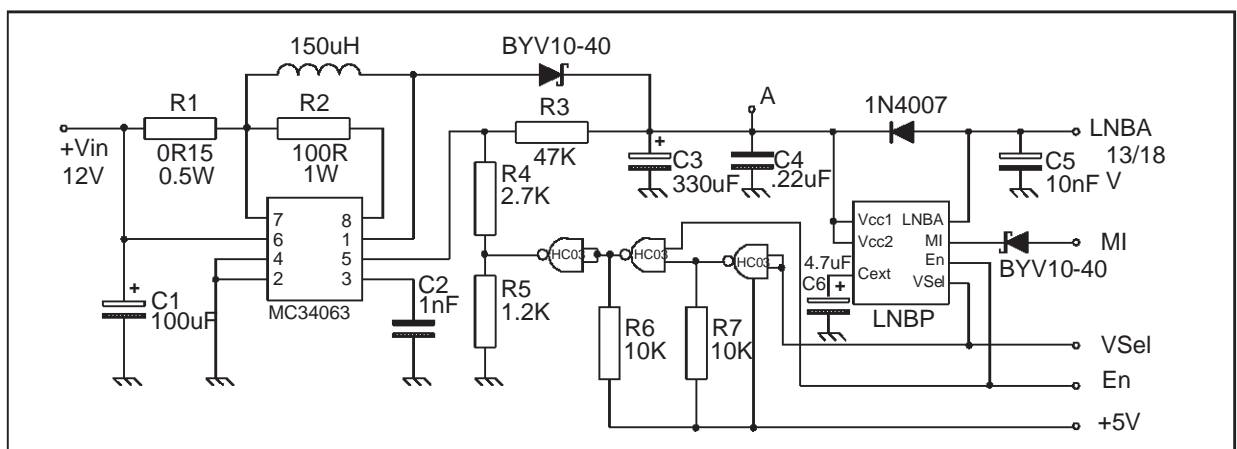

7. DiSEqC* SPECIFICATION.


Figure 17: Impedance Matching for DiSEqC

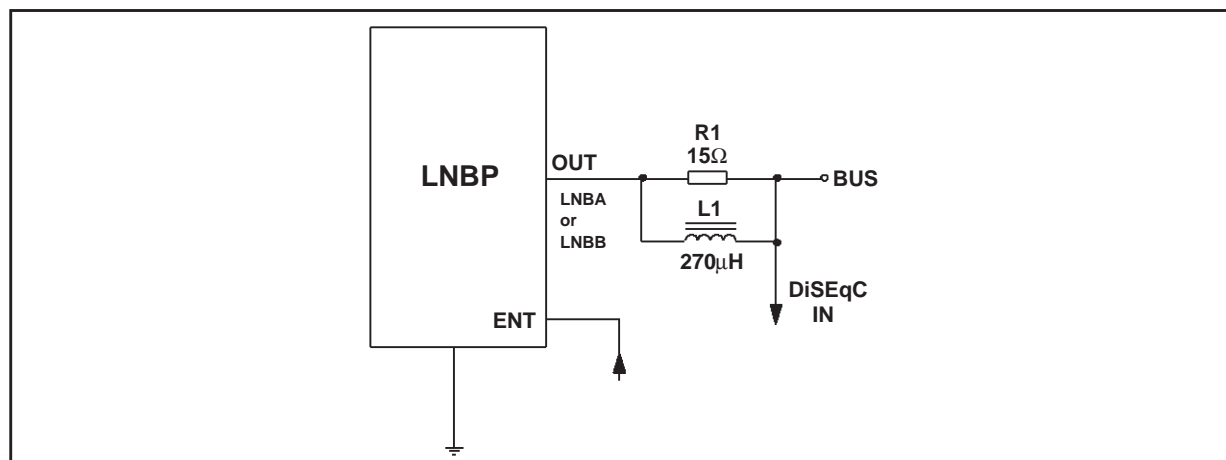

The DiSEqC standard was born to implement the most complex system required, for example, by multiple-satellite installations, where multiple LNB placed in the parabola must communicate with the receiver in a two-way mode. This standard is compatible with 13/18V and 22kHz tone and is easily implemented by a microcontroller. It requires hardware specifications that are faithfully satisfied by LNB. In particular, the bus impedance can be matched using the scheme reported in figure 17.

8. THERMAL MANAGEMENT.

Figure 18: Thermal Resistance versus On-Board Copper Heatsink Area

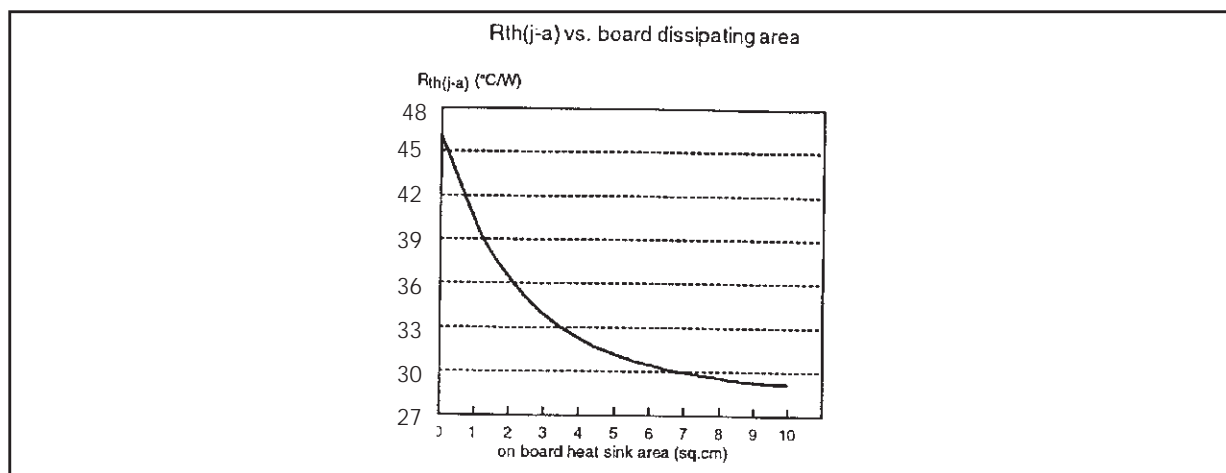

LNB has a built-in dynamic protection system that considerably lowers the power dissipation in short or overload conditions. Therefore, the operative condition is the worst condition for power dissipation. LNB is available in 3 packages: PowerSO-10, PowerSO-20 and MULTIWATT15. The last package can be assembled on a heatsink with:

$R_{th \text{ heatsink}} \leq (T_j - T_{amb}) / P_d - R_{thjc} - R_{thcs}$, where:

T_j = junction temperature (can be fixed at 150°C max);

P_d = dissipated power = $\sum (V_{in} - V_{out}) \cdot I_{out}$;

R_{thjc} = junction-case thermal resistance $\sim 2^\circ\text{C/W}$;

R_{Thcs} = case-heatsink thermal resistance $\sim 1 \div 1.5^{\circ}\text{C/W}$.

For SMD packages we must obtain the right R_{Thtot} . This can be achieved soldering the metallic case of the package on an adequate copper surface that acts like a heatsink. In the figure 18 the typical $R_{Thtot} = R_{Th} \text{ heatsink} + R_{Thjc} + R_{Thcs}$ vs. copper surface is shown, for a board with 1 or 2 layers. In the 2 layers case, a convenient number of ways ($\sim 9/\text{cmsq}$) must be provided. For best results these ways must be inserted below the device and near it. Doubling the surface we obtain a 3°C/W of R reduction.

Figure 19: Electrical Schematic Board of PowerSO-20™


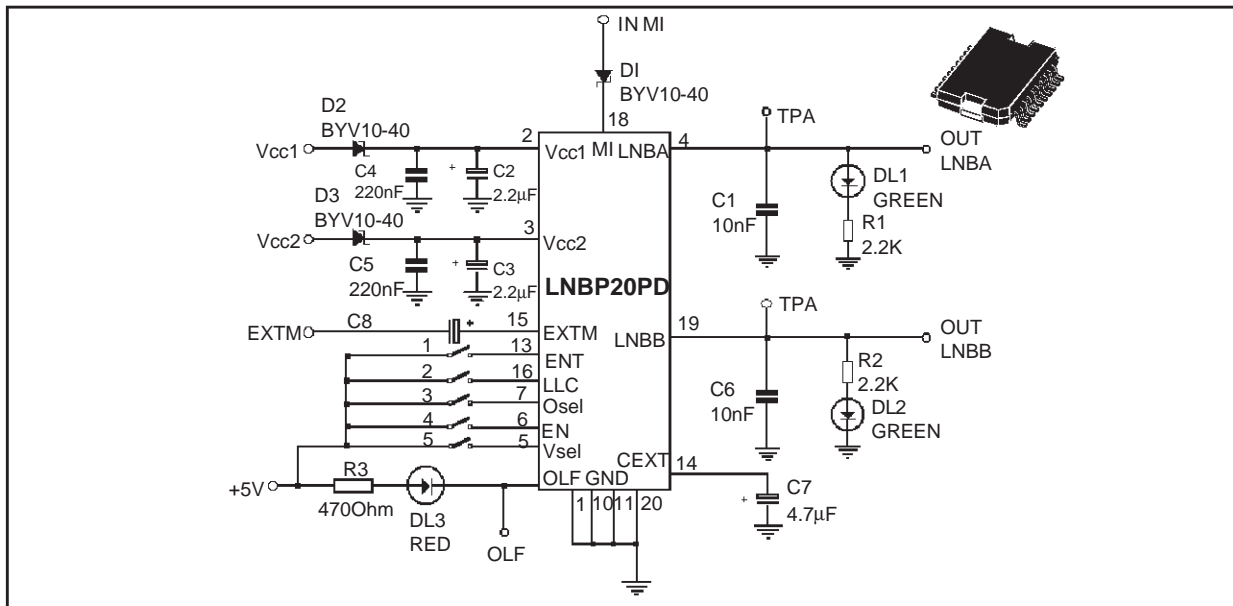


Figure 20: Electrical Schematic Demoboard of MULTIWATT15™

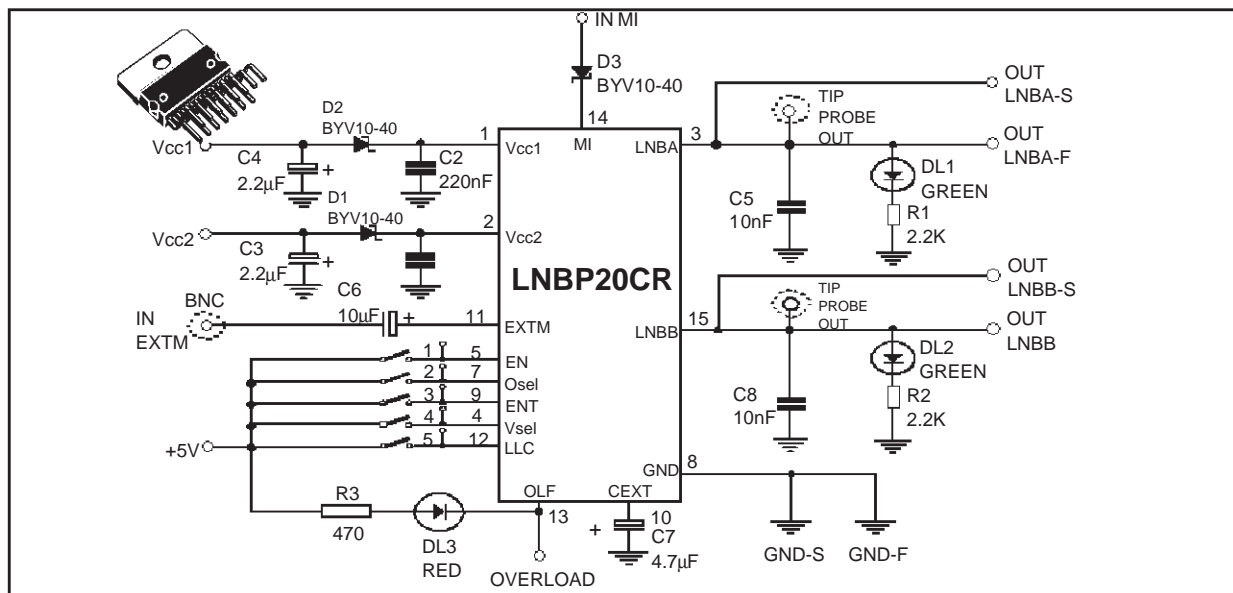

The two demoboards of the LNB of the PowerSO-20 and MULTIWATT packages are shown below. The different layer drawings are shown in figure 19 and 20. The first one is based on the PowerSO-20 package and the second on the MULTIWATT packages.

Figure 21: PowerSO-20 Demoboard


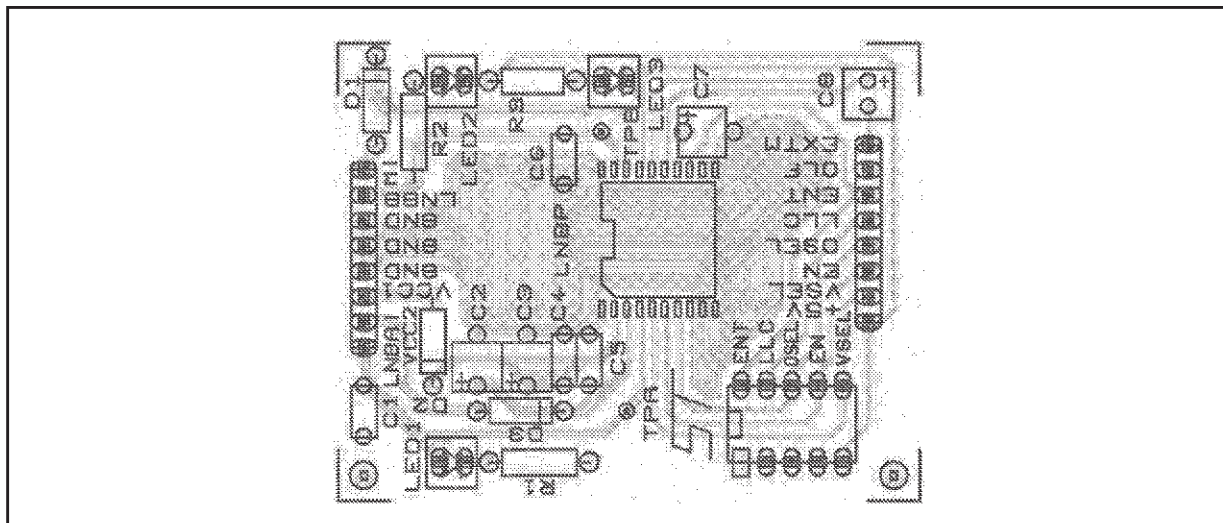


Figure 22: MULTIWATT15 Demoboard

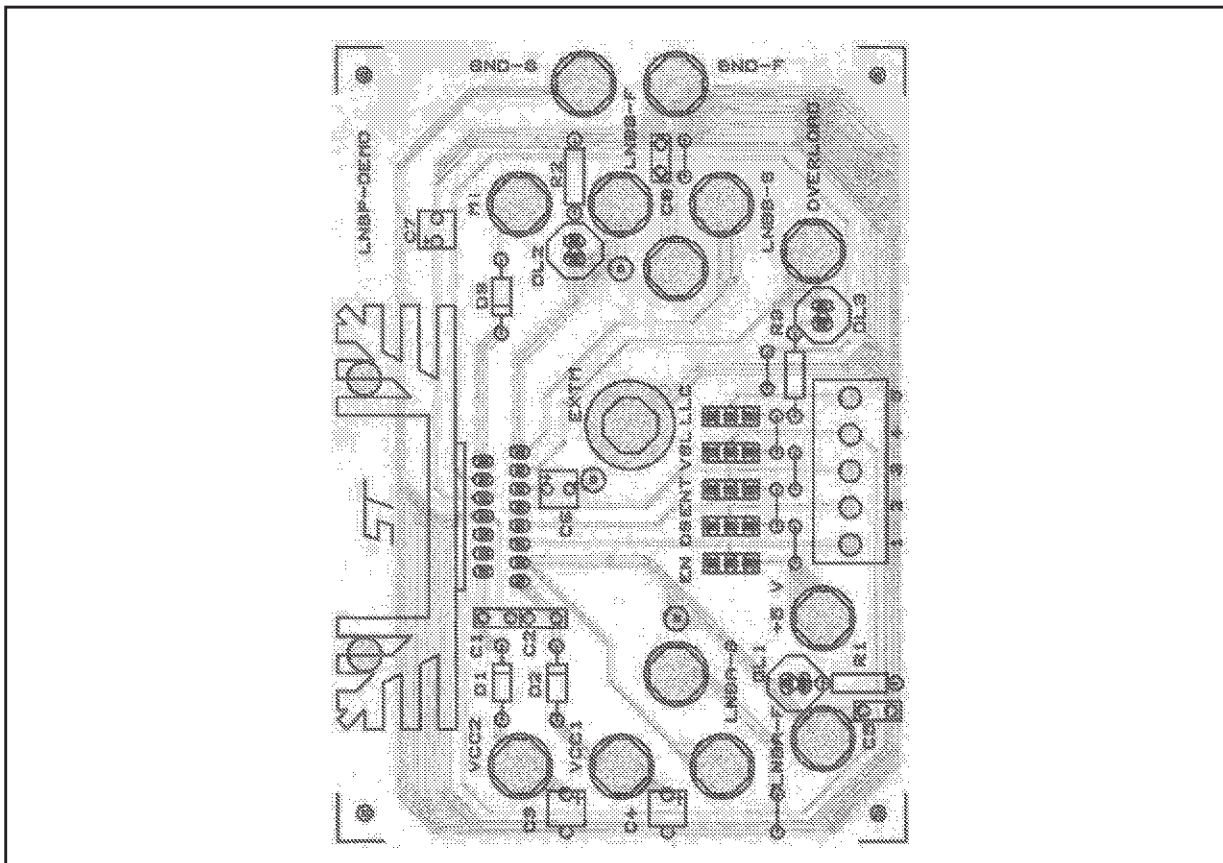

10. SCHEMATIC CIRCUIT DESCRIPTION.

10.1 POWER SO-20™ Package.

Two comb connectors (8 pins each) are used for the input and output voltage and for all control signals (Vsel, EN, Osel, LLC, ENT). It is possible to force at high levels all the control signals through a 5 pin dip-switch. If the control signals come from outside the board, the dip-switches must be in the OFF position. An oscilloscope probe can be connected to the TPA and TPB test points to monitor the 22KHz signal.

10.2 MULTIWATT™ Package.

The MULTIWATT electric schematics is shown in figure 20. In the board some plugs are provided for the input of the following signals: Vcc1, Vcc2, MI, +5V and GND (force and sense). Also, LNBA and LNBB (force and sense) are connected by plugs. The load is connected between the output connector LNBA-F (or LNBB-F) and GND-F. Between the LNBA-S (or LNBB-S) and GND-S two voltmeters can be connected to monitor the output voltage. Besides, two plugs connected with the two outputs permit the

insertion of the oscilloscope probes to monitor the 22kHz tone. The EXTM input can be connected to the relative BNC connector. It is, moreover, possible to force at high level the following inputs: *EN*, *Osel*, *ENT*, *Vsel*, and *LLC* by five switches. It is moreover possible to force such inputs even through the five poles connector. In this case all the switches must be in off position.

11. CONCLUSION

This paper gives practical information to develop numerous applications using this solution for supplying satellite LNB. The use of the existing LNBP Demoboard allows the development of the final product. On the next pages there are numerous examples of typical application schematics based on LNBP.

Typical Application Schematics are shown below.

Figure 23: Two Antenna Ports Receiver

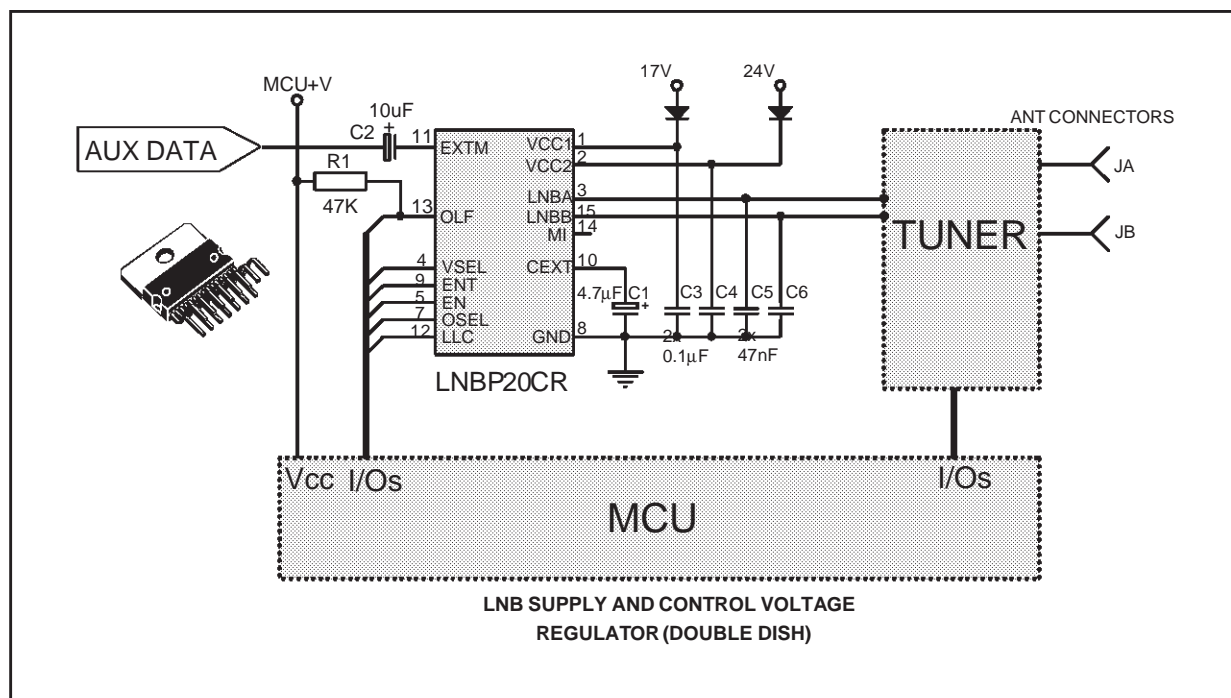


Figure 24: Single Antenna Receiver with Master Receiver Port


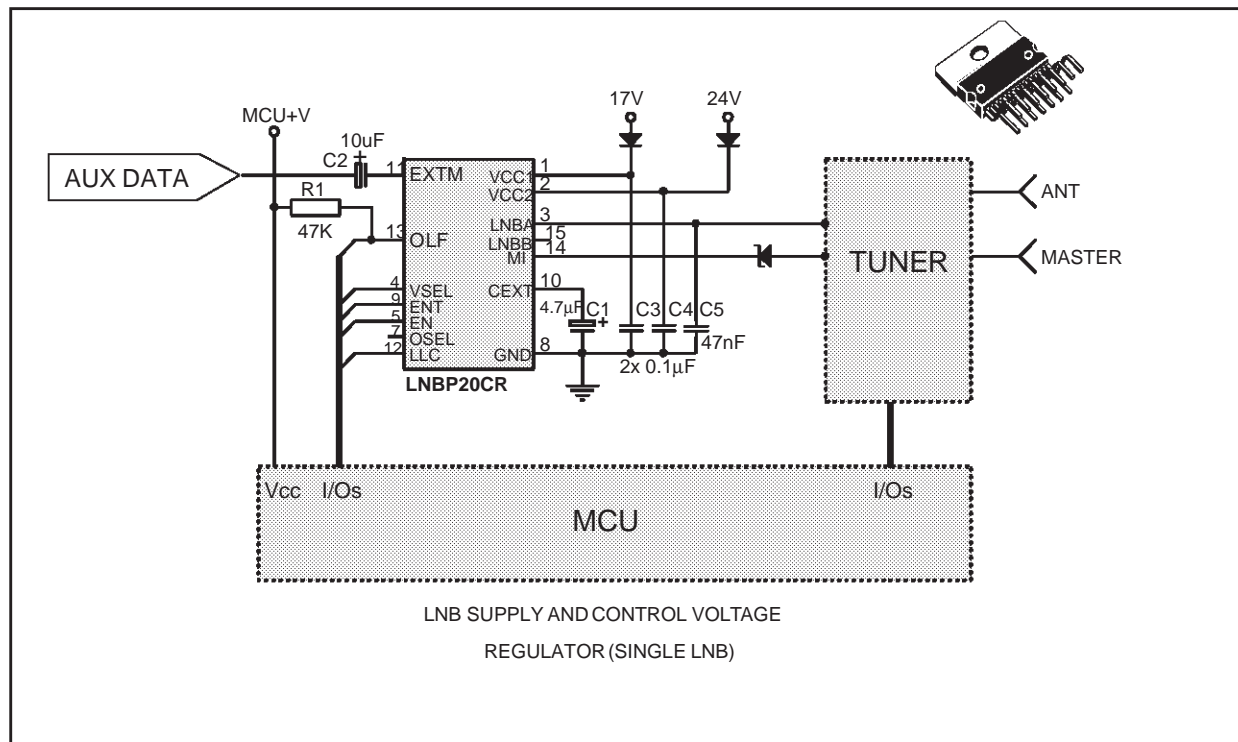


Figure 25: Using Serial Bus to Save MPU I/Os

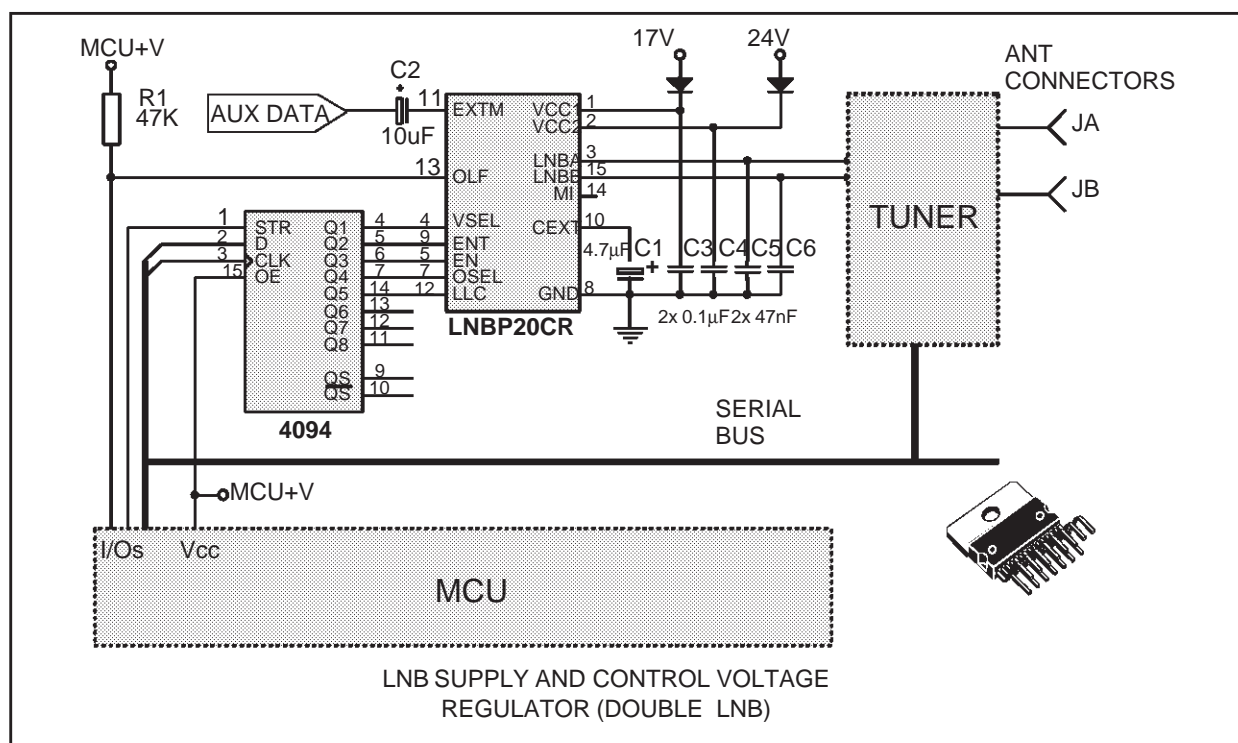

Typical Schematics cont'd

Figure 26: Two Antenna Ports Receiver

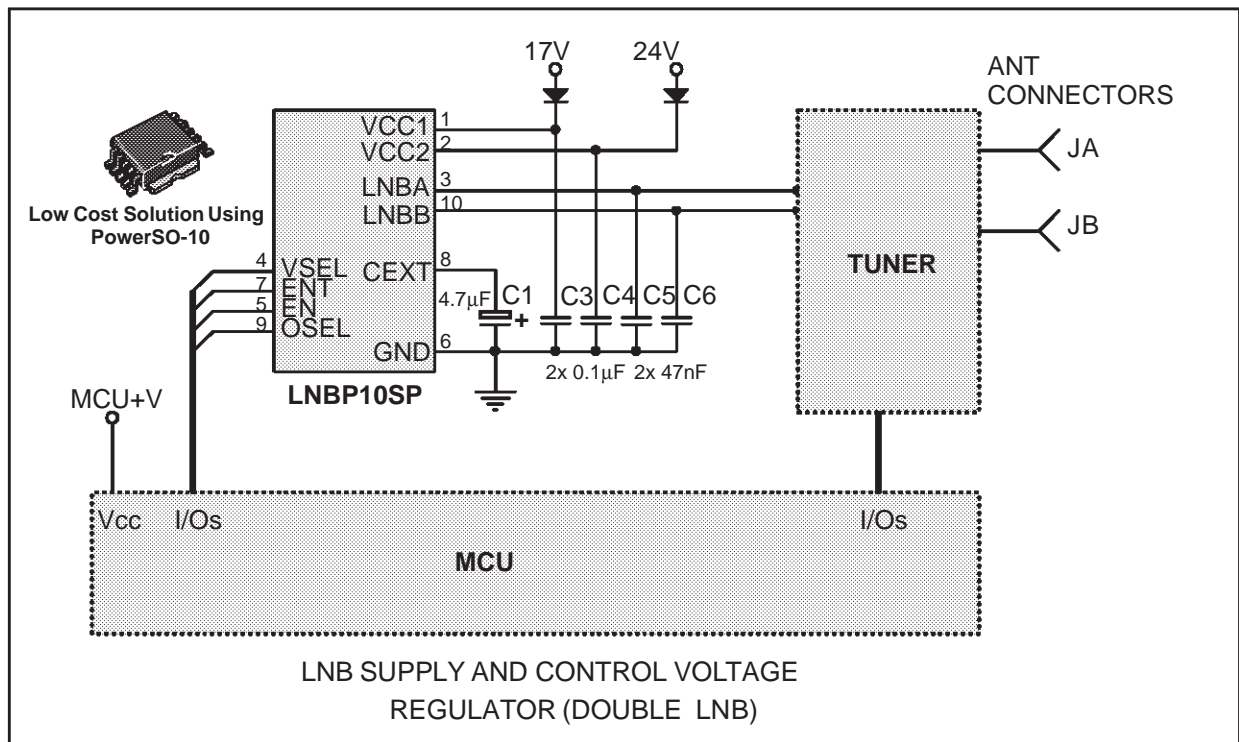


Figure 27: Connecting Together Vcc1 and Vcc2

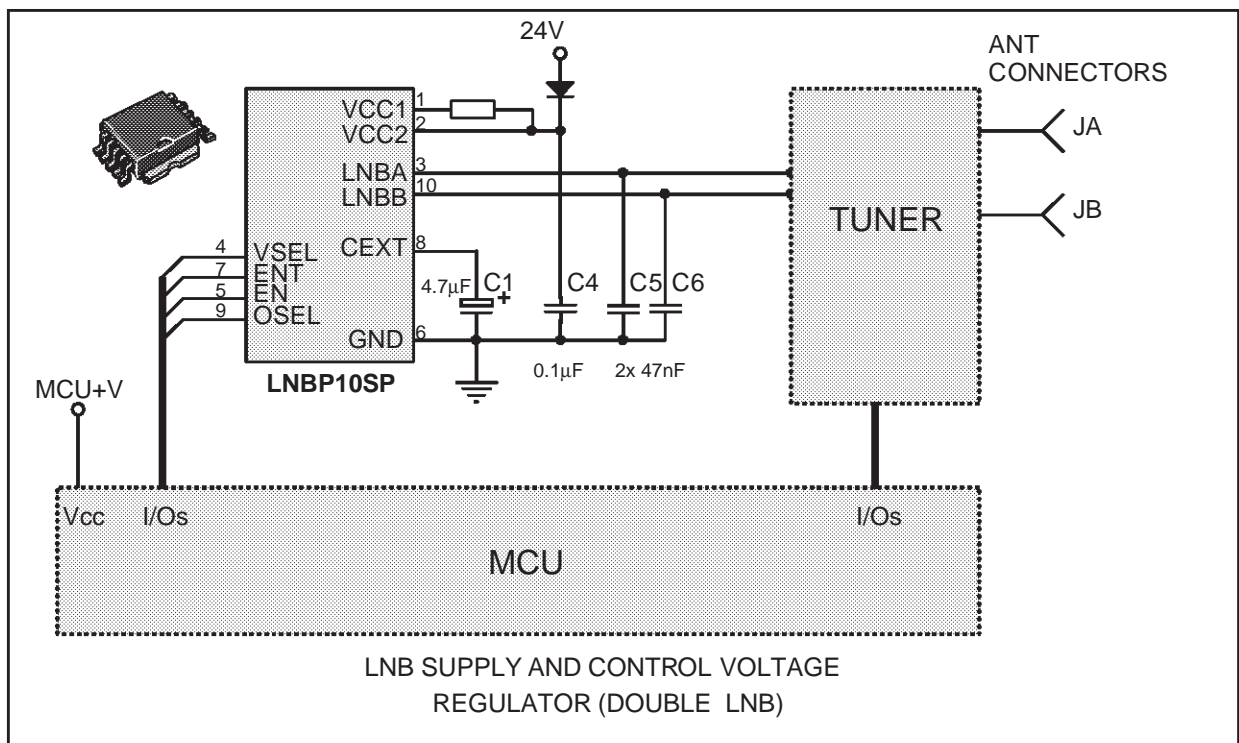


Figure 28: Single Antenna Receiver with Master Port


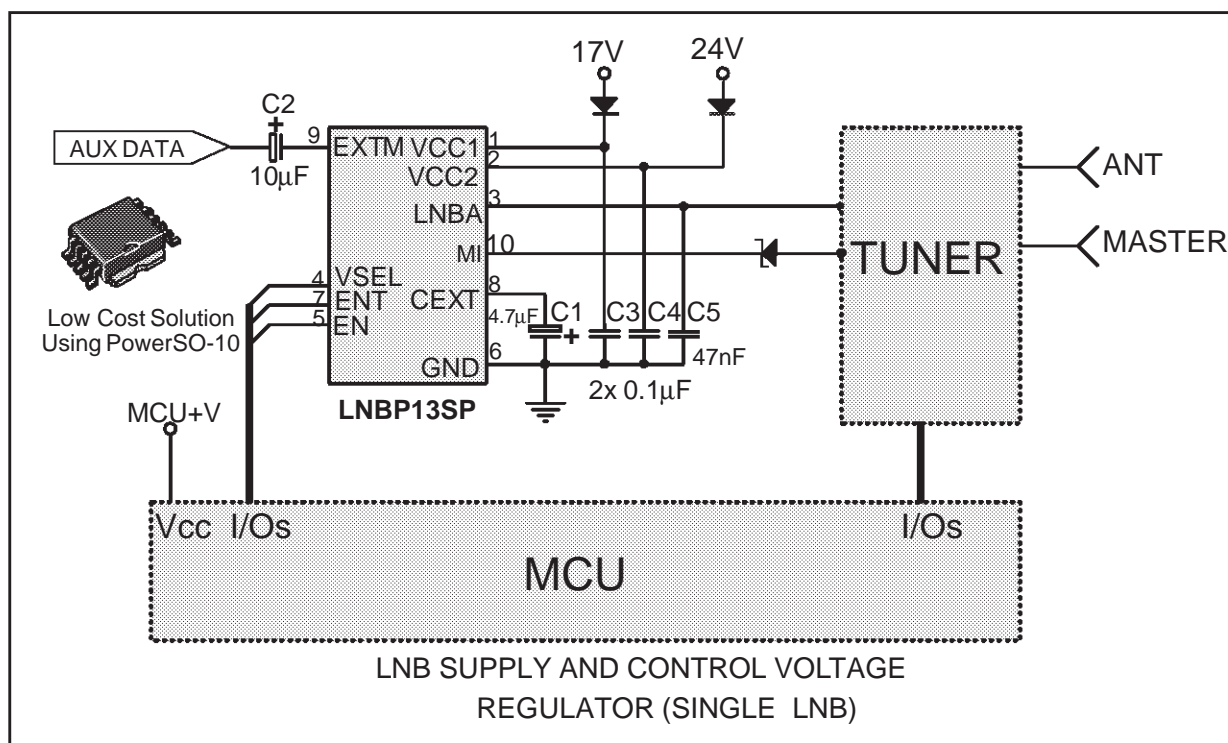


Figure 29: Single Antenna Receiver Overload Diagnostic

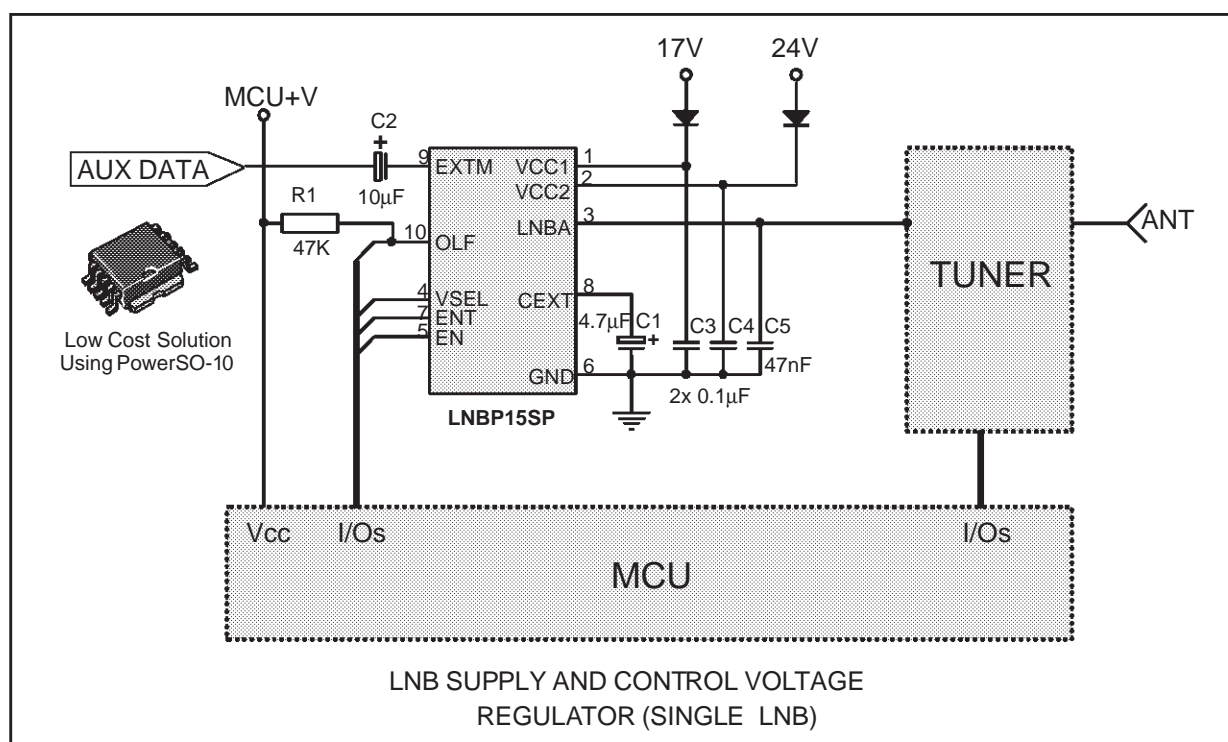

Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specification mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

The ST logo is a trademark of STMicroelectronics

© 2000 STMicroelectronics - Printed in Italy - All rights reserved

STMicroelectronics GROUP OF COMPANIES

Australia - Brazil - China - Finland - France - Germany - Hong Kong - India - Italy - Japan - Malaysia - Malta - Morocco - Singapore - Spain - Sweden - Switzerland - United Kingdom - U.S.A.

<http://www.st.com>