



# AN1304 APPLICATION NOTE

## USING THE TD340 : H-BRIDGE DRIVER FOR DC-MOTOR CONTROL

by J-F GARNIER

### INTRODUCTION

The TD340 is a quad N-Channel Power MOSFET Driver suitable for DC-Motor control. TD340 main features are:

- ☐ Speed and direction control
- ☐ Internal charge pump for high side drive
- ☐ Overvoltage and undervoltage protection
- ☐ Synchronous rectification
- ☐ Active reverse battery protection
- ☐ Inaudible 25kHz PWM frequency
- ☐ Standby mode
- ☐ Integrated 5V regulator for  $\mu$ C supply
- ☐ Integrated reset and watchdog circuits

This note presents some application hints:

- ☐ Zero current standby mode,
- ☐ Current limitation,
- ☐ Autoprotected H-bridge.

### ZERO CURRENT STANDBY

In some application, the standby current of the TD340 (180 $\mu$ A typ.) is still too high regarding the requirement. To achieve a true zero current standby mode, the schematic shown on figure 1


can be used by the means of only two lost cost bipolar transistors.

When the system is idle, transistor Q3 blocks the supply voltage. When the user press the command switch SW1, Q3 is activated and provides the power supply to the TD340. The  $\mu$ C wakes up and locks the supply by switching on transistor Q4. SW1 should be maintained long enough to allow the TD340 to start and the  $\mu$ C to wakeup, this time depends on the configuration and is usually about 100 ms. When the task is complete, Q4 is switched off by the  $\mu$ C (in the meantime, SW1 has been released), and Q3 returns to the off state.

TD340 standby mode is no more used and the STBY pin is wired to 5V (VOUT pin)

To improve the reliability of the system during power up and down, resistors can be added on the gates of the lower MOSFETs to ensure that the bridge remains off. Pull-down resistors must not be used on upper MOSFET gates, because the charge pump is not able to provide the necessary current.

Figure 1 : Zero Current Standby Circuit

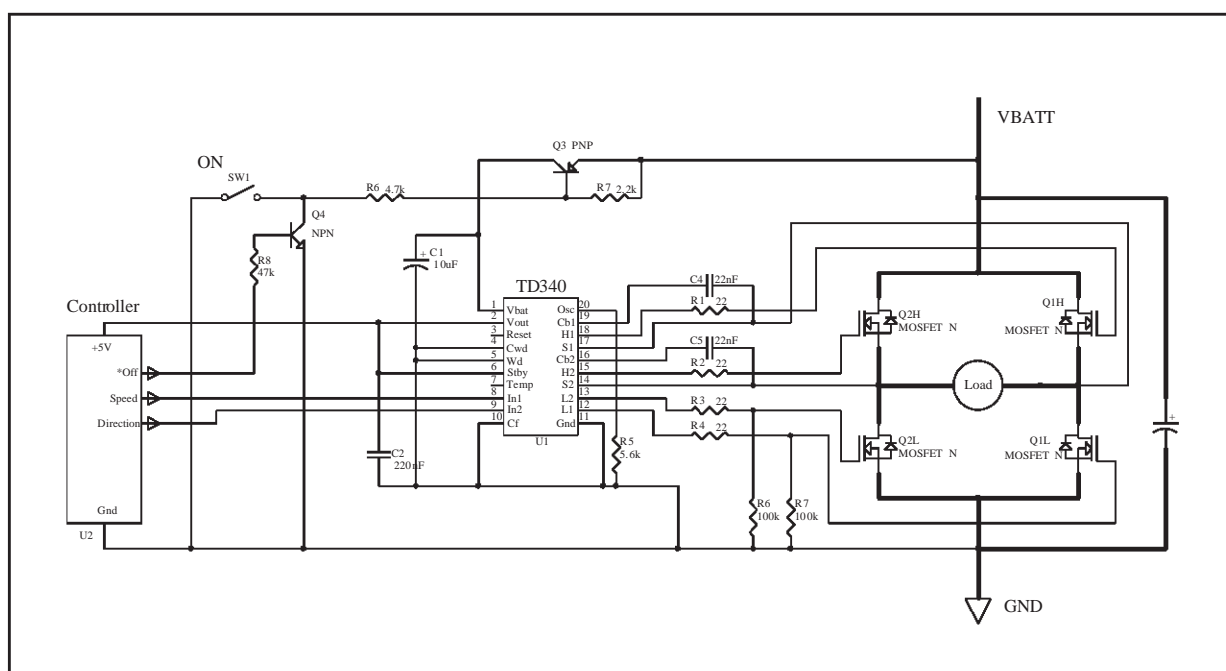

Many applications need to limit the maximum current through the load. Limiting the current through a motor actually limits the torque. Figure 3 shows a solution using a TS922A, a dual low offset (0.9mV), rail-to-rail op-amp. This scheme can be used with analog or digital IN1 mode.

Op-amp U3A is used to amplify the voltage  $V_{\text{sense}}$  across the shunt resistor. Voltage at the output of U3A is:

Op-amp U3B is used as a comparator. The

$$V_{ref} = 5V * R_{12}/(R_{11}+R_{12}).$$

The output of the comparator is also used to tell the microcontroller that an overcurrent event has occurred. The microcontroller can then lower the PWM level.


For a full discussion and other methods, see Application Note AN1305: Current Measurement and Limitation in TD340 Based Motor Control Systems.

### AUTOPROTECTED H-BRIDGE

Instead of using a current limiting circuit, an autoprotected full bridge can be built with two OMNIFETs. These devices, part of the ST VIPower family, provide current limiting and thermal shunt-down. OMNIFETs can be used as standard MOSFETs with the exception of a small current in the gate input. Therefore, they should be used only for low side. MOSFETs in high side should be rated to higher currents, so the

protection against overcurrent and overtemperature is provided by the OMNIFETs. Figure 3 illustrates an application of these devices. OMNIFETs VND14NV04 limit the current to 14A maximum, and the upper MOSFETs STD30NE06L (30A) are protected. Note that resistor bridge are used for driving the OMNIFETs, due to their lower gate voltage capability.

**Figure 3 :** Autoprotected H-bridge

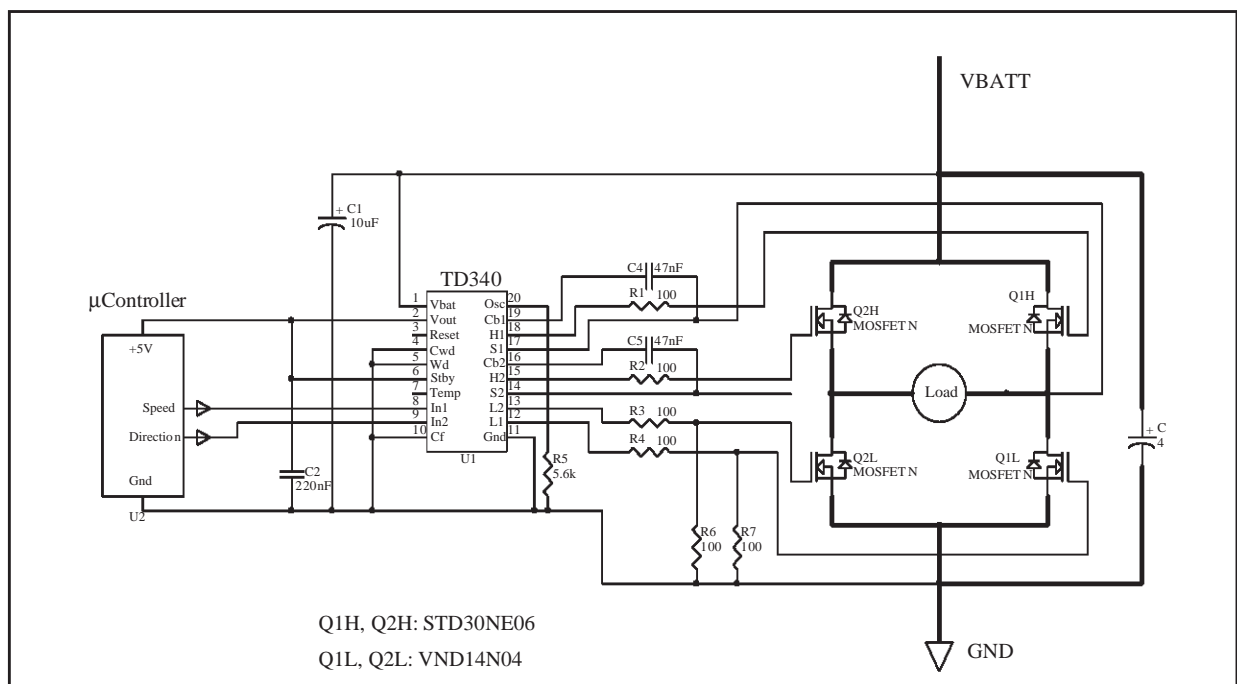

Information furnished is believed to be accurate and reliable. However, STMicroelectronics assumes no responsibility for the consequences of use of such information nor for any infringement of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of STMicroelectronics. Specifications mentioned in this publication are subject to change without notice. This publication supersedes and replaces all information previously supplied. STMicroelectronics products are not authorized for use as critical components in life support devices or systems without express written approval of STMicroelectronics.

© The ST logo is a registered trademark of STMicroelectronics

© 2000 STMicroelectronics - Printed in Italy - All Rights Reserved  
STMicroelectronics GROUP OF COMPANIES

Australia - Brazil - China - Finland - France - Germany - Hong Kong - India - Italy - Japan - Malaysia - Malta - Morocco  
Singapore - Spain - Sweden - Switzerland - United Kingdom

© <http://www.st.com>