
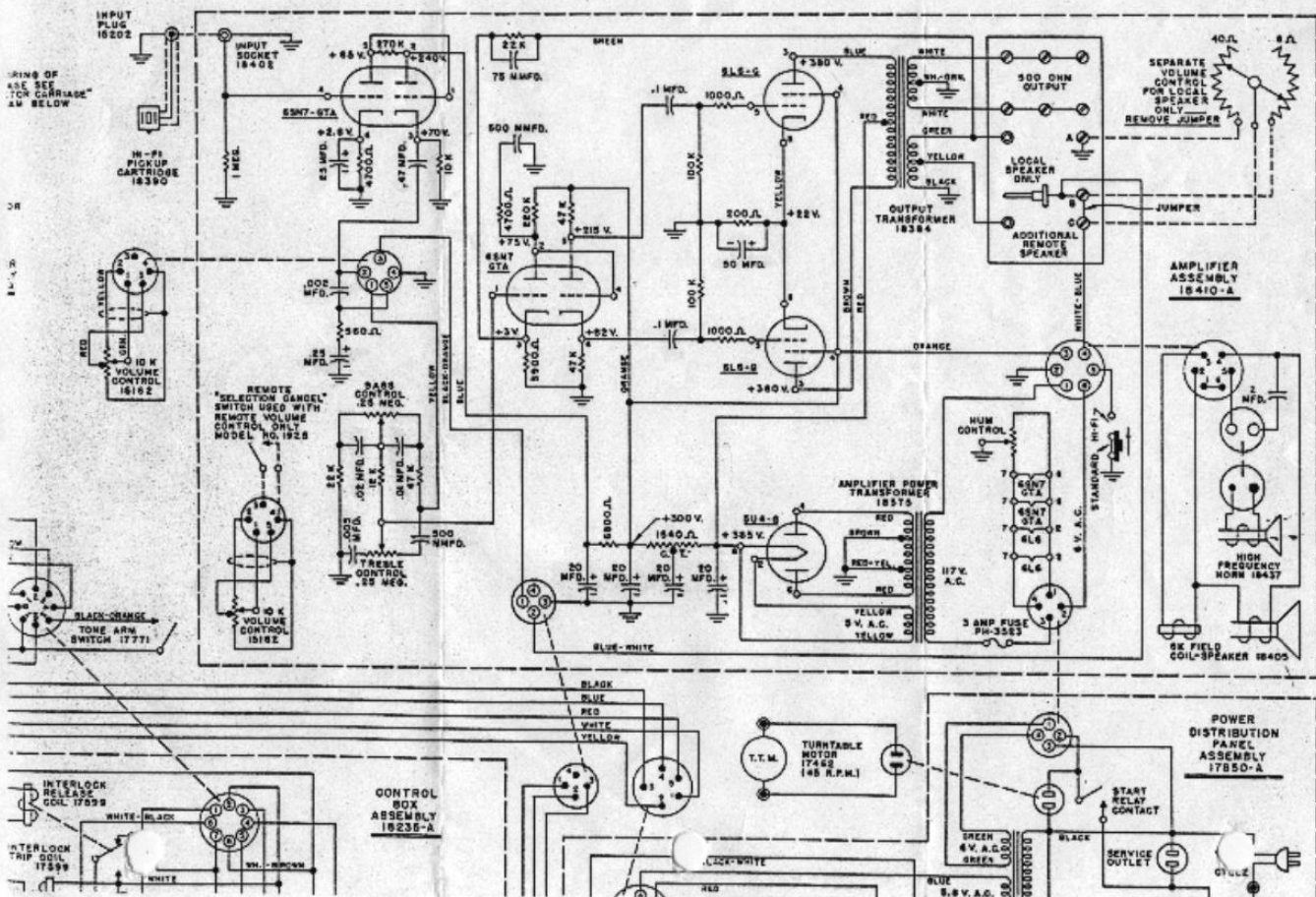


URING OF
AGE SEE
TOR CARRAGE
AM BELOW

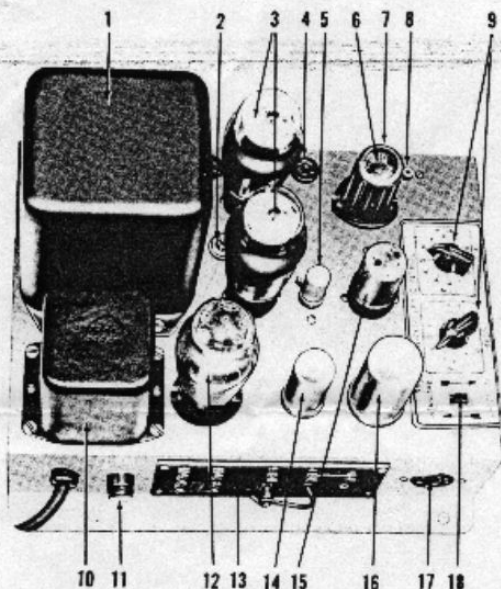

Rockola 1442

No. 18422-A Amplifier Assembly (Less Tubes)




Part No.	Description
1 18375	Power Transformer
2 18411	Hum Control
3 PH-3191	6L6 Tube
4 17275	Miniature 5 Prong Socket
5 18436	Stande Resistor
6 12546	6 SN7 Tube
7 18412	Tube Shield
8 18402	Input Socket
9 11578	Pointer Knob
10 18384	Output Transformer
11 PH-3523	3 Amp. Fuse
12 PH-3190	5U4 Tube
13 12769	Speaker Terminal Strip
14 16924	Input Capacitor {20 mfd. 475v.
15 12546	6 SN7 Tube
16 16926	Filter Capacitor {20 mfd. 475v.
17 18414	6 Prong Socket {20 mfd. 475v.
18 18403	Slide Switch

No. 18422-A Amplifier Assembly (Less Tubes)


Part No. Description

1 13320	1 Megohm Resistor
2 13010	270,000 Ohm Resistor
3 17788	.47 Mfd. 200 V. Condenser
4 16223	10,000 Ohm Resistor
5 18420	.002 Mfd. 400 V. Condenser
6 15204	25 Mfd. Condenser
7 18399	.1 Mfd. 600 V. Condenser
8 16228	100,000 Ohm Resistor
9 16224	1,000 Ohm Resistor
10 16925	Filter Resistor
11 11555	Fuse Holder
12 16228	100,000 Ohm Resistor
13 18399	.1 Mfd. 600 V. Condenser
14 PH-3177	50 Mfd. 50 V. Condenser
15 16222	6800 Ohm Resistor
16 18409	Tone Control
17 18439	12,000 Ohm Resistor
18 18409	Tone Control
19 18418	.0056 Mfd. 400 V. Condenser


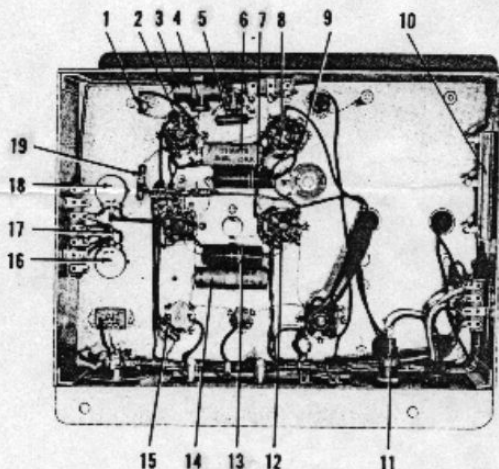


Rock-Ola model 1442 jukebox amplifier

Manufactured in 1954

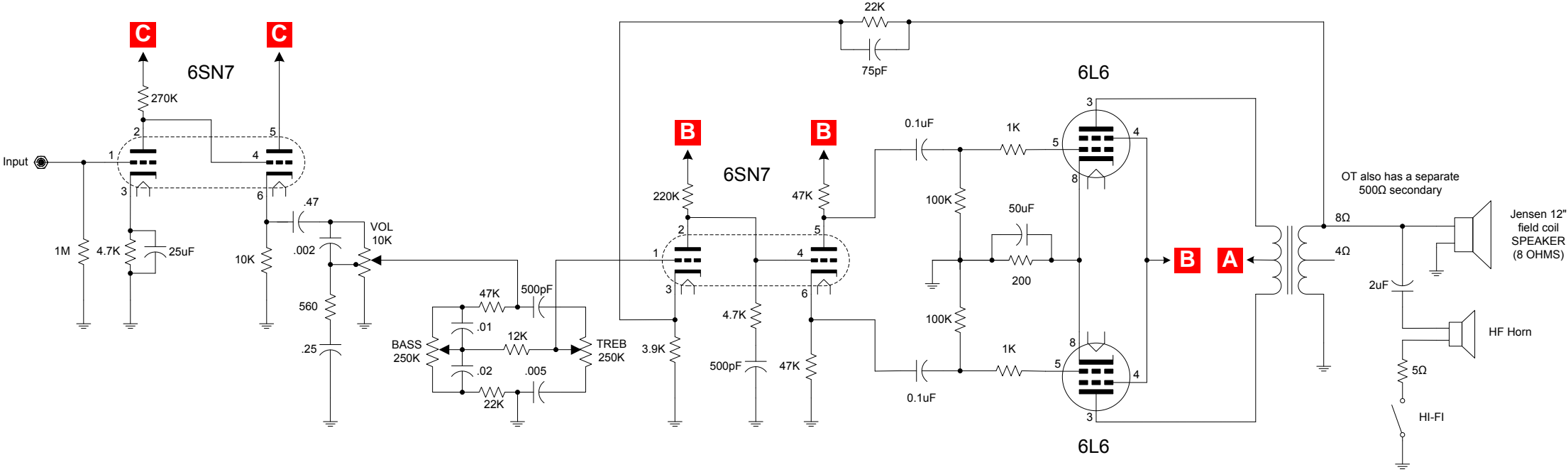

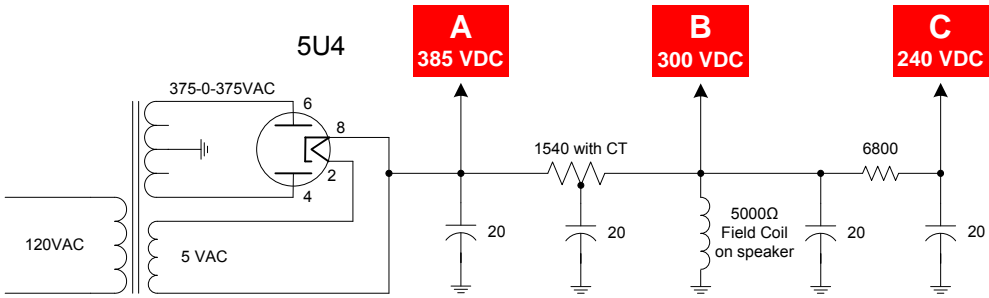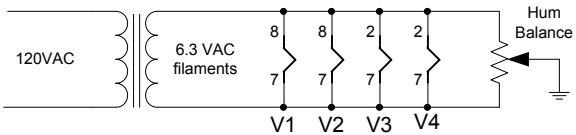This transformer is located on a separate control chassis. It has multiple secondaries that power various other circuits inside the jukebox. The 6.3VAC winding is used only to power the amplifier tube filaments.



This simplified schematic is electrically correct, but has purposefully omitted interconnection plugs and jacks to make the schematic easier to understand. The AC primary circuit, fuses, switches, relays, etc. have been omitted for the same reason.

Rock-Ola Model 1442 Jukebox Amplifier Conversion

Conversion by Steve Luckey, 08/20/09

