

Overview


The LA9410 final audio output IC for laser disk players has an internal input amplifier for the 1-bit DAC, 40 kHz LPF, digital/analog signal select circuit, output mute, volume circuit, mixing amplifier and limitter circuit for RF output, and voltage regulator for plus and minus power supply. It provides a compact implementation of audio output circuitry for LD and CD compatible players and laser karaoke systems.

Functions

- · Input amplifier for 1-bit DAC, LPF
- Input signal select (digital/analog audio)
- Output mute
- Volume circuit (for headphone amplifier. No headphone drive output amplifier is provided)
- . Mixing amplifier for RF output (with internal limitter circuit)
- Regulated power supply circuit (internal use only. Cannot be output to external circuits)


Features

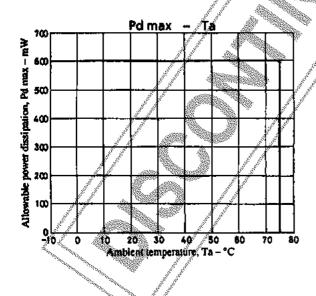- Provides compact implementation of LD player output circuits
- . Suitable for 1-bit DAC
- Internal voltage regulator allows direct use of non-regulated power supply
- Package: DIP-28S



Package Dimensions 3063

unit: mm

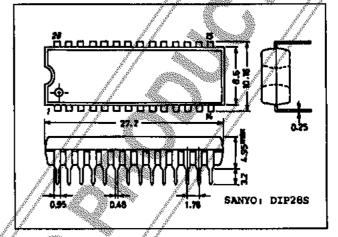


Specifications

Pin 19 threshold voltage

opeomeations						
Maximum Ratings at Ta = 25	° C			unit		
Maximum Supply Voltage	V _{CC} max	(IC only, V _{CC} -V _{BE})	14	V		
Allowable power dissipation	Pd max		600	m₩		
Operating temperature	Topr		-10 to +75	•€		
Storage temperature	Tstg		-40 to +150	•Ç/(`	N. idilaha	
Operating Conditions at Ta	= 25° C			polt	Printer Street, Street	
Recommended Supply Voltage	Vaup	(For use in application circuit)	±14	/ N	The state of the s	Silver Control of the
Power supply voltage operating range	Vsup op	(For use in application circuit)	±11 to ±18	/ / V /		Sell Market Fred
Reference output voltage	Vr		2 /	∕ Vrm∎		
Operating Characteristics at	Ta = 25°0	C, Vrup = ±14V, Vi= 2Vrms = 0d	B, 1kHz, R 🚑	10kΩ, Ve	ont = 0V	Jane Barrell
-			/min	CYP	max	Minit
Quiescent supply current	Icco	No signal	±17	±21	±25	/mA
Line output level / digital	Vod	Digital input, line output	### ## -1 .	a	-1 / s	/ dB
Line output level / analog	Von	Analog input, line output	// -1	0	+4	dB
Volume output level	VRo	Volume input/output			43	₫₿
Mixing output level	VMo	Volume input, Mixed output for L&R.	//5	-3	/ ² / ₂ -1	dB
		in-phase input			<i>.</i>	_
Line frequency response / digital 1	Fl	Digital input, -20dB, 20kHz/lkHz, line of	output O	0.7	1.5	dB
Line frequency response / digital 2	F2	Digital input, -20dB, 40kHz/1kHz, line (output 0	2.5	5	dB
Muting ratio	Mr	Digital input, line output	90	/เม่ง		dB
Volume attenuation fevel 1	VRrI	Volume input/output, Vcont = 1V	-15.5	-12.5	-9.5	dB
Volume attenuation level 2	VRr2	Volume input/output, Vcont =5V		⁰ ∕ -58	-50	dB
Signal/noise ratio digital	S/N1	Digital input mode, 20kHz/LPF, time of	atput 86	99		₫₿
Signal/noise ratio analog	S/N2	Analog input mode, 20kHz/LPF, line of	utput B6	99		dB
Channel separation	Sep	Digital input, line output	86	96		dB
Crosstalk	Cr	Digital input mode, line output	// 86	98		₫B
Total harmonic distortion (digital 1)	THD1	1kHz, OdB, Digital input, line output	AND STATE OF THE S	0.005	0.009	%
Total harmonic distortion (digital 2)	THD2	10kHz, -10dB, Digital Input, line outp	ut <i>} /</i> /	0.02	0.07	%
Total harmonic distortion (analog)	THD3	1kHz, OdB, Analog input, line output	86 86 ut	0.008	0.03	96
Line output offset voltage	Voff	Digital input mode, line output	_ 5 0	0	+50	mV
Pin 18 threshold voltage	Vth18		1.5	2.1	3	v
_		- 8° 8° - 38% - 7888 - 3° 8°				


Note: Unless otherwise specified, a 400Hz to 30kHz bandpass filter is used.

Vth19

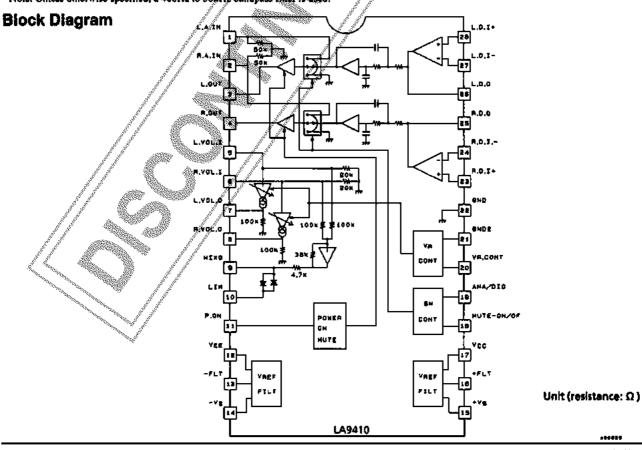

1.5


2.1

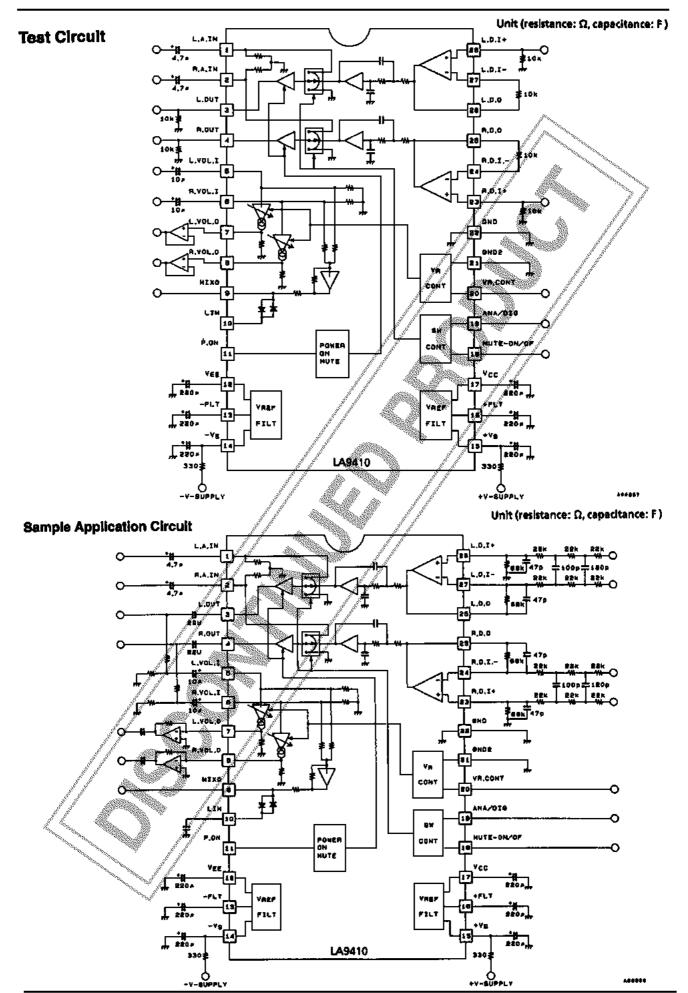

Technical information

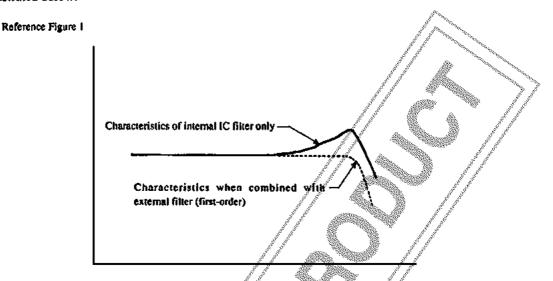1. Internal digital input filter

The filter internal to the LA9410 is designed to form a third-order filter when used in combination with an external first-order filter. Characteristics when used alone and when used in conjunction with the external filter are illustrated below.



External components for input circuit for 1-bit DAC

The LA9410 circuit is directly connected from the input to line output. If the differential of the external components used for the input circuit (differential input) of the 1-bit DAC is large, it will become a DC offset, and may cause popping noise during selection and muting.

3. Power supply

In the LA9410 the IC is protected from high voltage inputs by series resistors located in the power supply, and voltage regulator circuits in the IC. This means that IC current dissipation will be strongly affected by supply voltage and the series resistance. Power supply design requires sufficient leeway so that the allowable power dissipation of the IC is not exceeded.

Note: Use a series resistance in the power supply so that the IC current dissipation is 38mA or less.

4. Measurement of separation and crosstalk

The effects of the IC evaluation circuit board pattern may make accurate measurement of crosstalk and separation impossible. This is especially common when the peripheral resistor of the 1-bit DAC input circuit has a high resistance.

- No products described or contained herein are intended for use in surgical implants, life-support systems, aerospace equipment, nuclear power control systems, vehicles, disaster/orime-prevention equipment and the like, the failure of which may directly or indirectly cause injury, death or property loss.
- Anyone purchasing any products described or contained herein for an above-mentioned use shall;
 - O Accept full responsibility and indemnify and defend SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors and all their officers and employees, jointly and severally, against any and all claims and litigation and all damages, cost and expenses associated with such use:
 - Not impose any responsibility for any fault or negligence which may be cited in any such claim or litigation on SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors or any of their officers and employees jointly or severally.
- Information (including circuit diagrams and circuit parameters) herein is for example only; it is not guaranteed for volume production. SANYO believes information herein is accurate and reliable, but no guarantees are made or implied regarding its use or any infringements of intellectual property rights or other rights of third parties.