

PWM SWITCHER & LINEAR CONTROLLER IC

FEATURES

- LDO Controller allows the use of a low cost pass transistor for the I/O supply
- 8-pin SOIC combines switching and linear controller
- Internal pre-regulator eliminates cross talk between switching and linear regulators
- Automatic shut down of the linear regulator when connected to the Vcc2 detect pin
- On-board MOSFET driver
- Fastest transient response of any controller method. (0 to 100% Duty Cycle in 100nS)
- 1% internal voltage reference
- Internal undervoltage lockout protects MOSFET during start-up


APPLICATIONS

- Dual supply low voltage processor applications, such as: P55CTM, CYRIX M2TM, POWER PCTM and AMD K6TM
- Simple 5V to 3.3V switcher for Pentium with AGP or Pentium II™ applications

DESCRIPTION

The IRU3033 IC combines a switching controller and a linear regulator controller all in a compact 8-pin surface mount package, providing a total solution for dual supply processor applications such as an Intel P55C™, AMD K6™, as well as Cyrix 6X86L™ and the M2™ processors. Typically in these applications a dual supply regulator converts 5V to 3.3V for I/O supply and a jumper programmable supply of 1.25V to 3.5V for CORE supply. The linear regulator controller portion in the IRU3033 is a programmable controller allowing flexibility for the I/O regulator and has a minimum of 50mA drive current capability designed to provide ample current for an external pass transistor. The IC uses an internal regulator generated from the 12V supply to power the controller as well as the 12V supply to drive the power MOSFET, allowing a low cost N-channel MOSFET switch to be used. The IC also includes an error comparator for fast transient response, a precise voltage reference for setting the output voltage as well as a direct drive of the MOSFET for the minimum part count.

TYPICAL APPLICATION

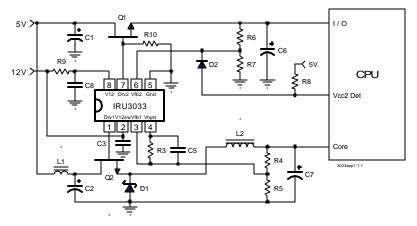

Typical application of IRU3033 in a flexible mother board designed for Intel P55™, P54™, AMD K5, K6™ as well as Cyrix M1™ and M2™ applications

Notes: P54C, P55C, Pentium II are trademarks of Intel Corp. K5 & K6 are trademarks of AMD Corp. Cyrix 6X86L, M1 ,M2 are trademarks of Cyrix Corp. Power PC is trademark of IBM Corp.


PACKAGE ORDER INFORMATION

TA (°C)	8-PIN PLASTIC SOIC (S)
0 TO 70	IRU3033CS

ABSOLUTE MAXIMUM RATINGS

V12,V12SW Supply Voltages20VF.B Pin Voltages-0.3V to 5VStorage Temperature Range-65 TO 150°COperating Junction Temperature0 TO 150°C

PACKAGE INFORMATION

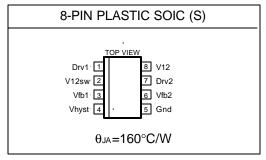

ELECTRICAL SPECIFICATIONS

Unless otherwise specified the following specification applies over $V_{12}=V_{12SW}=12V$, and $T_A=0$ to $70^{\circ}C$. Low duty cycle pulse testing are used which keeps junction and case temperatures equal to the ambient temperature.

Linear Controller Section

Ellicar Controller Cotton						
PARAMETER	SYM	TEST CONDITION	MIN	TYP	MAX	UNITS
F.B Voltage Initial Accuracy	V _{FB2}	T _J =25°C, Drv2=V _{FB2} , C _L =100μF	1.237	1.250	1.262	V
F.B Voltage Total Variation		Drv2=V _{FB2} , C _L =100μF	1.225	1.250	1.275	V
F.B Voltage Line Regulation		10 <v<sub>12<14V,Drv2=V_{FB2}, C_L=100μF</v<sub>		0.2		%
F.B Input Bias Current	FB2	V _{FB2} =1.25V	-1		+1	μΑ
Maximum Drive Current	DRVMAX	V _{FB2} =1V, V _{FB1} =1.5V		50		mA
V ₁₂ Supply Current	I ₁₂	VFB2 =1V, VFB1 =1.5V, IDRV2=0		5		mA

Switching Controller Section						
PARAMETER	SYM	TEST CONDITION	MIN	TYP	MAX	UNITS
F.B Voltage Initial Accuracy	V _{FB1}	T _J =25°C	1.237	1.250	1.262	V
F.B Voltage Total Variation			1.225	1.250	1.275	V
F.B Voltage Line Regulation				0.2		%
F.B Input Bias Current	FB1	V _{FB1} =1.25V	-1		+1	μΑ
Min On Time		V _{FB1} is sq wave with 300 ns on		800		nS
		time and 2µS off time				
Min Off Time		V _{FB1} is sq wave with 300 ns off		800		nS
		time and 2µS on time				
Vhyst pin output-HI		Isource =500μA, V _{FB1} =1.5V	11			V
Vhyst pin output-LO		Isink =500µA, Vfb1 =1V			1	V
Supply Current	I _{12SW}	V _{FB1} =1V, V _{FB2} =1.5V		10		mA
Maximum Duty Cycle	DMAX	V _{FB1} =1V			100	%
Minimum Duty Cycle	DMIN	V _{FB1} =1.5V	0			%
Gate Drive Rise/Fall Time	VGATE	Load=IRL3303		70		nS

4-78

Rev. 1.5
1/14/99

PIN DESCRIPTIONS

PIN#	PIN SYMBOL	PIN DESCRIPTION
3	V _{FB1}	A resistor divider from this pin to the output of the switching regulator and ground sets the
		Core supply voltage.
6	V _{FB2}	The feedback pin of the linear regulator. A resistor divider from this pin to the output of the
		linear regulator and ground sets the I/O supply voltage.
7	Drv2	The drive pin of the linear regulator. This pin controls the base of a transistor or the gate
		of a MOSFET acting as the series pass element for the linear regulator.
5	Gnd	This pin is connected to the IC substrate and must be connected to the lowest potential
		in the system.
1	Drv1	The PWM output of the switching controller. This pin is a totem pole drive that is con-
		nected to the gate of the power MOSFET. A resistor may be placed from this pin to the
		gate in order to reduce switching noise.
4	VHYST	A resistor and a 10pF capacitor is connected from this pin to the V _{FB1} pin to set the
		output ripple voltage for the switching regulator.
2	V _{12SW}	This pin supplies the voltage to the PWM drive and hysterises circuitry and it is con-
		nected to the 12V supply. A 1μF, high frequency capacitor must be connected from this
		pin to ground to provide the peak current for charging and discharging of the MOSFET.
8	V ₁₂	This pin provides the biasing for the chip and drive for the linear regulator controller. It is
		connected to 12V supply. A 10 ohm resistor in series from this pin to the 12V supply and
		a 1μF, high frequency capacitor connected from this pin to Gnd is required to filter the
		switching noise of the switching regulator.

BLOCK DIAGRAM

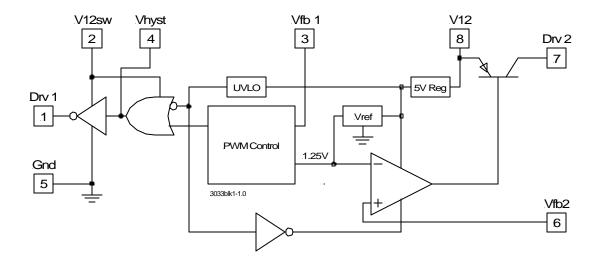


Figure 1 - Simplified block diagram of the IRU3033

TYPICAL APPLICATION

Pentium Dual Supply Application

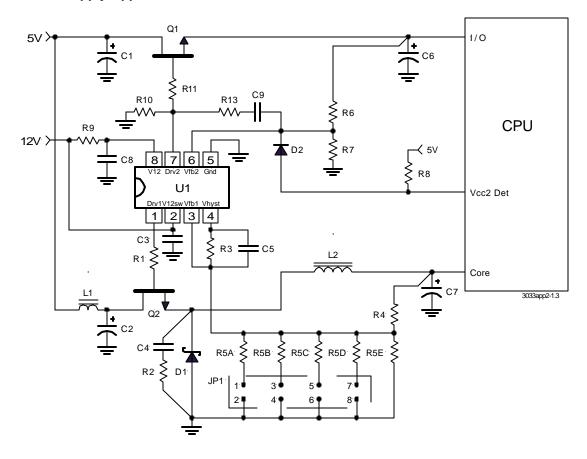


Figure 2- Typical application of IRU3033 in a flexible motherboard with the 4 bit VID output voltage selection. This circuit uses a single jumper that programs the output voltage in 16 steps with 0.1V steps from 2V to 3.5V, designed for Intel P55™, P54™, AMD K5 & K6™ as well as Cyrix M1™ and M2™ applications. The Vcc2Det pin automatically shuts down the I/O regulator when a single plane processor is dropped in the socket.

JP1	JP1	JP1	JP1	Output	
1-2	3-4	5-6	7-8	Voltage	
0	0	0	0	3.5	
0	0	0	1	3.4	
0	0	1	0	3.3	
0	0	1	1	3.2	
0	1	0	0	3.1	
0	1	0	1	3.0	
0	1	1	0	2.9	
0	1	1	1	2.8	
1	0	0	0	2.7	
1	0	0	1	2.6	
1	0	1	0	2.5	
1	0	1	1	2.4	
1	1	0	0	2.3	
1	1	0	1	2.2	
1	1	1	0	2.1	0 = Jumper block is installed.
1	1	1	1	2.0	1 = Jumper block is not installed.

4-80 Rev. 1.5

Pentium Dual Supply Application Parts List

Ref Desig	Description	Qty	Part #	Manuf
U1	LDO/Switcher IC	1	IRU3033CS (8-pin SOIC)	IR
Q1	MOSFET	1	MTP3055 (TO-220)	Motorola
Q2	MOSFET	1	IRL3303 (TO-220)	IR
			IRL3103S (TO-263) (note 1)	
D2	Diode, GP	1	1N4148	
D1	Schottky Diode	1	MBR1045CT (TO-220)	
			MBRB1545CT (TO-263) (note1)	Motorola
L2	Inductor	1	Core: T50-18, L=4μH	Micro Metal
			Turns: 10T, 18 AWG	(core)
L1	Inductor	1	L=2μH	
R1	Resistor	1	22 ohm, 5%, SMT 1206 size	
R2	Resistor	1	10 ohm, 5%, SMT 1206 size	
R3	Resistor	1	324 kohm, 1%, SMT 0805 size	
R4A *	Resistor	1	806 ohm, 1%, SMT 0805 size	
R4B *	Resistor	1	90.9 kohm, 1%, SMT 0805 size	
R5A	Resistor	1	1.24 kohm, 1%, SMT 0805 size	
R5B	Resistor	1	2.49 kohm, 1%, SMT 0805 size	
R5C	Resistor	1	4.99 kohm, 1%, SMT 0805 size	
R5D	Resistor	1	1 kohm, 1%, SMT 0805 size	
R5E	Resistor	1	1.30 kohm, 1%, SMT 0805 size	
R6	Resistor	1	2 kohm, 1%, SMT 0805 size	
R7	Resistor	1	1.21 kohm,1%, SMT 0805 size	
R8	Resistor	1	1 kohm, 5%, SMT 0805 size	
R9	Resistor	1	10 ohm, 5%, SMT 0805 size	
R10	Resistor	1	1k ohm, 5%, SMT 0805 size	
R11	Resistor	1	2.4k ohm, 5%, SMT 0805 size	
R13	Resistor	1	7.5k ohm, 5%, SMT 0805 size	
C1	Capacitor	1	6MV1500GX, 1500μF, 6.3V, Elect	
C2	Capacitor	1	6MV1500GX, 1500μF, 6.3V, Elect	Sanyo
C3	Capacitor	1	1μF, Ceramic, SMT 0805 size	
C4	Capacitor	1	470pF, Ceramic, SMT 0805 size	Sanyo
C5	Capacitor	1	10pF, Ceramic, SMT 0805 size	Sanyo
C6	Capacitor	1	6MV1500GX, 1500μF, 6.3V, Elect	Sanyo
C7	Capacitor	4	6MV1500GX, 1500μF, 6.3V, Elect	Sanyo
C8	Capacitor	1	1μF, Ceramic, SMT 0805 size	
C9	Capacitor	1	470p, Ceramic, SMT 0805 size	
HS1	Heat Sink	1	For MOSFET, 577002	Aavid
HS2	Heat Sink	1	For Schottky Diode , 577002	Aavid
HS3	Heat Sink	1	For Q1, 507222 (I/O curren<5A)	Aavid
			576602 (I/O current< 3.5A)	

 * R4 is a parallel combination of R4A and R4B Note 1: For the applications where it is desirable to eliminate the heat sink, the IRL3103S for Q2 and MBR1545CT for D2 in TO-263 packages with minimum of 1" square copper pad can be used.

TYPICAL APPLICATION

5V to 3.3V for Pentium Application with AGP or Pentium II Application without ATX power supply Dual mode Operation between Switching or Linear mode.

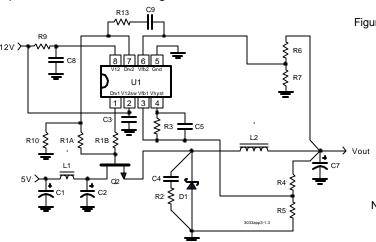


Figure 3 - This unique application of IRU3033 allows the designer to switch between Linear or Switching mode of operation using a single IC. This circuit has the flexibility to be used for low current operation in Linear mode for cost reasons and yet be able to operate in the Switching mode if the load current increases and the heat generated by the Linear operation will be an issue. Table below describes the components that will be effected for the two modes of operation.

Note 1: For the applications where it is desirable to eliminate the heat sink, the IRL3103S for Q2 and MBR1545CT for D2 in TO-263 packages with minimum of 1" square copper pad can be used.

Mode of Operation	L1	L2	D1	C4	C5	R1A	R1B	R2	R3	R4	R5	R6	R7
Switching	V	٧	V	V	٧	0	V	V	V	V	V	V	0
Linear	S	S	0	0	0	V	0	0	0	V	0	V	V

V = See parts list for value	S = Short	$\Omega = \Omega nen$
v – See Dails list for value	3 – SHUL	

Ref Desig	Description	Qty	Part #	Manuf
U1	LDO/Switcher IC	1	IRU3033CS (8-pin SOIC)	IR
Q2	MOSFET	1	IRL3303 (TO-220)	IR
			IRL3103S (TO-263) (note 1)	
D1	Schottky Diode	1	MBR1045CT (TO-220)	
			MBRB1545CT (TO-263) (note1)	Motorola
L2	Inductor	1	Core:T50-18,L=4μH	Micro Metal
			Turns: 10T, 18 AWG	(core)
L1	Inductor	1	L=2µH	
R1A	Resistor	1	2.4k ohm, 5%, SMT 1206 size	
R1B	Resistor	1	22 ohm, 5%, SMT 1206 size	
R2	Resistor	1	10 ohm, 5%, SMT 1206 size	
R3	Resistor	1	249 kohm, 1%, SMT 0805 size	
R4	Resistor	1	1 kohm, 1%, SMT 0805 size	
R5	Resistor	1	576 ohm, 1%, SMT 0805 size	
R6	Resistor	1	180 ohm, 1%, SMT 0805 size	
R7	Resistor	1	100 ohm, 1%, SMT 0805 size	
R9	Resistor	1	10 ohm, 5%, SMT 1206 size	
R10	Resistor	1	1k ohm, 5%, SMT 1206 size	
R13	Resistor	1	7.5k ohm, 5%, SMT 1206 size	
C1,2	Capacitor	2	6MV1500GX, 1500μF, 6.3V, Elect	Sanyo
C3	Capacitor	1	1μF, Ceramic, SMT 0805 size	
C4	Capacitor	1	470pF, Ceramic, SMT 0805 size	Sanyo
C5	Capacitor	1	10pF, Ceramic, SMT 0805 size	Sanyo
C7	Capacitor	1	6MV1500GX, 1500uF, 6.3V, Elect	Sanyo
C8	Capacitor	1	1μF, Ceramic, SMT 0805 size	
C9	Capacitor	1	470pF, Ceramic, SMT 0805 size	
HS1	Heat Sink	1	For MOSFET in Switching mode, 577002	Aavid
			For MOSFET in Linear mode:	
			507222 (3.3V current<5A),	
			576602 (3.3V current< 3.5A)	
HS2	Heat Sink	1	For Schottky Diode, 577002	Aavid

4-82 Rev. 1.5

TYPICAL APPLICATION

5V to 3.3V for Pentium application with AGP or Pentium II application without ATX power supply switching mode operation

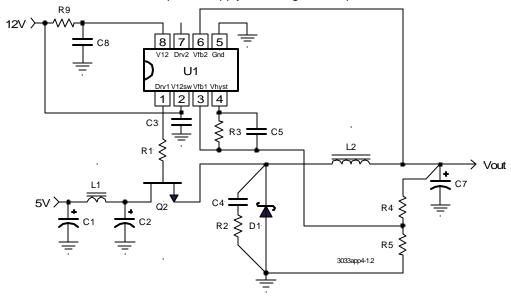


Figure 4 - The circuit in figure 4 is the application of the IRU3033 in a switching mode only. This circuit can be used to generate a low cost 5V to 3.3V for either Pentium application with AGP socket or in Pentium II applications where it is desirable to generate an accurate on board 3.3V supply.

Ref Desig	Description	Qty	Part #	Manuf		
U1	LDO/Switcher IC	1	IRU3033CS (8-pin SOIC)	IR		
Q2	MOSFET	1	IRL3303 (TO-220)	IR		
			IRL3103S (TO-263) (note 1)			
D1	Schottky Diode	1	MBR1045CT (TO-220)			
			MBRB1545CT (TO-263) (note1)	Motorola		
L2	Inductor	1	Core: T50-18,L=4μH	Micro Metal		
			Turns: 10T, 18 AWG	(core)		
L1	Inductor	1	L=2μH			
R1	Resistor	1	22 ohm, 5%, SMT 1206 size			
R9	Resistor	1	10 ohm,5%, SMT 0805 size			
R2	Resistor	1	10 ohm, 5%, SMT 1206 size			
R3	Resistor	1	249 kohm, 1%, SMT 0805 size			
R4	Resistor	1	1 kohm, 1%, SMT 0805 size			
R5	Resistor	1	576 ohm, 1%, SMT 0805 size			
C1,2	Capacitor	2	6MV1500GX, 1500μF, 6.3V, Elect	Sanyo		
C3	Capacitor	1	1μF, Ceramic, SMT 0805 size			
C4	Capacitor	1	470pF, Ceramic, SMT 0805 size	Sanyo		
C5	Capacitor	1	10pF, Ceramic, SMT 0805 size	Sanyo		
C7	Capacitor	1	6MV1500GX, 1500μF, 6.3V, Elect			
C8	Capacitor	1	1μF, Ceramic, SMT 0805 size			
HS1	Heat Sink	1	For MOSFET, 577002 Aavid			
HS2	Heat Sink	1	For Schottky Diode, 577002	Aavid		

Note 1: For the applications where it is desirable to eliminate the heat sink, the IRL3103S for Q2 and MBR1545CT for D2 in TO-263 packages with minimum of 1" square copper pad can be used.

APPLICATION INFORMATION

Introduction

The IRU3033 device is an application specific product designed to provide an onboard dual supply for the new generation of microprocessors requiring separate Core and I/O supplies. One of the processors fitting this requirement is the new Intel P55C™ multimedia microprocessor. Intel specifies a Core voltage of 2.8V nominal (±100mV max) with maximum Core supply current of 6A while the I/O supply is set for 3.3V with a maximum I/O current of 0.65A. However, in most applications the I/O regulator also provides the voltage for other IC functions such as the chipset, cache, etc. Typically a low cost solution such as a Low Dropout (LDO) Linear Regulator is selected to provide the I/O supply with the maximum designed current of 3A, keeping the power dissipation and the heat sink to a reasonable size. The Core supply regulator, however, if also selected to be a linear regulator, will be dissipating a maximum of 12.6W [(5V-2.8V)X5.7A] of power, which requires a substantial amount of heat sinking and perhaps forced air cooling in order to keep it operational. Some manufacturers suggest using two regulators to current share and therefore distribute the power dissipation equally between the regulators. The problem is that, in order to equally current share you need to sense both currents and force the slave regulator to match the master regulator. This can be done, but at the cost of the circuit complexity and much higher system cost and the total power dissipation is still the same. In fact, if the task is to design a flexible motherboard to accommodate the Cyrix 6X86L or their future MMX processors, then the power dissipation could easily reach 20W or more. At this power dissipation level the choice for a switching regulator approach becomes evident. However, the main reason that designers have always shied away from the switching regulators is their higher price tag and more complex circuit design that is associated with this kind of technique.

The IRU3033 device is designed to take advantage of the high efficiency of the switching regulator technique for the Core supply while maintaining the low cost LDO regulator for the I/O supply by offering both control functions in a single 8-pin surface mount package. In fact as the typical application circuit shows, one can design a complete flexible motherboard using the IRU3033 and a few external components yielding a very low component count switching regulator and with an addition of a

low cost pass transistor for the I/O supply provide a complete dual supply power solution.

LDO Section

The output voltage of the LDO regulator is externally programmable via 2 external resistors from 1.25V to 5V. The internal voltage reference of the LDO regulator is set to 1.25V and the output of the regulator can be programmed using the following formula:

Vout=(1+R1/R2)xVref

Where Vref=1.25V Typical

R1=Resistor connected from Vout to the Vfb2 pin of IRU3033

R2=Resistor connected from Vfb2 pin to GND.

The IRU3033 requires the use of an output capacitor as part of the frequency compensation in order to be stable. Typical designs for the microprocessor applications use standard electrolytic capacitors with typical ESR in the range of 50 to $100m\Omega$ and an output capacitance of 500 to $1000\mu F$. Fortunately as the capacitance increases, the ESR decreases resulting in a fixed RC time constant. The IRU3033 takes advantage of this phenomena in making the overall regulator loop stable. For most applications a minimum of $100\mu F$ aluminum electrolytic capacitor such as Sanyo, MVGX series, Panasonic FA series or Nichicon PL series insures both stability and good transient response.

An external filtering is suggested as shown in the application circuit that reduces the switching ripple that might show in the output of the LDO regulator.

Switching Controller Operation

The operation of the switching controller is as follows:

After the power is applied, the output drive, "Drv1" goes to 100% duty cycle and the current in the inductor charges the output capacitor causing the output voltage to increase. When output reaches a pre-programmed set point the feedback pin "Fb1" exceeds 1.25V causing the output drive to switch low and the "Vhyst" pin to switch high which jumps the feedback pin higher than 1.25V resulting in a fixed output ripple which is given by the following equation:

 $\Delta Vo=(Rt/Rh)x11$

Where:

Rt=Top resistor of the output divider, resistor connected from Vout to the Vfb1 pin of IRU3033

4-84 Rev. 1.5

Rh=Bottom resistor of the divider, resistor connected from Vfb1 pin to Vhyst pin.

For example, if Rt=1k and Rh=422k, then the output ripple is:

 Δ Vo=(1/422)x11=26mV

The advantage of fixed output ripple is that when the output voltage changes from 2V to 3.5V, the ripple voltage remains the same which is important in meeting the Intel maximum tolerance specification.

Switcher Output Voltage Setting

The output voltage of the switcher can be set using the following equations:

Assuming, Vo=3.38V and the selected output ripple is \approx 1.3%(44mV) of the output voltage, a set of equations are derived that selects the resistor divider and the hysterises resistor.

Assuming, Rt=1k Ω , 1%

 $Rh=(11*Rt)/\Delta V$

Where:

Rt=Top resistor of the resistor divider

Rh=Hysterises resistor connected between pins 3 and 4 of the IRU3033

 Δ Vo=Selected output ripple (typically 1% to 2% of output voltage)

Assuming, Δ Vo=44mV Rh=(11*1000)/0.044=250k Ω Select Rh=249k Ω , 1%

The bottom resistor of the divider is then calculated using the following equations:

Rb=Rt/X

Where:

Rb=Bottom resistor of the divider

 $X=[(Vo + (\Delta Vo/2))/Vref] - 1$

Vref=1.25 V typical

X=[(3.38+(0.044/2))/1.25] - 1 = 1.72

Rb= $1000/1.72=580\Omega$

Select Rb=576 Ω , 1%

Frequency Calculation

The IRU3033 frequency of operation is calculated using the following formula:

 $Fs=[(Vo*(1-D)*ESR)]/(L*\Delta Vo)$ (MHz)

Where:

Vo=Output voltage (V)

D=Duty cycle

ESR=Output capacitor ESR (V)

L=Output inductance (µH)

 Δ Vo=Output ripple voltage (V)

For our example:

D≈(Vo + Vf)/Vin

Where, Vf=Forward voltage drop of the Schottky diode

D=(3.38 + 0.5)/5=0.78

The ESR=18m Ω for 2 of the Sanyo 1500 μ F, 6MV1500GX caps. If L=3.5 μ H then, Fs is calculated as follows:

Fs=[(3.38*(1-0.78)*0.018)]/(3.5*0.044)=0.087Mhz= 87kHz

IRU3033 Notes