

CS5360

24-Bit Stereo A/D Converter for Digital Audio

The following information is based on the technical datasheet:

CS5360 DS280PP1 SEP '97

Please contact Cirrus Logic : Crystal Semiconductor Products Division for further information.

CRYSTAL SEMICONDUCTOR PRODUCTS DIVISION PRODUCT INFORMATION

Copyright © Cirrus Logic, Inc. 1998
(All Rights Reserved)

PI280PP1 MAR '98

24-Bit Stereo A/D Converter for Digital Audio

Features


- 24 Bit Digital Output
- 105 dB Dynamic Range
- -95 dB THD+N
- 128X Oversampling
- Fully Differential Inputs
- Linear Phase Digital Anti-Alias Filtering
 - 21.7 kHz passband ($F_s = 48\text{kHz}$)
 - 85 dB stop band attenuation
 - 0.0025 dB pass band ripple
- High Pass Filter - DC Offset Removal
- Peak Signal Level Detector
 - High Resolution and Bar Graph Modes
- Pin Compatible with CS5334 and CS5335

Description

The CS5360 is a 2-channel, single +5 V supply, 24-bit analog-to-digital converter for digital audio systems. The CS5360 performs sampling, analog-to-digital conversion and anti-alias filtering, generating 24-bit values for both left and right inputs in serial form. The output word rate can be up to 50 kHz per channel.

The CS5360 uses 4th-order, delta-sigma modulation with 128X oversampling followed by digital filtering and decimation, which removes the need for an external anti-alias filter. This ADC uses a differential architecture which provides excellent noise rejection.

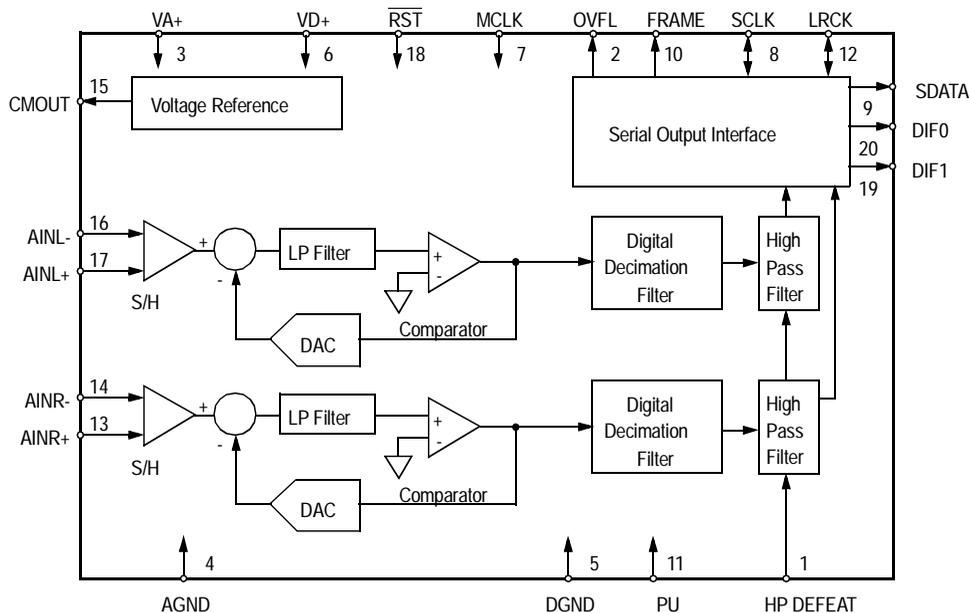The CS5360 has a filter passband to 21.7 kHz. The filter has linear phase, 0.0025 dB passband ripple, and >85 dB stopband rejection. An on-chip high pass filter is also included to remove DC offsets.



Overview

The CS5360 is a 24-bit, 2-channel analog-to-digital converter designed for digital audio applications. This device uses two one-bit delta-sigma modulators which simultaneously sample the analog input signals at 128 times the output sample rate (F_s). The resulting serial bit streams are digitally filtered, yielding a pair of 24-bit values. This technique yields nearly ideal conversion performance independent of input frequency and amplitude. The converter does not require difficult-to-design or expensive anti-alias filters and does not require external sample-and-hold amplifiers or a voltage reference. Very few external components are required to support this ADC. Normal power supply decoupling components and a resistor and capacitor on each input for anti-aliasing are all that's required.

An on-chip voltage reference provides for a differential input signal range of 2.0 Vrms. Output data is available in serial form, coded as 2's complement, 24-bit numbers. Typical power consumption is 325 mW which can be reduced to 1.0 mW by using the power-down feature.

FAQs

1) Is the CS5360 Crystal's lowest priced 24-bit converter?

A: Yes. The CS5360 is the lowest priced 24-bit converter offering 105 dB dynamic range and -95 dB total harmonic distortion + noise. Crystal also offers three higher performance 24-bit audio A/D converters - the CS5394, CS5396, and CS5397. The CS5394 offers 117 dB dynamic range with -103 dB THD+N and the CS5396 and CS5397 are the worlds only 24-bit, 96 kHz audio A/D converters. The CS5396 and CS5397 are also the first audio A/D converters to achieve 120 dB dynamic range.

2) When used with the CS4390 24-bit DAC, what is the dynamic range performance in loopback mode (analog in to analog out)?

A: 102-103 dB dynamic range.

3) What advantage does the high pass filter offer over traditional calibration techniques to reduce offsets?

A: The CS5360 high pass filter can remove both offsets in the input circuitry driving the ADC and internal offsets generated within the ADC. The use of a digital high pass filter technique to reduce offsets consistently produces a zero LSB offset which cannot be achieved with traditional calibration techniques.

4) Is the high pass filter defeatable for applications where DC information is important.

A: Yes.

- 5) How is the peak signal level detector used?
- A: The peak signal detector monitors the input signal level into the ADC and outputs 8 bits which correspond to the peak input level. These bits can be used to implement a low cost bar graph display. These 8 bits are output from the ADC following the audio data, and they indicate whether the input signal is clipping (5 dB above full scale) or -60 dB from full scale in 1 dB step resolution. The peak signal detector is updated by toggling the PU (peak update) pin.
- 6) How is the overflow output used?
- A: The OVFL pin goes high when the audio data exceeds the analog input range of the ADC. This pin can be used to light an LED on a system front panel indicating an overrange condition. This pin is cleared with the PU (peak update) pin.

Ordering Information

CS5360-KS -10° to 70°C 20-pin Plastic SSOP

For further information on Crystal products, please visit our website “www.crystal.com” or call our literature department (800) 888-5016 ext. 3594 or (512) 912-3594 for data sheets and application notes.

Schematic & Layout Review Service

Confirm Optimum
Schematic & Layout
Before Building Your Board.

For Our Free Review Service
Call Applications Engineering.



C a l l : (5 1 2) 4 4 5 - 7 2 2 2

Sales Office and Applications Support

UNITED STATES

Western Area

Cirrus Logic, Inc.
3100 West Warren Ave.
Fremont, CA 94538
Ph: 510-623-8300
FAX: 510-252-6020

Southern California, Sales
Westlake Village
The Townsgate Executive Bldg.
2659 Townsgate Road,
Suite 238
Westlake Village, CA 91361
Ph: 805-371-5860
FAX 805-371-5861

Cirrus Logic, Inc.
6650 S.W. Redwood Lane,
Ste. 105, First Floor Bldg. 16
Portland, Oregon 97224
Ph: 503-620-5547
FAX: 503-620-5665

Central Area

Cirrus Logic, Inc.
14205 Burnet Rd., Ste. 400
Austin, TX 78728
Ph: 512-255-8893
FAX: 512-255-0733

Sotheastern Area

Cirrus Logic, Inc..
5511 Capital Center Dr., Ste. 103
Raleigh, NC 27606
Ph: 919-859-5210
FAX: 919-859-5334

Northeastern Area

Cirrus Logic, Inc.
10 New England Business
Center, Ste. 100
Andover, MA 01810
Ph: 978-794-9992
FAX: 978-794-9998

Cirrus Logic, Inc.
10440 Little Patuxent Pkwy.,
Ste. 300
Columbia, MD 21044-3559
Ph: 410-740-5654
FAX: 410-740-6961

EUROPE

Cirrus Logic International SARL
Immeuble Andre Malraux
1 rue de Rome
F-93561 Rosny-sous-Bois
CEDEX, France
Ph: +33148122812
FAX: +33148122810

Cirrus Logic UK.
Angler's Court
4-5 Spittal St.
Marlow
Bucks, England SL7 1DB
Ph: +44(0)1628 472 211
FAX: +44(0)1628 486 114

Cirrus Logic GmbH
Muehlfelder-Strasse 2
D-82211 Herrsching, Germany
Ph: +49815292460
FAX: +498152924699

FAR EAST

China

Cirrus Logic International Ltd.
A-1403, Qiancun Commercial
Mansion
Beijing, China 100029
Ph: (8610)6443-0783
Ph: (8610)6443-0784
Ph: (8610)6443-0785
FAX: (8610)6443-0786

Hong Kong

Cirrus Logic International Ltd.
1203 Park Tower
15 Austin Rd., Tsimshatsui
Kowloon, Hong Kong
Ph: (852)2376-0801
FAX: (852)2375-1202

Korea

Cirrus Logic, Korea Co., Ltd.
Rm 1302 SangKyung
Bldg., 824-21 YeokSam-Dong,
Kang Nam-Ku,
Seoul, Korea
Ph: +82(2)565-8561
FAX: +82(2)565-8565

Singapore

Cirrus Logic
6 Kaki Bukit Ave. 1,
Ste. 03-03
Singapore 417940
Ph: +65-743-4111
FAX: +65-742-4111

Taiwan

Cirrus Logic International Ltd.
Taiwan Branch
10F, No.214 Tun Hwa North Rd.
Taipei, Taiwan R.O.C.
Ph: +886(22)718-4533
FAX: +886(22)718-4526

JAPAN

Cirrus Logic K.K.
Shinjuku Green Tower,
Bldg. 26F
6-14-1 Nishi-Shinjuku,
Shinjuku-ku,
Tokyo, 160
Japan
Ph: +81(03)3340-9111
FAX: +81(03)3340-9120



**CRYSTAL SEMICONDUCTOR
PRODUCTS DIVISION**

**PO BOX 17847
4210 S. INDUSTRIAL DRIVE
AUSTIN, TEXAS 78744
512.445.7222 / 800.888.5016
FAX: 512.445.7581**

**WORLDWIDE WEB:
<http://www.crystal.com>**